



# Introduction to Principles of Circuits

Nikolai Poliakov

(polyakov\_n\_a@itmo.ru)

Nikolay Nikolaev

(nanikolaev@itmo.ru)

- The course focuses on the analog and digital components of electronic circuits which can be used in control systems area.



<b>Nikolai Poliakov,</b>	<b>Arina Arbuzina</b>	<b>Nikolay Nikolaev,</b>	<b>Olga Kazachek Madina Sinetova</b>
Assoc. Prof.	Assistant Professor	Assoc. Prof.	Assistant Professor
<a href="mailto:polyakov_n_a@itmo.ru">polyakov_n_a@itmo.ru</a>	<a href="mailto:arbyzina99@gmail.com">arbyzina99@gmail.com</a>	<a href="mailto:nanikolaev@itmo.ru">nanikolaev@itmo.ru</a>	<a href="mailto:oakozachek@itmo.ru">oakozachek@itmo.ru</a> <a href="mailto:sinetovamadina@gmail.com">sinetovamadina@gmail.com</a>
Analog electronic circuits Lectons 1-7; Practice 1-4; Labs 1-3		Digital electronic circuits Lectons 8; Practice 5; Labs 4	

## Main course topics:

- Semiconductor materials;
- Components of analog electronics (diode, transistors (BJT and FET));
- Components of digital electronics (logic elements, flip-flops, encoders, decoders multiplexers, registers, counters);
- Operational amplifiers;
- Active filter;
- Simple analog and digital circuits design.

- In our course you will have:
- Lecture part – 9(10);
- Practice part – 5;
- Laboratory part – 4;
- Control tests – 4;
- Final written test.

# Course content (Week 1)

№	Class Type	Topic	Date		Score: +-min/+max
			AT	CS	
1	Lecture 1	Introduction in Principles of Circuits. Semiconductor materials and devices	21.10.2024	21.10.2024	Attendance: Min:+1/ Max:+2;
2	Lecture 2	Transistor circuits basics (BJT transistors, FET transistors, MOSFET transistors)	21.10.2024	21.10.2024	Attendance: Min:+1/ Max:+2;
3	Lab 1	Simple semiconductor device circuits design and simulation	22.10.2024	22.10.2024	Min:+1/ Max:+2;
4	Practice 1 (task)	Simple semiconductor device circuits design			Min:+1/ Max:+2;
5	Lecture 3.1	BJT, JFETs, MOSFET amplifier configurations	25.10.2024	25.10.2024	Attendance: Min:+1/ Max:+2;
6	Lecture 3.2		25.10.2024	25.10.2024	Attendance: Min:+1/ Max:+2;

№	Class Type	Topic	Date		Score:
			AT	CS	+ -min/+max
7	Practice 2 (task)	BJT, JFETs, MOSFET amplifier configuration	28.10.2024	28.10.2024	Min:+1/ Max:+2
8	Control test 1	Semiconductor materials and devices. BJT, JFETs, MOSFET amplifier configuration (Comprehension check/theory control test)			Min:+6/ Max:+10;
9	Lecture 4	Operational amplifiers: ideal operational amplifier and its characteristics	29.10.2024	29.10.2024	Attendance: Min:+1/ Max:+2;
9	Lecture 5	Operational amplifiers circuits design basics	29.10.2024	29.10.2024	Attendance: Min:+1/ Max:+2;
11	Lab 2	Operational amplifiers circuits design and simulation	30.10.2024	29.10.2024	Min:+1/ Max:+2;
12	Practice 3 (task)	Operational amplifiers circuits design	31.10.2024	30.10.2024	Min:+1/ Max:+2;
13	Control test 2	Operational amplifiers: ideal operational amplifier and its characteristics. Operational amplifiers circuits design basics (Comprehension check/theory control test)			Min:+6/ Max:+10;
14	Lecture 6	Filter theory introduction	01.11.2024	01.11.2024	Attendance: Min:+1/ Max:+2;
15	Lecture 7	Active filter circuits design	01.11.2024	01.11.2024	Attendance: Min:+1/ Max:+2;

№	Class Type	Topic	Date		Score: +-min/+max
			AT	CS	
16	Lab 3	Active filter circuits design and simulation	04.11.2024	04.11.2024	Min:+1/ Max:+3;
17	Practice 4 (task)	Active filter circuits design	06.11.2024	06.11.2024	Min:+1/ Max:+2;
18	Control test 3	Filter theory introduction. Active filter circuits design. (Comprehension check)			Min:+6/ Max:+10;

Week	№	Class Type	Topic	Date		Score: +-min/+max
				AT	CS	
4	19	Lecture 8	Digital circuits design basics. Transistor switch logic families (DTL, TTL, ESL, MOSFET)	15.11.2024	15.11.2024	Attendance: Min:+1/ Max:+2;
5	20	Lecture 9	Digital circuits design basics. Flip-flops (SR, D, JK), Decoders, Decoders Multiplexers, Registers, Counters	19.11.2024	19.11.2024	Attendance: Min:+1/ Max:+2;
	21	Lab 4	Simple digital circuits design and simulation	18.11.2024	21.11.2024	Min:+1/ Max:+3;
	22	Practice 5 (task)	Simple digital circuits design	20.11.2024	22.11.2024	Min:+1/ Max:+2
	23	Control test 4	Digital circuits design basics. Transistor switch logic families (DTL, TTL, ESL, MOSFET). Flip-flops (SR, D, JK), Decoders, Decoders Multiplexers, Registers, Counters (Comprehension check)			Min:+6/ Max:+10;
6	24	Final test	Consultation Final written test	25.11.2024	26.11.2024	Min:+12/ Max:+20;









# Semiconductor materials and devices

Nikolai Poliakov


(polyakov\_n\_a@itmo.ru)

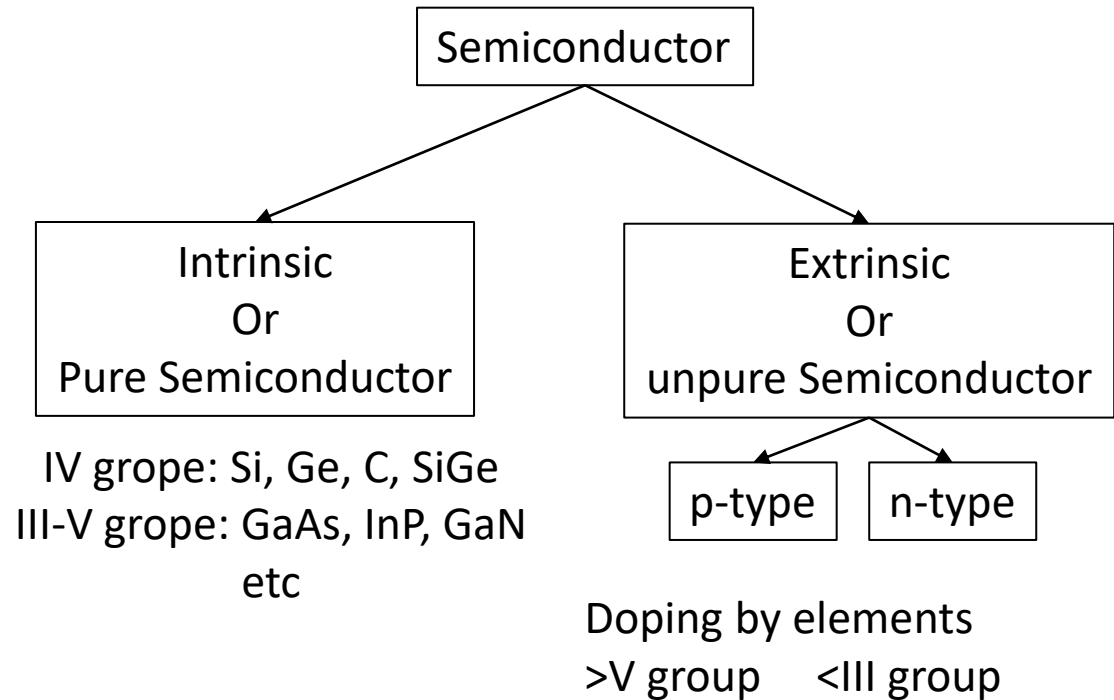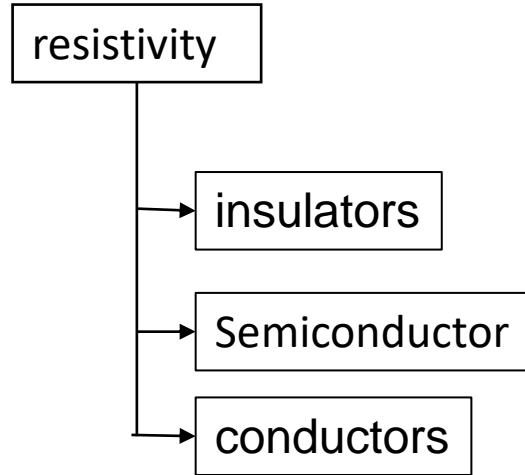

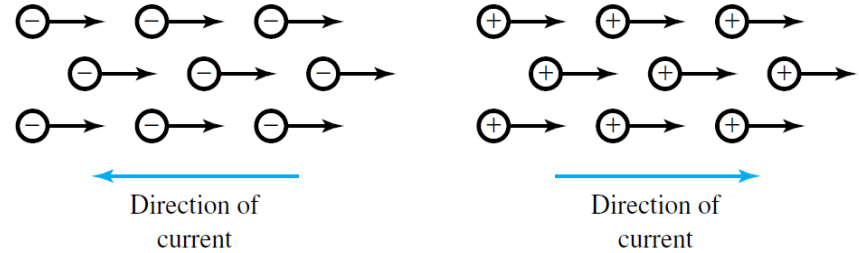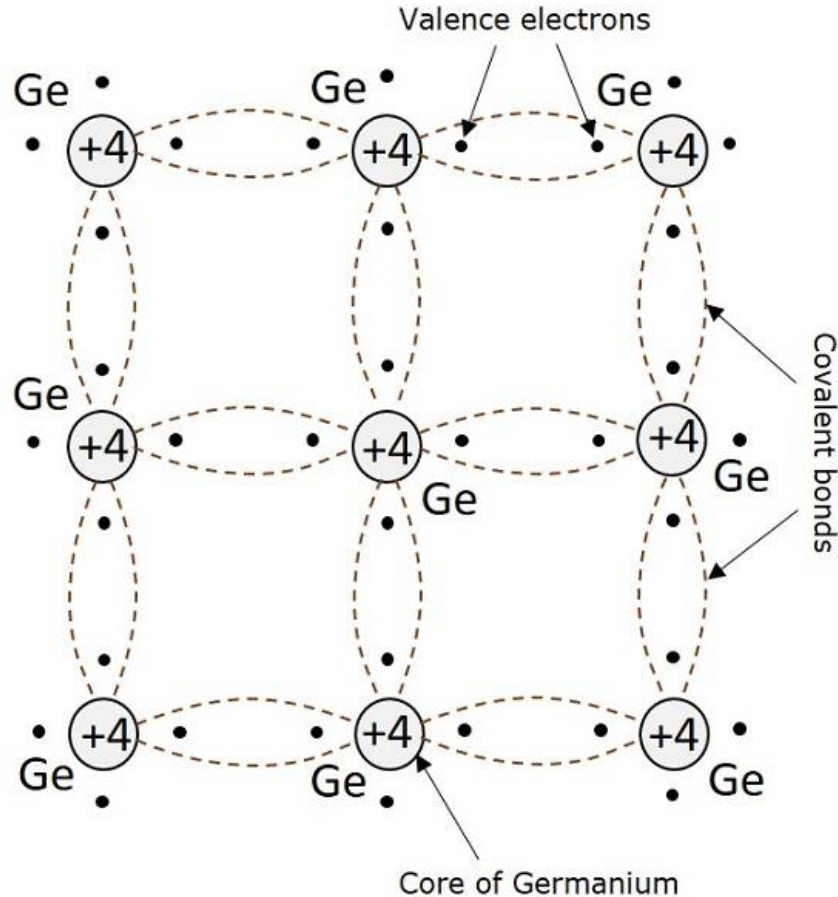




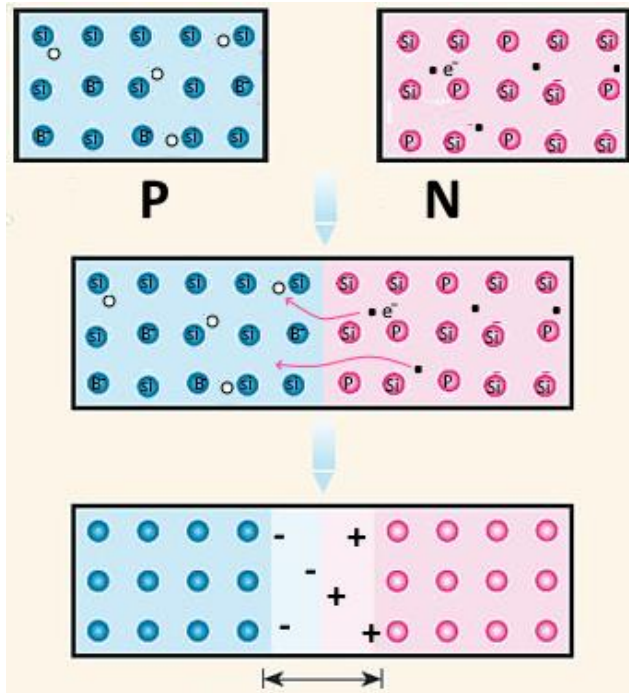
- (a)
- Electrical conduction.
  - **(a)** Electrons moving from left to right give rise to a current directed from right to left.
- (b)
- **(b)** Holes moving from left to right give rise to a current directed from left to right.




- The energy band gap is 0.7eV, whereas it is 0.2eV for germanium.
- The thermal pair generation is smaller.
- The formation of SiO<sub>2</sub> layer is easy for silicon, which helps in the manufacture of many components along with integration technology.
- Si is easily found in nature than Ge.
- Noise is less in components made up of Si than in Ge.



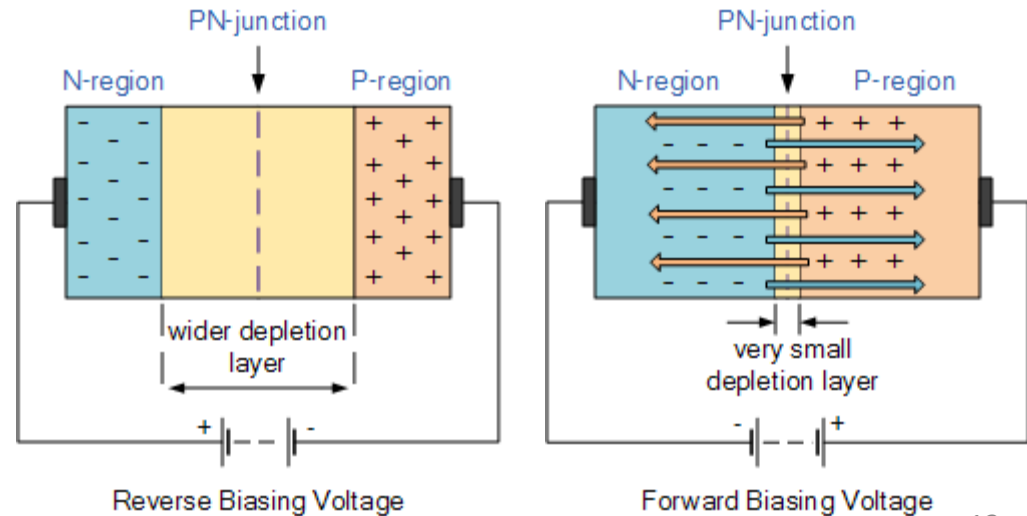
- N-type material has electrons as majority carriers and few holes as minority carriers.
- P-type material has holes as majority carriers and few electrons as minority carriers.



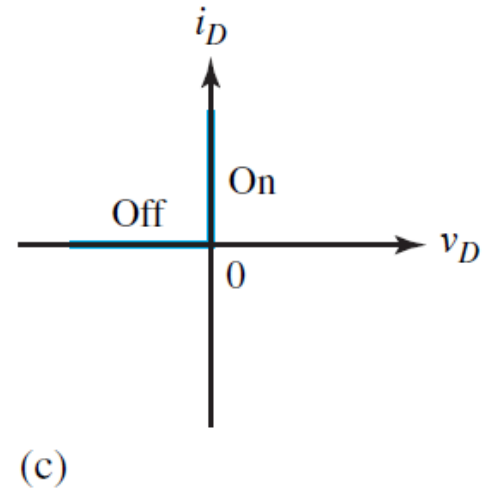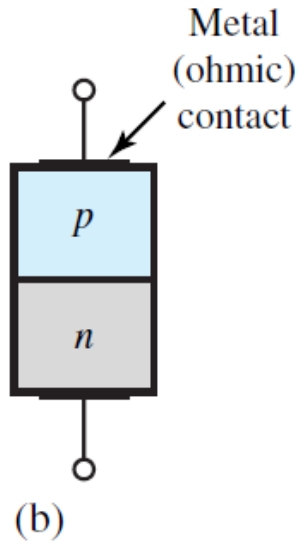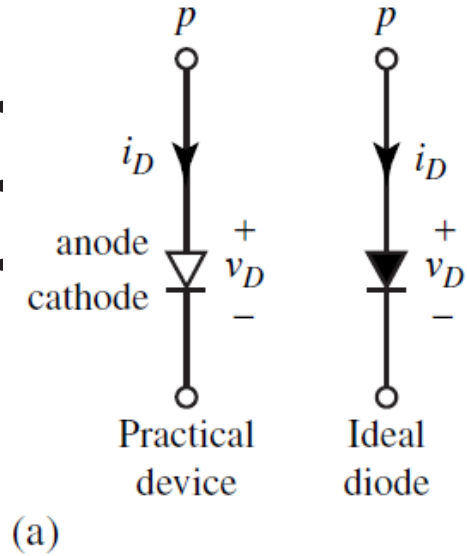

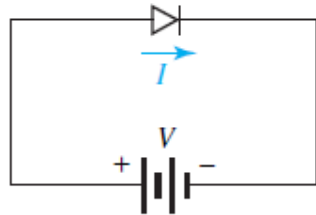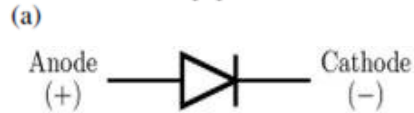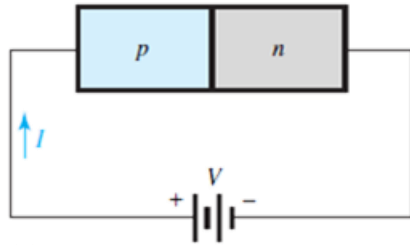

(b)

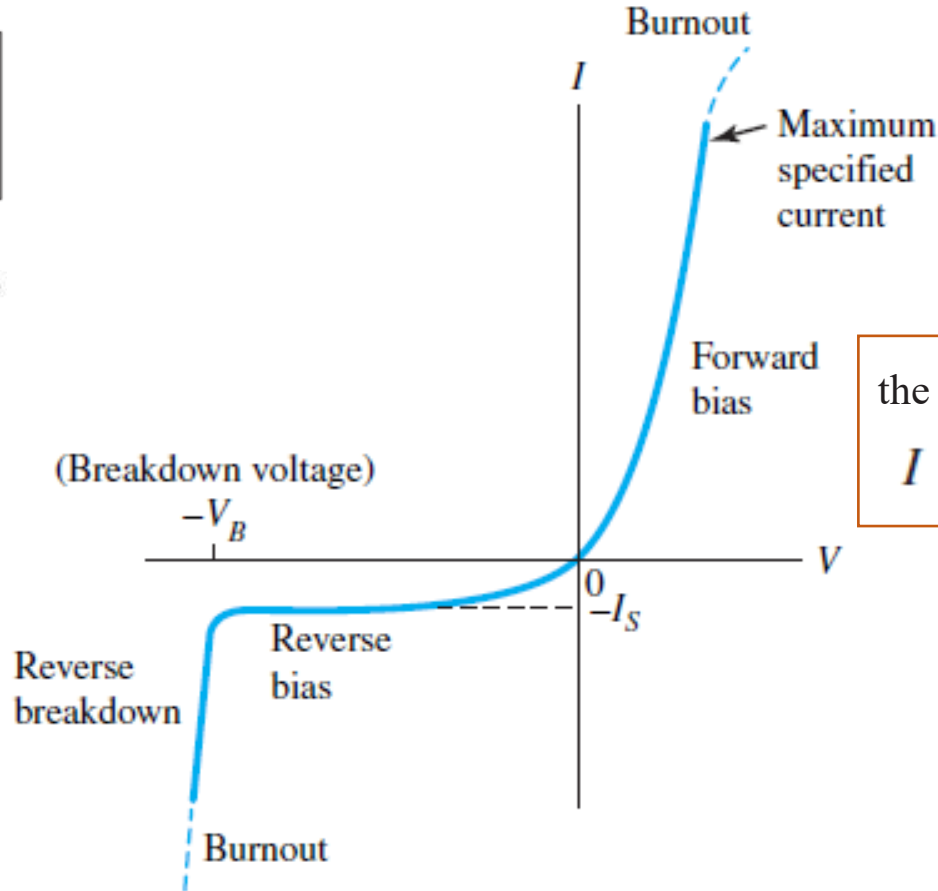


the Boltzmann diode equation

$$I = I_S(e^{V/\eta V_T} - 1)$$


$$V_T = \frac{kT}{q}$$

$$\eta = \begin{cases} 1, & \text{for Si} \\ 2, & \text{for Ge} \end{cases}$$


## Transition Capacitance

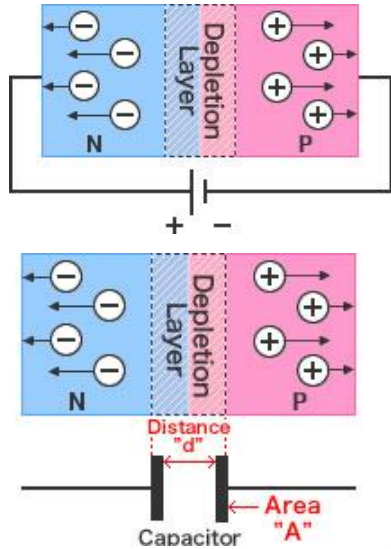
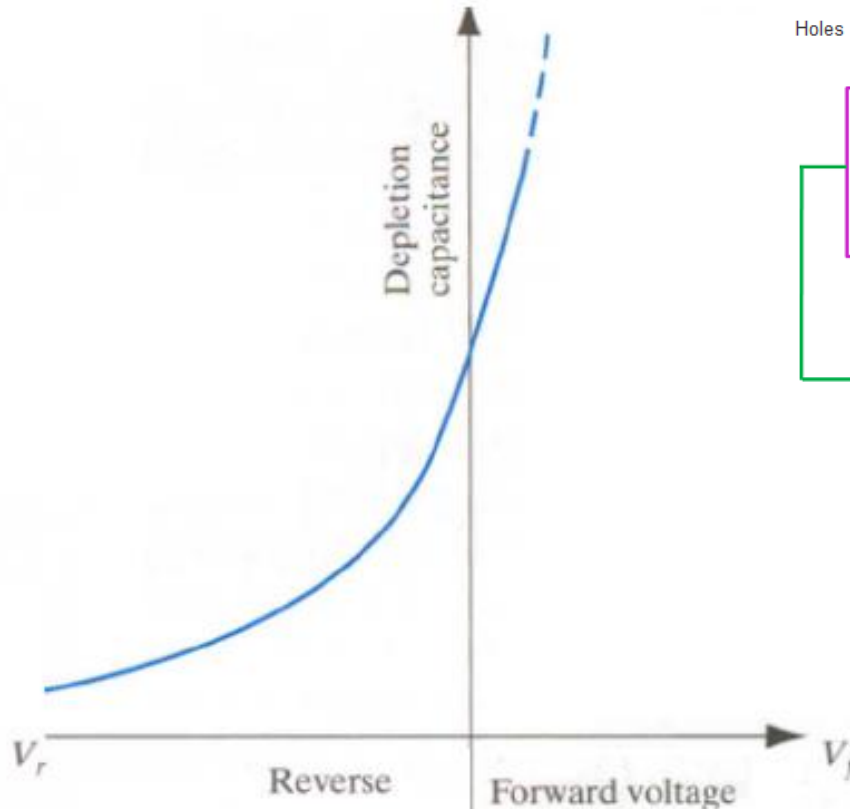
$$\text{Capacitance}(C_t) = \epsilon \frac{\text{Area "A"}}{\text{Distance "d"}}$$



## Diffusion Capacitance

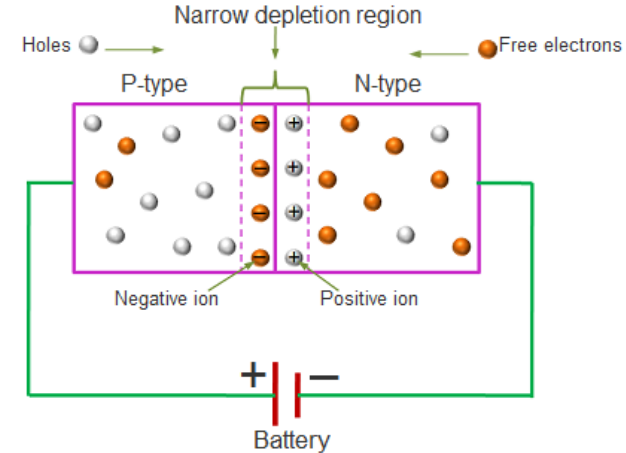

Forward bias

$$C_D = dQ / dV$$

$dQ$  = Change in number of minority carriers stored outside the depletion region

$dV$  = Change in voltage applied across diode




## Diode breakdown

Reversible:  
*Zener breakdown*  
(at low voltages)  
*Avalanche breakdown*  
(at higher voltages)

Irreversible:  
thermal  
breakdown

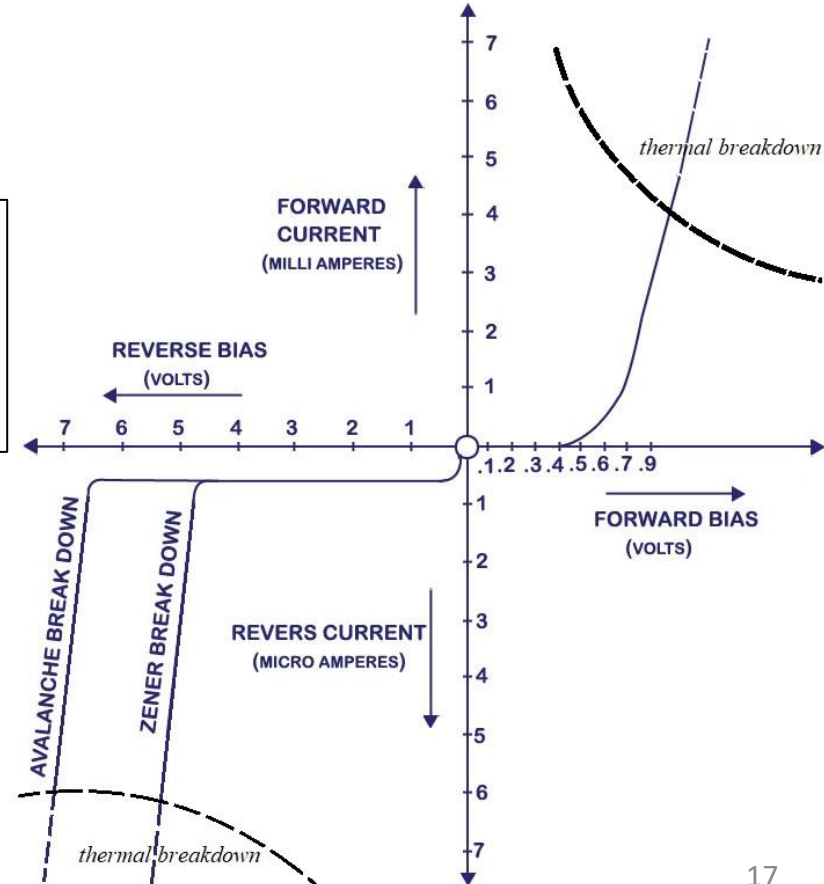Zener and Avalanche breakdown  
find application in stabilitrons.



## By used material


- Si
- Ge
- GaAs
- etc

## By type of p-n junction

- p-n junction
- pin junction
- metal-semiconductor junctions
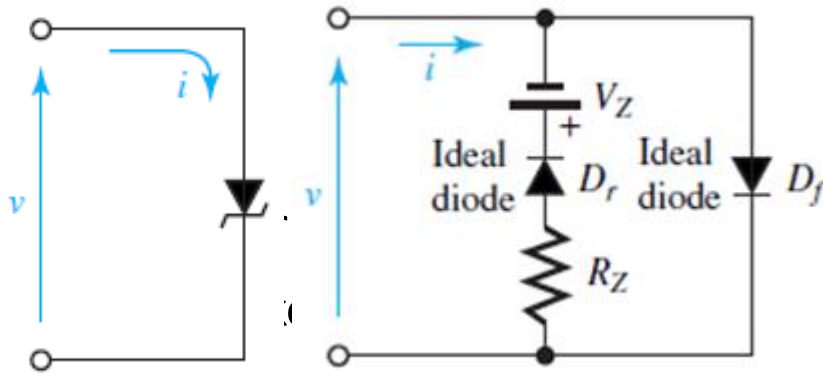
## By purpose


- Rectifying diodes
- Zener Diode
- Schottky Diode
- Tunnel Diode
- Light Emitting Diode (LED)
- Laser Diode (LD)
- Transient Voltage Suppression Diode
- Peltier Diode
- Avalanche Diode
- etc



## Main parameters:

Zener Voltage  $V_Z$



Breakover Current  $I_{ZK}$

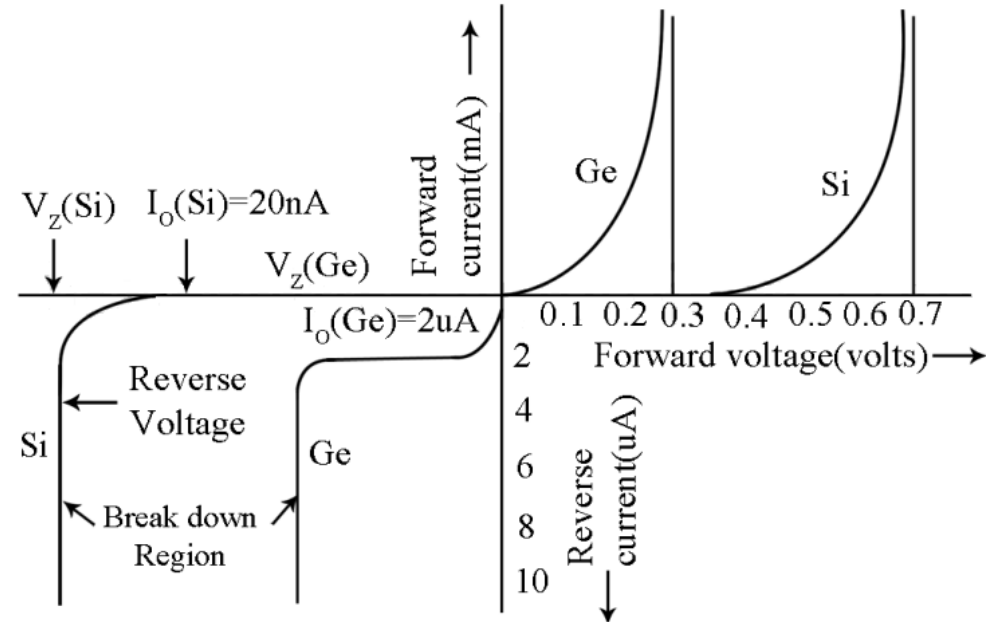


Power Dissipation

Dynamic Impedance

Effect of Temperature on  $V_Z$  Voltage

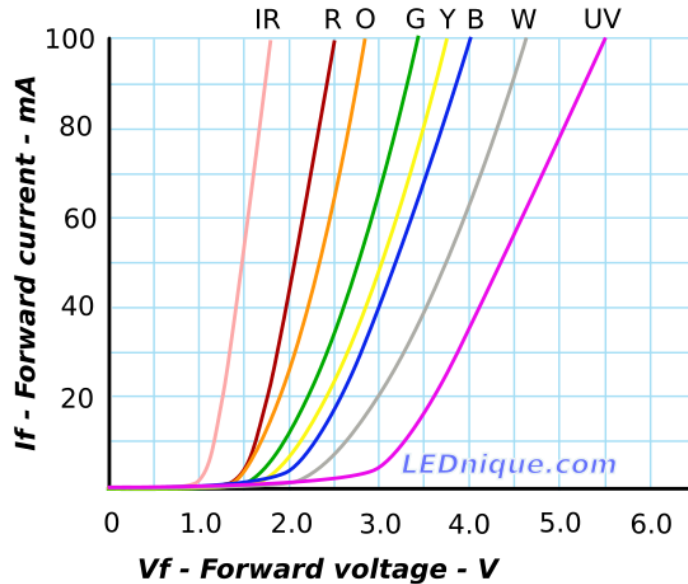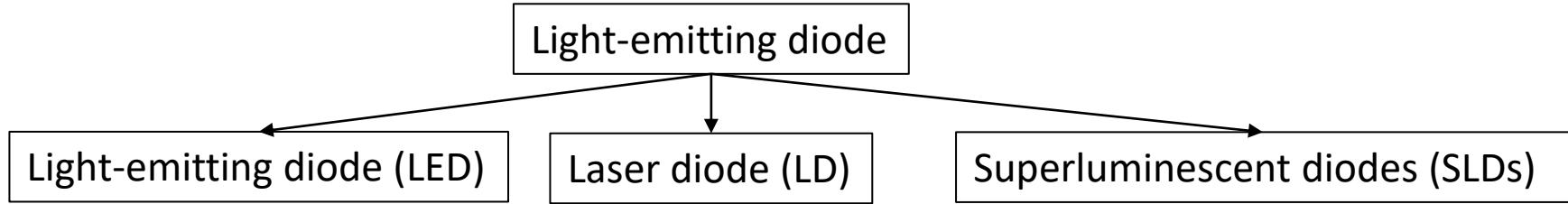

Typical LED Characteristics			
Semiconductor Material	Wavelength	Colour	V <sub>F</sub> @ 20mA
GaAs	850-940nm	Infra-Red	1.2v
GaAsP	630-660nm	Red	1.8.v
GaAsP	605-620nm	Amber	2.0v
GaAsP:N	585-595nm	Yellow	2.2v
AlGaP	550-570nm	Green	3.5v
SiC	430-505nm	Blue	3.6v
GaInN	450nm	White	4.0v

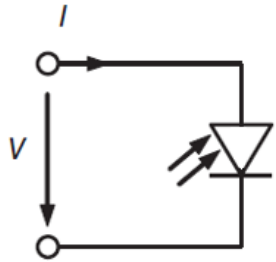

Load reference-arrow system



## Photodiode (PD)

pn-PD

pin-PD


APD (Avalanche-PD)

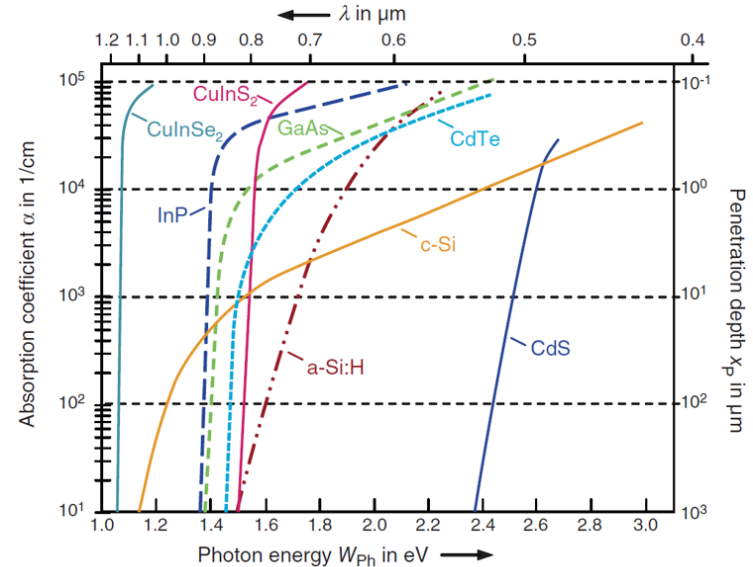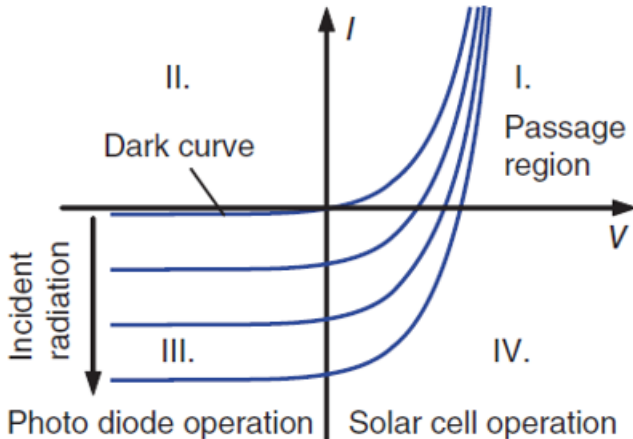This is the most basic photodiode. The physics of how the P-N junction photodiode operates was reviewed earlier. The PIN and APD photodiode are variations from the P-N junction.



Source: K. Mertens: textbook-pv.or

	P-N	PIN	APD
PHOTOVOLTAIC	Best	Good	Poor
REVERSE BIASED	Good	Best	Good
LOW LIGHT	Poor	Good	Best
COST	Best	Good	Poor
LOW NOISE	Good	Best	Poor

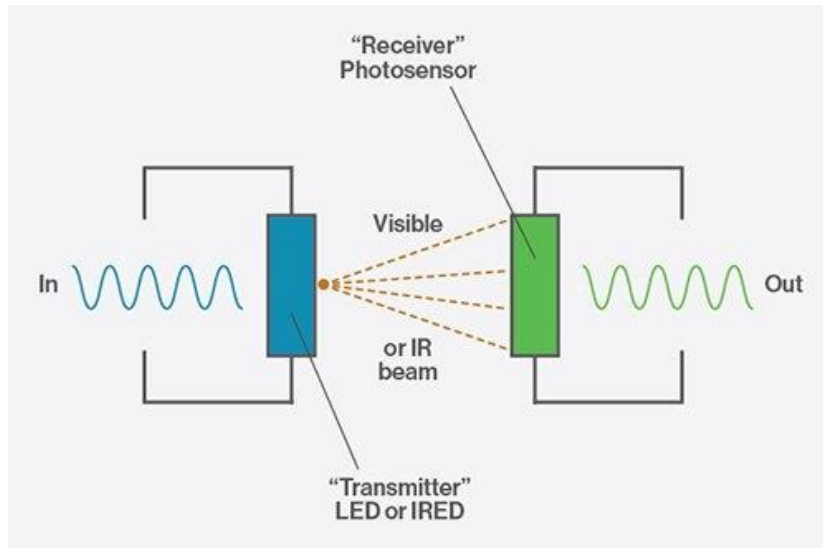

The Current – Transfer – Ratio (CTR)

$$CTF = \frac{I_C}{I_F} * 100\%$$

were:

$I_F$  – current flowing through the LED,

$I_C$  – current flowing through the photosensor

An Optocoupler Can Effectively:

- Remove electrical noise from signals
- Isolate low-voltage devices from high-voltage circuits. The device is able to avoid disruptions from voltage surges (ex: from radio frequency transmissions, lightning strikes, and spikes in a power supply)
- Allow the usage of small digital signals to control larger AC voltages

	Rectifier diode	Zener diode	LED	PD
Forward bias	✓	X	✓	X
Reverse bias	✓	✓	X	✓
Reverse breakdown	X	✓	X	X













# Elementary Diode Circuits

Nikolai Poliakov

(polyakov\_n\_a@itmo.ru)

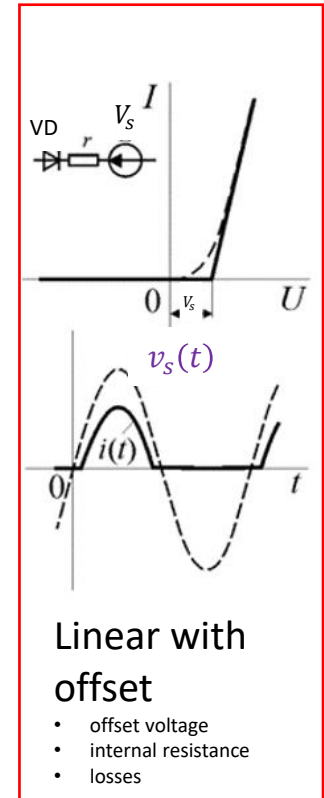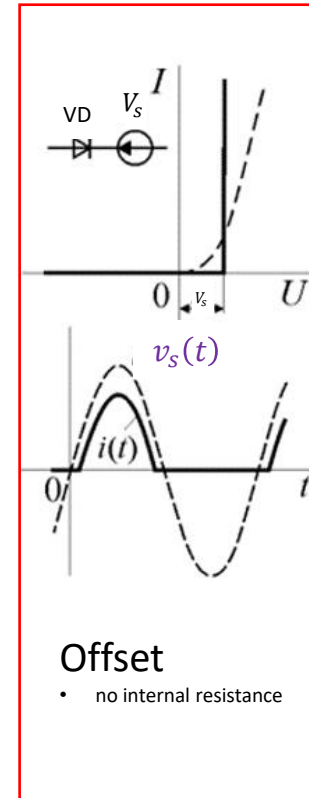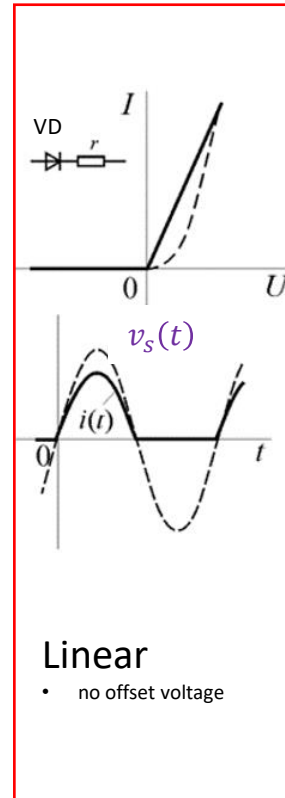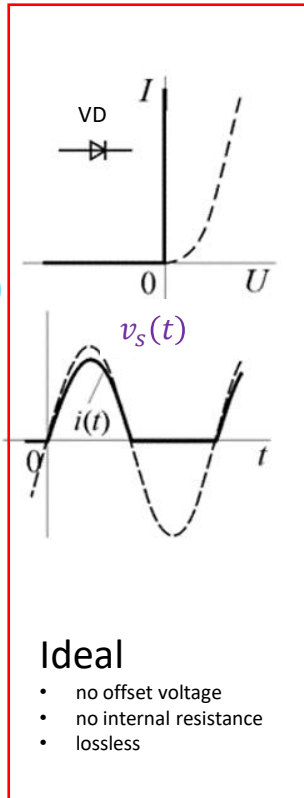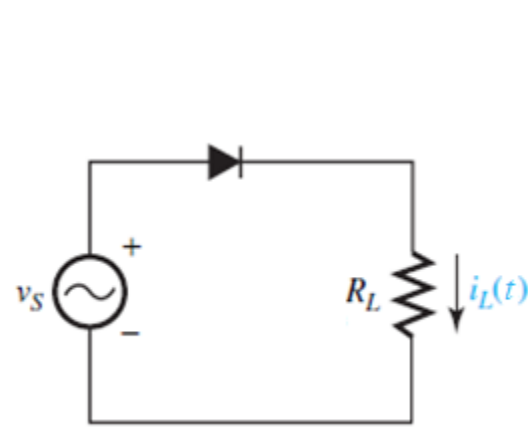

# Voltage limiter

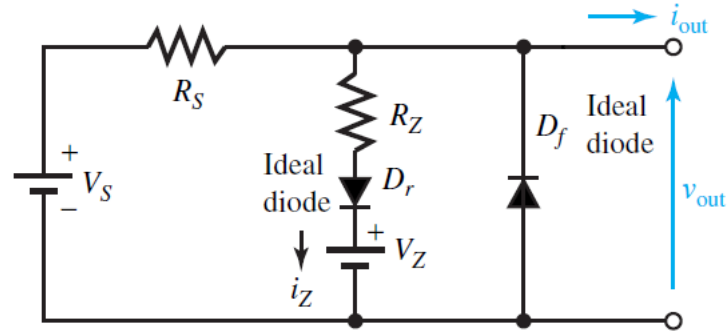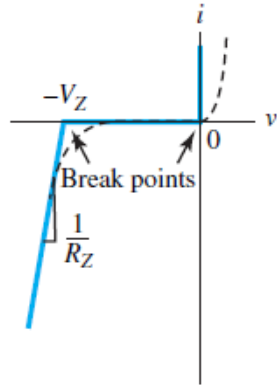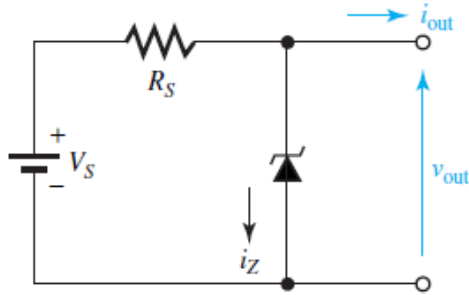

$$V_S > V_Z$$

The forward diode  $D_f$  and reverse diode  $D_r$  will be off

$$V_S - R_S i_{out} < V_Z$$

$$v_{out} \cong V_S$$


The forward diode  $D_f$  will be off while the reverse diode  $D_r$  is on

$$V_S - R_S i_{out} > V_Z$$

$$v_{out} \cong V_Z$$
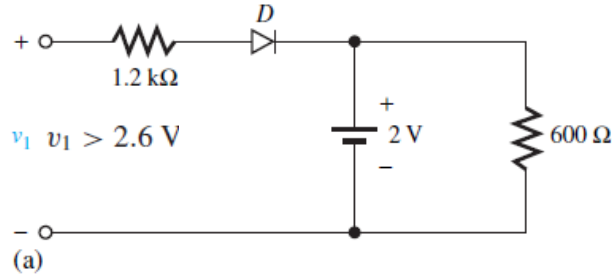
# One-way limiter circuit


- Use the offset diode model with a threshold voltage of 0.6 V to determine the value of  $v_1$  for which the diode D will first conduct



$$v_1 = v_D + 0.6 + 2$$

$$v_0 = 2$$

$$v_D = v_1 - 2.6$$

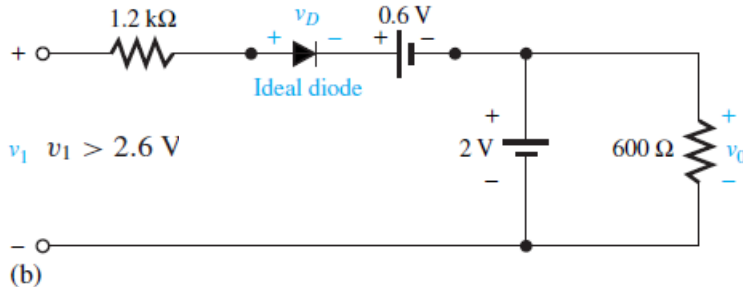

The background is a dark purple grid. In the top right and bottom left corners, there are decorative wavy lines in a lighter purple color, resembling smoke or liquid splashes.

**iTMO**

# **Elementary rectifiers circuits**







## AC Voltage:

- ~50 countries 100-127V
- ~200 countries 220-240V
- ~180 countries 50Hz
- ~50 countries 60Hz

Why do we use AC voltage?

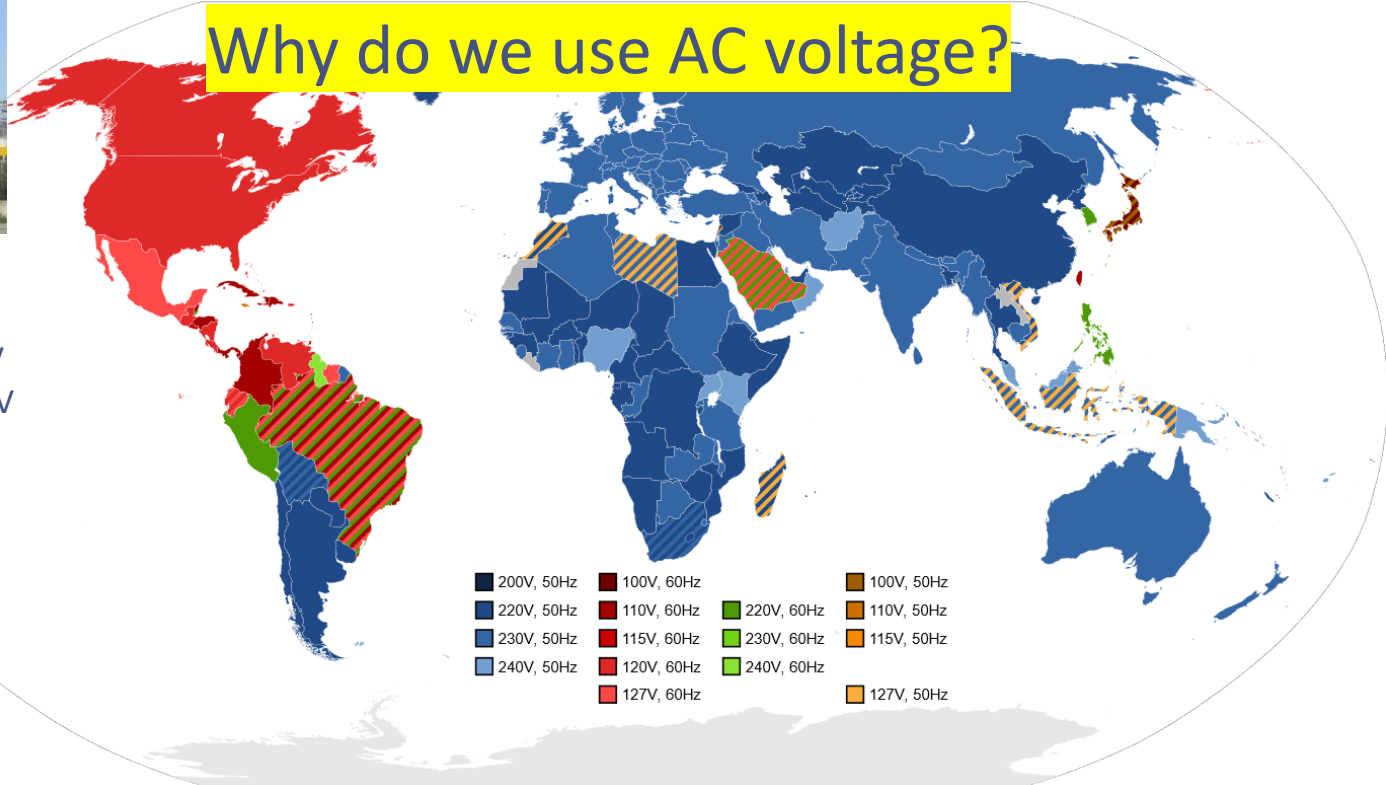

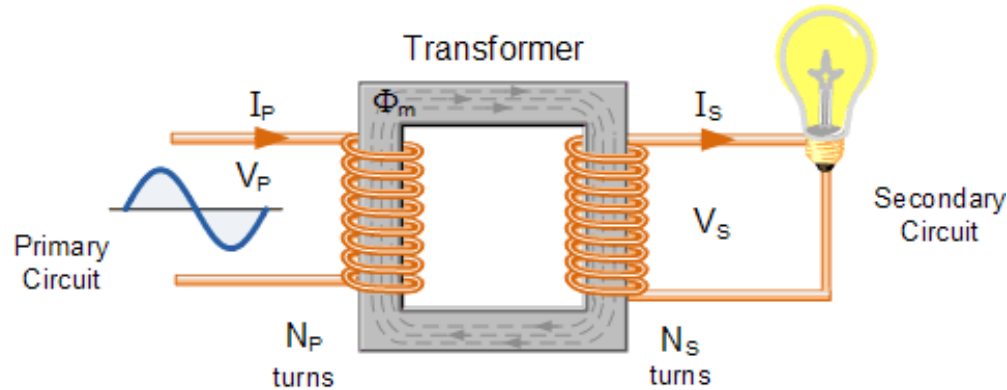

Transformers!

✓ Only AC amplitude changes

✓ Very efficient!

Power losses reduces with voltage increase

$$P_{losses} = I^2 * R$$

If

$$P_{total} = UI = P_{load} + P_{losses} = \text{CONST}$$

and if  $U \uparrow$


then  $I \downarrow$

and consequently,

✓  $P_{losses} \downarrow$



# Half-Wave Rectifier (HWR)

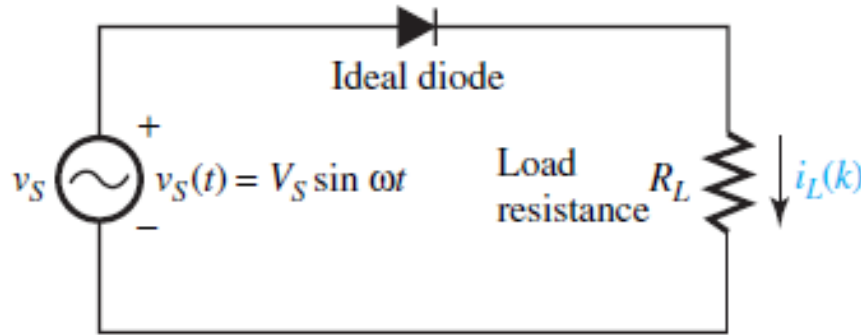



Source voltage  $v_S(t)$


$$v_S(t) = V_S \cdot \sin(f \cdot 2\pi \cdot t) = V_S \cdot \sin(\omega \cdot t)$$

$$V_{S_{RMS}} = \frac{V_S}{\sqrt{2}}$$

Voltage on the load resistance  $R_L$
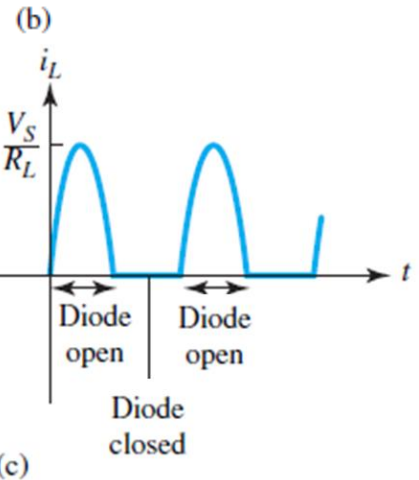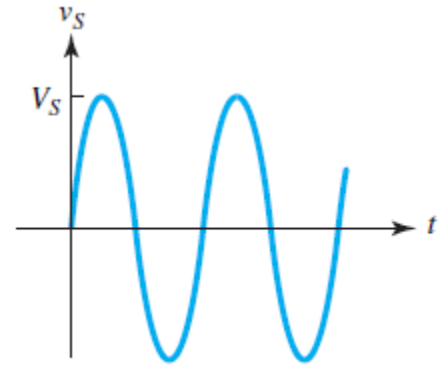
$$v_{R_L}(t) = \begin{cases} 0, & \text{if } v_S(t) \leq 0 \\ v_S(t), & \text{if } v_S(t) > 0 \end{cases}$$




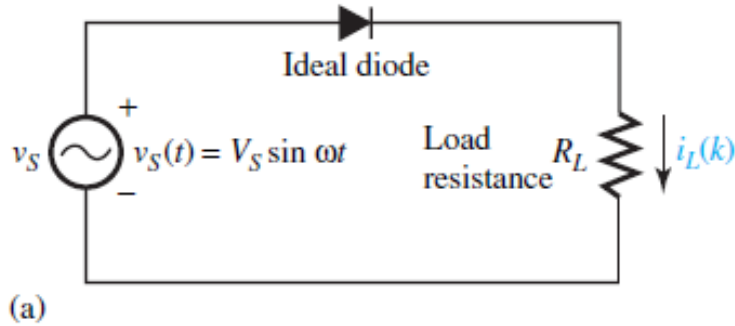


$$v_{R_L}(t) = \begin{cases} 0, & \text{if } v_S(t) \leq 0 \\ v_S(t), & \text{if } v_S(t) > 0 \end{cases}$$

Load voltage is the sum of the DC ( $V_{R_{L_{AVG}}}$ ) and AC ( $v_{R_{L\sim}}(t)$ ) components
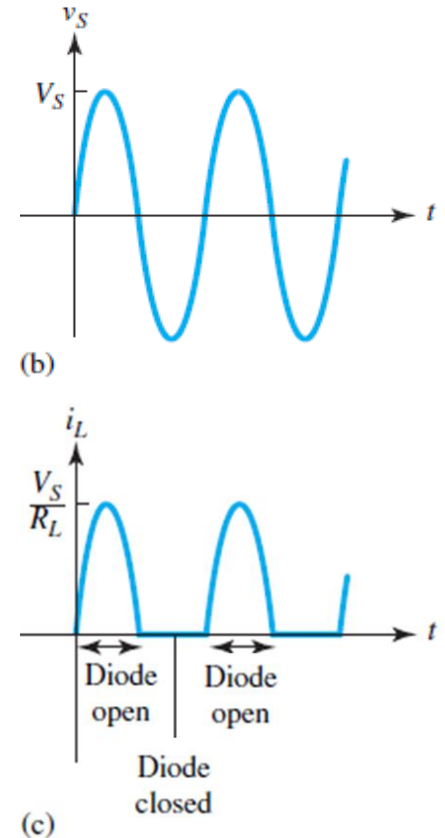
$$v_{R_L}(t) = V_{R_{L_{AVG}}} + v_{R_{L\sim}}(t)$$



# Half-Wave Rectifier (HWR)

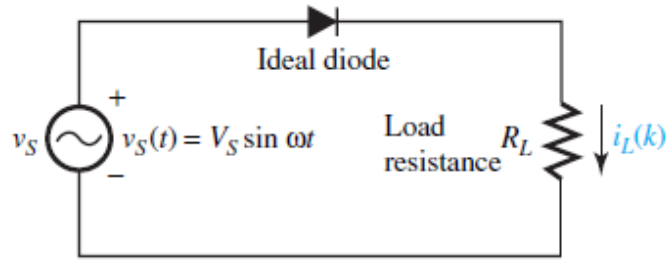

Source voltage  $v_s(t)$

$$v_s(t) = V_s \cdot \sin(f \cdot 2\pi \cdot t) = V_s \cdot \sin(\omega \cdot t)$$

Voltage on the load resistance  $R_L$

$$v_{R_L}(t) = \begin{cases} 0, & \text{if } v_s(t) \leq 0 \\ v_s(t), & \text{if } v_s(t) > 0 \end{cases}$$

Voltage on the load resistance is  $R_L$  a sum of DC voltage  $V_{R_{L_{AVG}}}$  and voltage ripple  $v_{R_{L\sim}}(t)$

$$v_{R_L}(t) = V_{R_{L_{AVG}}} + v_{R_{L\sim}}(t)$$

Average voltage on the load resistance  $R_L$  :

$$V_{R_{L_{AVG}}} = \int_0^{2\pi/\omega} V_s \cdot \sin(\omega \cdot t) dt = \int_0^T V_s \cdot \sin(\omega \cdot t) dt = \frac{V_s}{T \cdot \omega} \cos(\omega \cdot t) \Big|_0^{T/2} = \frac{V_s}{\pi} = \frac{\sqrt{2} \cdot V_{s_{RMS}}}{\pi} \approx 0.45 \cdot V_{s_{RMS}}$$

RMS value of the voltage on the load resistance  $R_L$  :

$$V_{R_{L\sim}RMS} = \sqrt{V_{R_{L1\sim}RMS}^2 + V_{R_{L2\sim}RMS}^2 + V_{R_{L3\sim}RMS}^2 + \dots + V_{R_{Ln\sim}RMS}^2} = \sqrt{V_{R_{LRMS}}^2 - V_{R_{L_{AVG}}}^2}$$

$$\text{Ripple factor } K_P = \frac{V_{R_{L\sim}RMS}}{V_{R_{L_{AVG}}}} = \sqrt{\frac{(V_{R_{LRMS}}^2 - V_{R_{L_{AVG}}}^2)}{V_{R_{L_{AVG}}}^2}} = \sqrt{\frac{V_{R_{LRMS}}^2}{V_{R_{L_{AVG}}}^2} - 1} = \sqrt{\left(\frac{\pi}{2}\right)^2 - 1} = 1.21$$

## Rectifier Main parameters

Average load voltage:

$$V_{RLAVG} = V_{SRMS}$$

RMS value of the variable voltage component

$$V_{RL \sim RMS} = \sqrt{V_{RLRMS}^2 - V_{RLAVG}^2}$$

RMS value of load current

$$I_L = \frac{V_S}{2 R_L} = 0.707 \frac{V_{SRMS}}{R_L}$$

RMS voltage on the load

$$V_{RLRMS}^2 \approx 0.707 V_{SRMS}$$

Average load current

$$I_{LAVG} \approx 0.45 \frac{V_{SRMS}}{R_L}$$

Ripple factor

$$K_p = \gamma = \sqrt{\left(\frac{V_{SRMS}}{V_{RLAVG}}\right)^2 - 1} = 1.21$$

## Diode Main parameters

Average current flowing through the diode

$$I_{VD AVG} = I_{LAVG} = 0.45 \frac{V_{SRMS}}{R_L}$$


Maximum reverse voltage across the diode

$$V_{VD max} = V_S$$

Maximum diode current

$$I_{VD max} = \frac{V_S}{R_L}$$

# Half-Wave Rectifier (HWR)

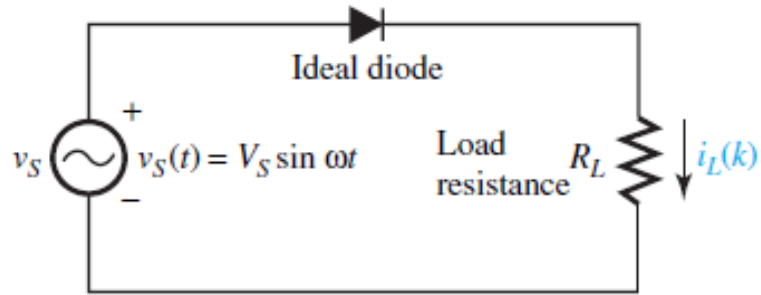

## Load parameters:

### Average load voltage

$$V_{R_{L_{AVG}}} = \frac{V_s}{\pi} = \frac{\sqrt{2}V_{S_{RMS}}}{\pi} \approx 0.45V_{S_{RMS}}$$

### RMS load voltage

$$V_{R_{L_{RMS}}} = \frac{V_s}{2} = \frac{V_{S_{RMS}}}{\sqrt{2}} \approx 0.707V_{S_{RMS}}$$

### Average load current

$$I_{L_{AVG}} = \frac{V_{R_{L_{AVG}}}}{R_L} = \frac{\sqrt{2}V_{S_{RMS}}}{\pi R_L} \approx 0.45 \frac{V_{S_{RMS}}}{R_L}$$

### RMS load current through diode

$$I_{L_{RMS}} = \frac{V_s}{2R_L} = \frac{V_{S_{RMS}}}{\sqrt{2}R_L} \approx 0.707 \frac{V_{R_{L_{RMS}}}}{R_L}$$

Source voltage  $v_s(t)$

$$v_s(t) = V_s \cdot \sin(f \cdot 2\pi \cdot t) = V_s \cdot \sin(\omega \cdot t)$$

Voltage on the load resistance  $R_L$

$$v_{R_L}(t) = \begin{cases} 0, & \text{if } v_s(t) \leq 0 \\ v_s(t), & \text{if } v_s(t) > 0 \end{cases}$$

## Diode parameters:

### Average diode current







$$I_{VD_{AVG}} = I_{L_{AVG}} = \frac{\sqrt{2}V_{S_{RMS}}}{\pi R_L} \approx 0.45 \frac{V_{S_{RMS}}}{R_L}$$

### MAX diode current

$$I_{VD_{max}} = \frac{V_s}{R_L}$$

### MAX diode reverse voltage

$$V_{VD_{max}} = V_s$$

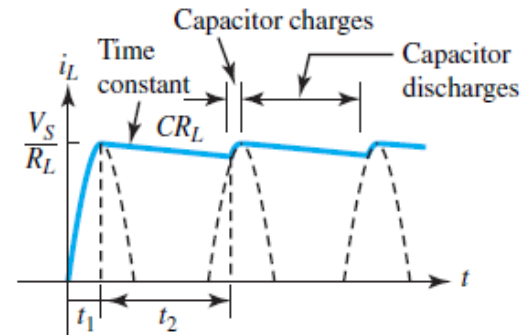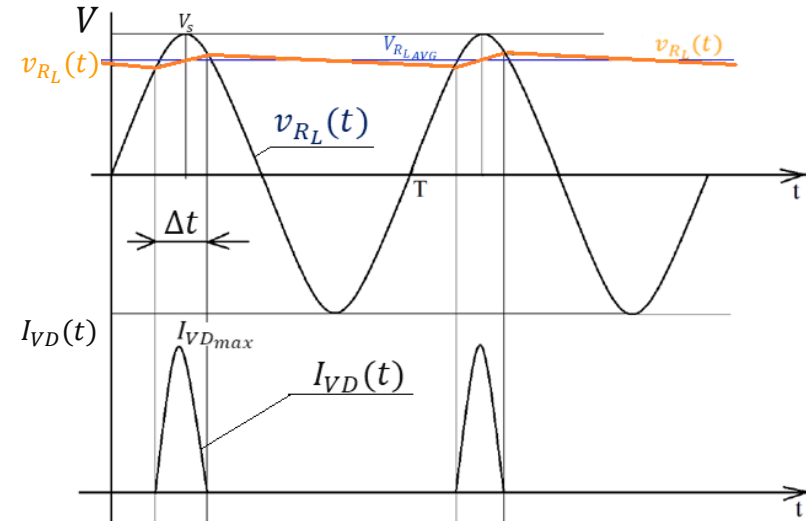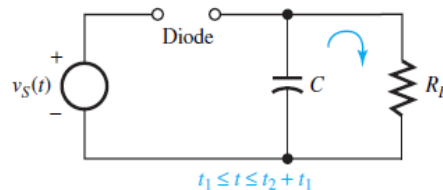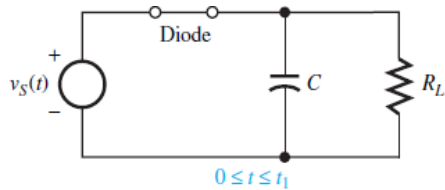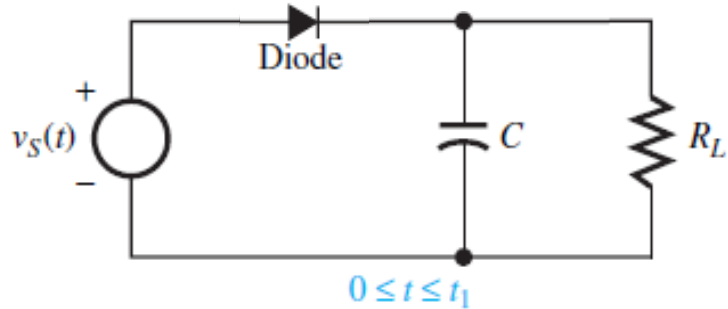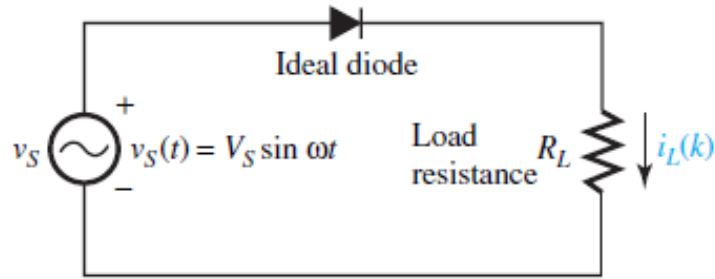

$$v_{RL}(t) = V_{RLAVG} + v_{RL\sim}(t) \approx V_{RL} = \text{const}$$

Diode Voltage

Average diode current

$$v_{VD}(t) = v_s(t) - V_{RLAVG} \quad I_{LAVG} = I_{VD AVG} = \frac{1}{T} \sqrt{\int_0^T I_{VD}(t) dt}$$

$$I_{LAVG} = \frac{1}{T} \sqrt{\int_{\frac{T}{4}-\theta/(2\omega)}^{\frac{T}{4}+\theta/(2\omega)} \frac{1}{r_{IN}} (V_s \cdot \sin(\omega \cdot t) - V_{RLAVG}) dt} = \frac{V_{RLAVG}}{R_L}$$

where

$$r_{IN} = r_{VD} + r_{VS}$$

$r_{VD}$

$r_{VS}$

$$\theta = \omega \cdot \Delta t = \frac{2\pi}{T} \cdot \Delta t$$

$\Delta t$

– input resistance of the rectifier




– diode resistance

– voltage source resistance

– angle of diode open state

– diode open state time interval
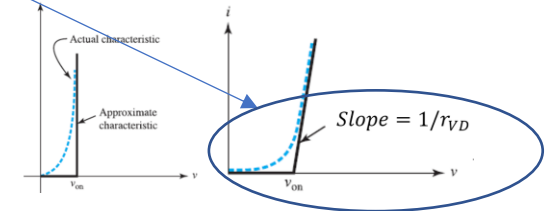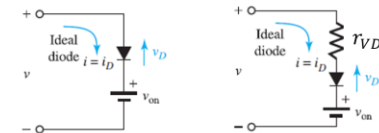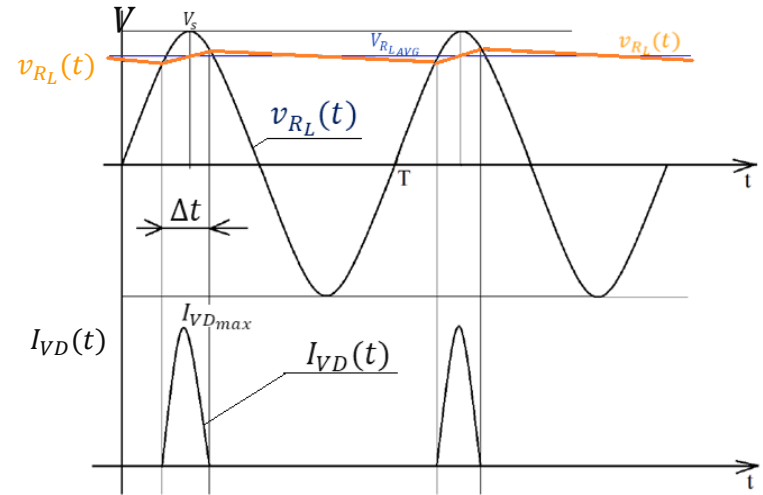
$$\frac{V_{RLAVG}}{V_s} = \frac{R_L}{\pi r_{IN}} \left( \sin\left(\frac{\theta}{2}\right) - \frac{V_{RLAVG}}{V_s} \frac{\theta}{2} \right)$$



Average diode current

$$I_{L_{AVG}} = \frac{1}{T} \int_{\frac{T}{4} - \frac{\theta}{2\omega}}^{\frac{T}{4} + \frac{\theta}{2\omega}} \frac{1}{r_{IN}} (V_S \cdot \sin(\omega \cdot t) - V_{R_{L_{AVG}}}) dt = \frac{V_{R_{L_{AVG}}}}{R_L}$$

where

$$r_{IN} = r_{VD} + r_{VS}$$

$r_{VD}$

$r_{VS}$

$$\theta = \omega \cdot \Delta t = \frac{2\pi}{T} \cdot \Delta t$$

$\Delta t$

– input resistance of the rectifier

– diode resistance

– voltage source resistance


– angle of diode open state

– diode open state time interval

$$\frac{V_{R_{L_{AVG}}}}{V_S} = \frac{R_L}{\pi r_{IN}} \left( \sin\left(\frac{\theta}{2}\right) - \frac{V_{R_{L_{AVG}}}}{V_S} \frac{\theta}{2} \right)$$

$$V_{VD} \left( \frac{T}{4} \pm \frac{\theta}{2\omega} \right) = V_S \sin\left(\omega \left( \frac{T}{4} \pm \frac{\theta}{2\omega} \right)\right) - V_{R_{L_{AVG}}} = 0 \Rightarrow V_{R_{L_{AVG}}} = V_S \left( \sin\left(\omega \left( \frac{T}{4} \pm \frac{\theta}{2\omega} \right)\right) \right) = V_S \sin\left(\frac{\pi}{2} \pm \frac{\theta}{2}\right)$$
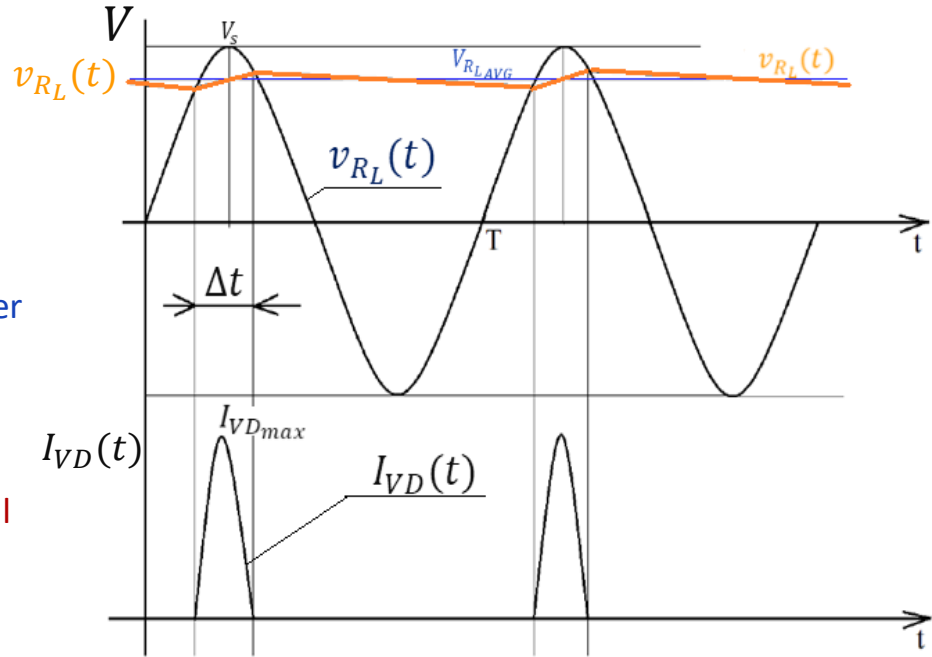
$$\frac{V_{R_{L_{AVG}}}}{V_S} = \cos\left(\frac{\theta}{2}\right) \Rightarrow \cos\left(\frac{\theta}{2}\right) = \frac{R_L}{\pi r_{IN}} \left( \sin\left(\frac{\theta}{2}\right) - \cos\left(\frac{\theta}{2}\right) \cdot \frac{\theta}{2} \right) \Rightarrow \frac{r_{IN}}{R_L} = \frac{1}{\pi} \left( \tan\left(\frac{\theta}{2}\right) - \frac{\theta}{2} \right)$$





From  $\frac{r_{IN}}{R_L} = \frac{1}{\pi} \left( \tan\left(\frac{\theta}{2}\right) - \frac{\theta}{2} \right)$

angle of diode open state  $\theta$  can be evaluated:

$$\tan\left(\frac{\theta}{2}\right) \approx \frac{\theta}{2} + \frac{1}{3}\left(\frac{\theta}{2}\right)^3 \Rightarrow \theta = 2 \cdot \sqrt[3]{3\pi \frac{r_{IN}}{R_L}}$$


Average load voltage:  $V_{R_{L_{AVG}}} = V_S \cos\left(\frac{\theta}{2}\right)$

Average diode current:  $I_{VD} = \frac{V_S}{R_L} \cos\left(\frac{\theta}{2}\right)$

Peak (repetitive) diode current:  $I_{VD_{max}} = \frac{V_S - V_{R_{L_{AVG}}}}{r_{IN}}$


Peak (turn on) diode current:  $I_{VD_{ON}} = \frac{V_S}{r_{IN}}$

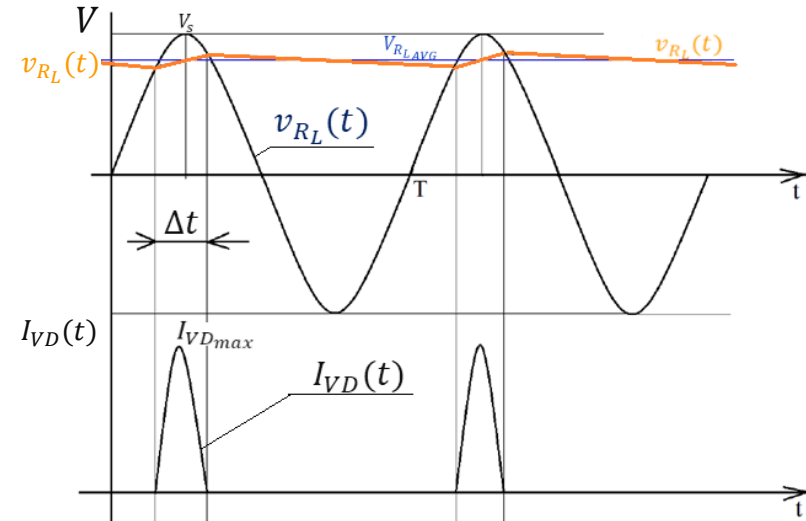Diode reverse voltage:  $V_{VD_{max}} = V_S + V_{R_{L_{AVG}}} \approx 2 \cdot V_S$



From the charge balance condition at
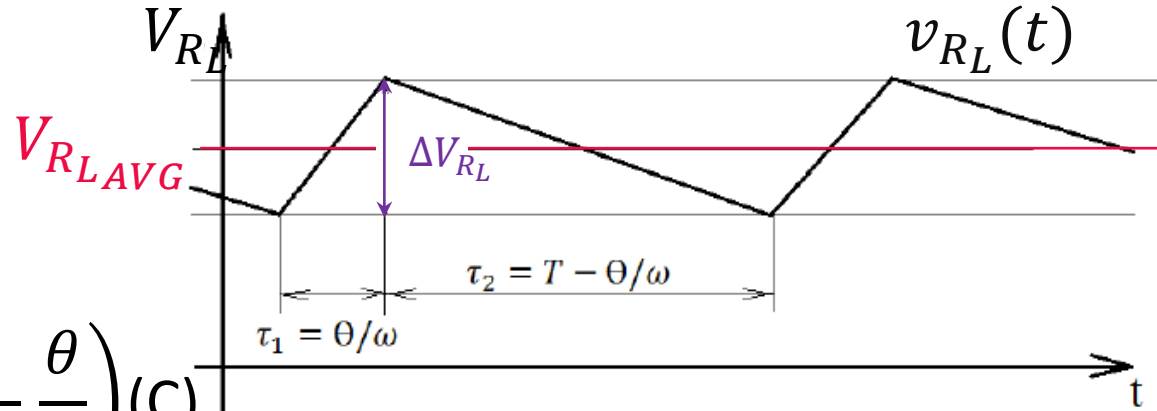
$$\tau_1 < t < \tau_2 = T - \frac{\theta}{\omega}$$








$$\Delta Q = C \cdot \Delta V_{RL} = I_C \left( T - \frac{\theta}{\omega} \right) (C)$$


capacitance value depending on the value of the permissible voltage ripple on the load

$$C = \frac{I_C}{2\pi f \cdot \Delta V_{RL}} (2\pi - \theta) = \frac{I_C}{\omega \cdot \Delta V_{RL}} (2\pi - \theta) \quad (F)$$


# Center-tapped Full Wave Rectifier

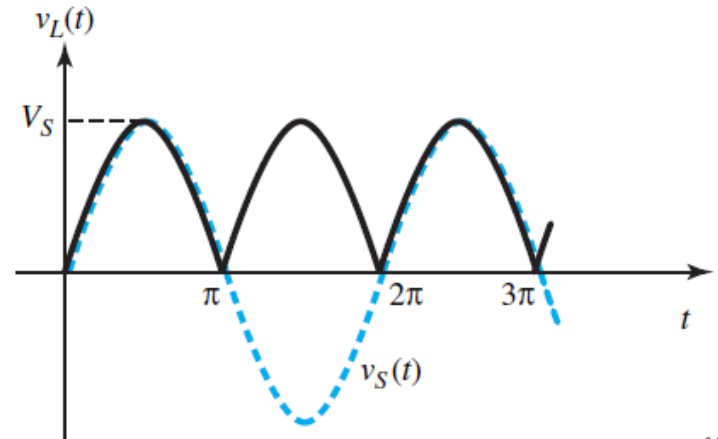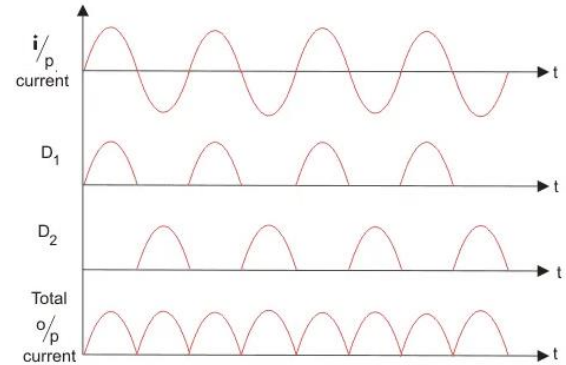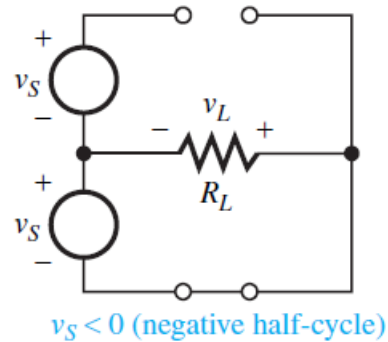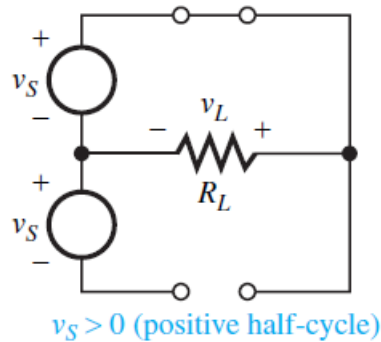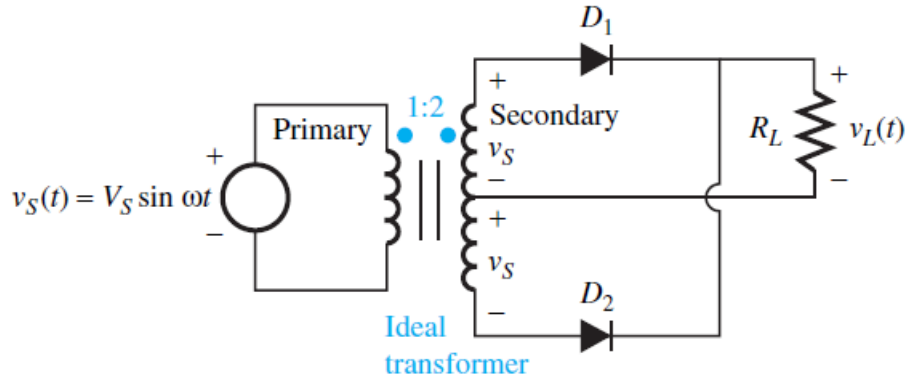


# Full Wave Bridge Rectifier

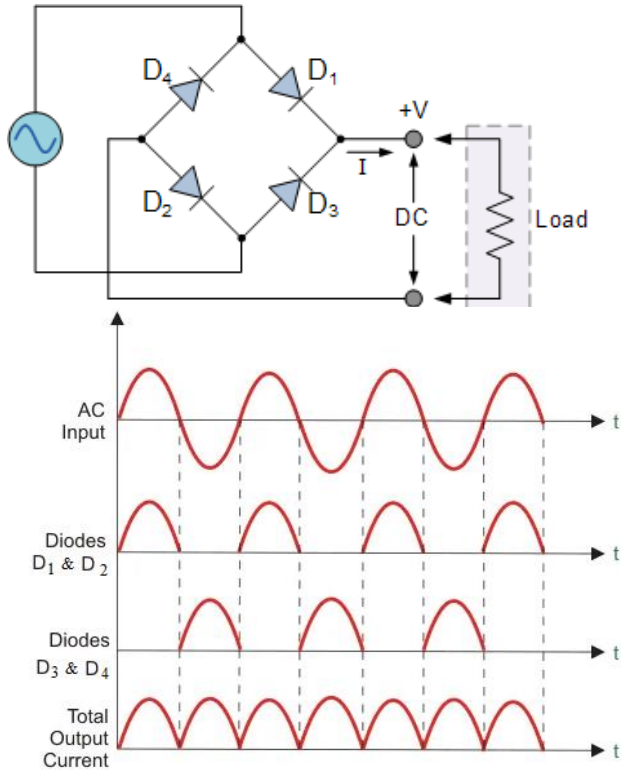

The Positive Half-cycle

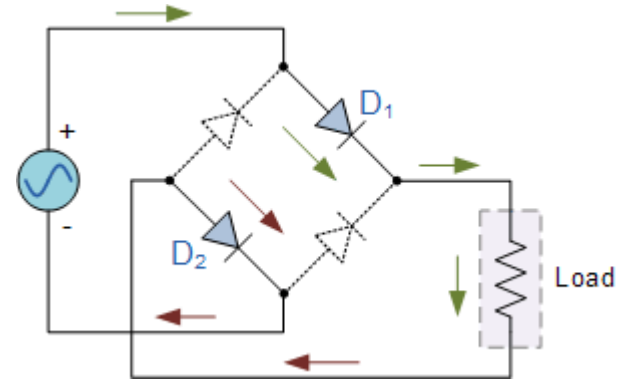

The Negative Half-cycle

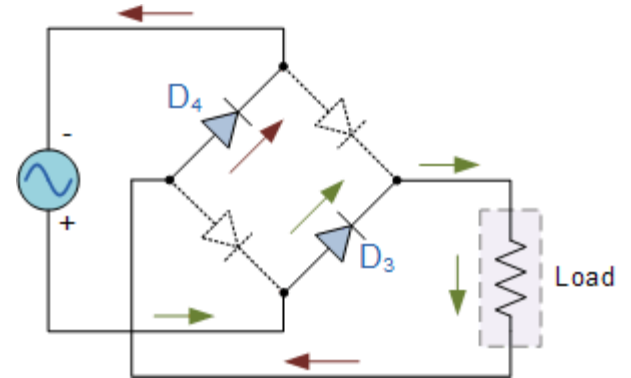

- **Average load voltage:** 
$$V_{RLAVG} = \begin{cases} \frac{V_S}{\pi}, & \text{for HWR schemes} \\ \frac{2 \cdot V_S}{\pi}, & \text{for FBR or CTR schemes} \end{cases} \quad (V)$$
- **RMS load voltage:** 
$$V_{RLRMS} = \begin{cases} \frac{V_S}{2}, & \text{for HWR schemes} \\ \frac{V_S}{\sqrt{2}}, & \text{for FBR or CTR schemes} \end{cases} \quad (V)$$
- **Max peak diode reverse voltage:** 
$$V_{VDmax} = V_{VDmax} = \begin{cases} 2V_S, & \text{for CTR schemes} \\ V_S, & \text{for HWR and FBR scheme} \end{cases} \quad (V)$$
- **Average load current:** 
$$I_{LAVG} = \frac{V_{RLAVG}}{R_L} = \begin{cases} \frac{V_S}{\pi R_L}, & \text{for HWR schemes} \\ \frac{2 \cdot V_S}{\pi R_L}, & \text{for FBR or CTR schemes} \end{cases} \quad (A)$$
- **RMS load current:** 
$$I_{LRMS} = \frac{V_{RLRMS}}{R_L} = \begin{cases} \frac{V_S}{2R_L}, & \text{for HWR schemes} \\ \frac{V_S}{\sqrt{2}R_L}, & \text{for FBR or CTR schemes} \end{cases} \quad (A)$$

- **Average diode rectified output current:**  $I_{VD} = \begin{cases} I_{L_{AVG}}, & \text{for HWR schemes} \\ \frac{I_{L_{AVG}}}{2}, & \text{for FBR or CTR schemes} \end{cases}$  (A)

- **Peak repetitive forward output current:**

- $I_{VD_{max}} = \begin{cases} \frac{V_S}{R_L}, & \text{for HWR schemes} \\ \frac{V_S}{2R_L}, & \text{for FBR or CTR schemes} \end{cases}$  (A)

- **Voltage ripple factor:**

$$K_p = \sqrt{\left(\frac{V_{R_{LRMS}}}{V_{R_{LAVG}}}\right)^2 - 1}$$

- **Voltage ripple evaluated for the rectifier scheme:**

$$\Delta V_{R_L} = 2 \cdot K_p \cdot V_{R_{LAVG}} \quad (V)$$

- **Source output resistance (overcurrent protection):**  $r_{on} = \frac{V_S}{I_{FSM}}$  ( $\Omega$ )
- **Input rectifier resistance:**  $r_{IN} = \begin{cases} r_{vd} + r_{V_S}, & \text{for HWR or CTR schemes} \\ 2 \cdot r_{vd} + r_{V_S}, & \text{for FBR schemes} \end{cases}$  ( $\Omega$ )
- **Diode opening state angle:**  $\theta = \begin{cases} 2 \cdot \sqrt[3]{3 \cdot \pi \cdot \frac{r_{IN}}{R_L}}, & \text{for HWR schemes} \\ 2 \cdot \sqrt[3]{\frac{3}{2} \cdot \pi \cdot \frac{r_{IN}}{R_L}}, & \text{for FBR or CTR schemes} \end{cases}$  (rad)
- **Average load voltage**  $V_{R_{L_{AVG}}} = V_S \cdot \cos\left(\frac{\theta}{2}\right)$  (V)
- **Average load current:**  $I_{L_{AVG}} = \begin{cases} \frac{1}{\pi \cdot r_{IN}} (V_S \cdot \sin\left(\frac{\theta}{2}\right) - V_{R_{L_{AVG}}} \cdot \frac{\theta}{2}), & \text{for HWR schemes} \\ \frac{2}{\pi \cdot r_{IN}} (V_S \cdot \sin\left(\frac{\theta}{2}\right) - V_{R_{L_{AVG}}} \cdot \frac{\theta}{2}), & \text{for FBR or CTR schemes} \end{cases}$  (A)
- **Average diode current:**  $I_{VD} = \begin{cases} \frac{V_S}{R_L} \cdot \cos\left(\frac{\theta}{2}\right), & \text{for HWR schemes} \\ \frac{V_S}{2 \cdot R_L} \cdot \cos\left(\frac{\theta}{2}\right), & \text{for FBR or CTR schemes} \end{cases}$  (A)

1. Maximum repetitive rectifier scheme diode current: 
$$I_{VDmax} = \frac{V_S - V_{RLAVG}}{r_{IN}} \quad (A)$$

2. Starting (Non-repetitive) maximum peak surge diode current in rectifier scheme: 
$$I_{VDON} = \frac{V_S}{r_{IN}} \quad (A)$$

3. Peak repetitive reverse voltage: 
$$V_{VDmax} = \begin{cases} V_S + V_{RLAVG}, & \text{for HWR or CTR schemes} \\ \frac{V_S + V_{RLAVG}}{2}, & \text{for FBR schemes} \end{cases} \quad (V)$$


4. Voltage ripple evaluated for the rectifier scheme with C-filter: 
$$\Delta V_{RL} = 2 \cdot K_p \cdot V_{RLAVG} \quad (V)$$

5. Capacitance evaluation: 
$$C = \begin{cases} \frac{I_{LAVG}}{2\pi f \cdot \Delta V_{RL}} (2\pi - \theta), & \text{for HWR schemes} \\ \frac{I_{LAVG}}{2\pi f \cdot \Delta V_{RL}} (\pi - \theta), & \text{for FBR or CTR schemes} \end{cases} \quad (F)$$

6. Voltage ripple: 
$$\Delta V_{RL} = \begin{cases} \frac{I_{LAVG}}{2\pi f \cdot C} (2\pi - \theta), & \text{for HWR schemes} \\ \frac{I_{LAVG}}{2\pi f \cdot C} (\pi - \theta), & \text{for FBR or CTR schemes} \end{cases} \quad (V)$$



	$I_{VD_{AVG}}$	$I_{VD_{max}}$	$V_{VD_{max}}$	$r_{IN}$
Half – wave rectifier	$= I_{L_{AVG}}$	$\approx 7I_{L_{AVG}}$	$=V_S \cdot 2 \approx 3V_{R_{L_{AVG}}}$	$= r_{vd} + r_{V_S}$
Central tap rectifier	$= \frac{I_{L_{AVG}}}{2}$	$\approx 3.5I_{L_{AVG}}$	$=V_S \cdot 2 \approx 3V_{R_{L_{AVG}}}$	$= r_{vd} + r_{V_S}$
Full bridge (Graetz) rectifier	$= \frac{I_{L_{AVG}}}{2}$	$\approx 3.5I_{L_{AVG}}$	$=V_S \approx 1.5V_{R_{L_{AVG}}}$	$=2r_{vd} + r_{V_S}$

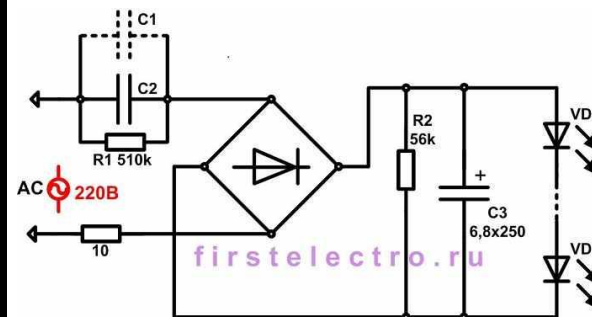

# LED -lamp parameters




$$K_p = \sqrt{\left(\frac{V_{RLRMS}}{V_{RLAVG}}\right)^2 - 1}$$

$$K_p \cong \frac{V_{RLmax} - V_{RLmin}}{V_{RLmax} + V_{RLmin}} = \frac{V_{RLmax} - V_{RLmin}}{2V_{RLAVG}}$$

	бренд	модель	описание	цена	Вт	Лм	эфф	экв	К	CRI	угол	пул	ВН	итог	гар	акт
📷	Smartbuy	<a href="#">SBL-P45-05-30K-E14</a>	G45 350Lm 5W 3000K M E14		4.8	471	98.1	50	3054	73.5	126	1		3.5		+
📷	Smartbuy	<a href="#">SBL-P45-07-30K-E14</a>	G45 530Lm 7W 3000K M E14		5.8	451	77.8	50	2798	72.6	176	1	-	3.1	24	+
📷	Smartbuy	<a href="#">SBL-P45-07-30K-E14.2</a>	G45 530Lm 7W 3000K M E14		5.7	480	84.2	55	2786	73.7	132	2	-	3.2	24	+
📷 🛒	Smartbuy	<a href="#">SBL-P45DF-5-40K-E14</a>	G45 370Lm 5W 4000K F E14	221	3.6	267	75.2	30	3755	85.5	294	100	+	0.2	24	+

# Rectifier example



<https://www.tinkercad.com>

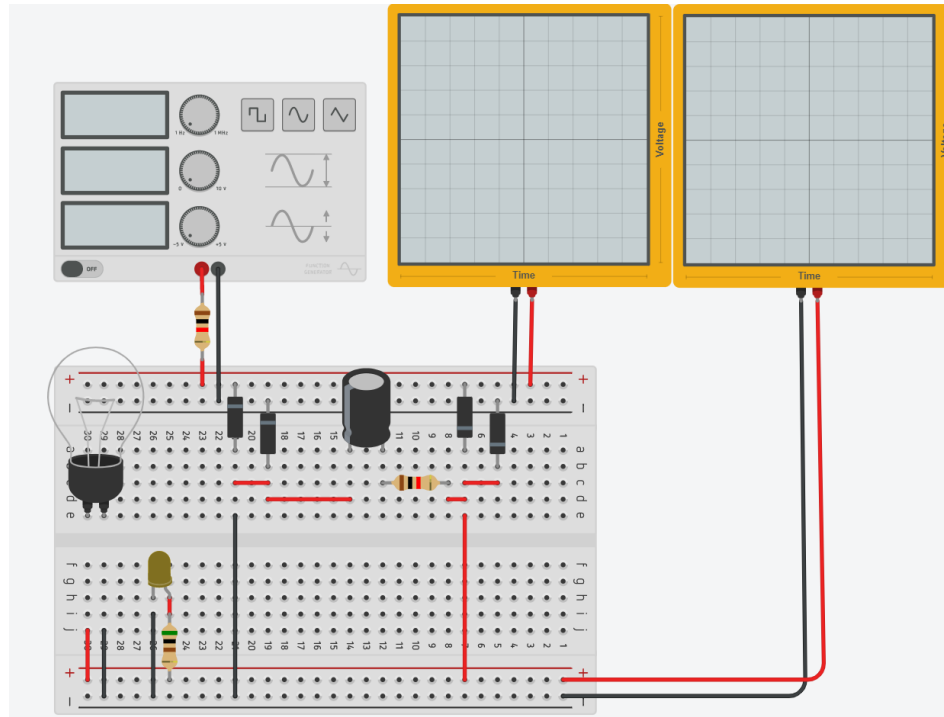



# Voltage doubler (Greinacher multiplier)



Heinrich Greinacher, 1914

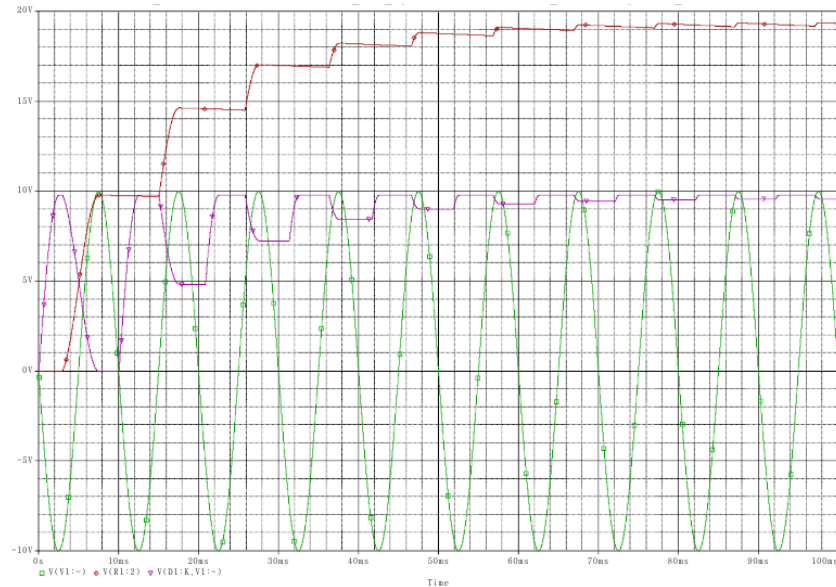
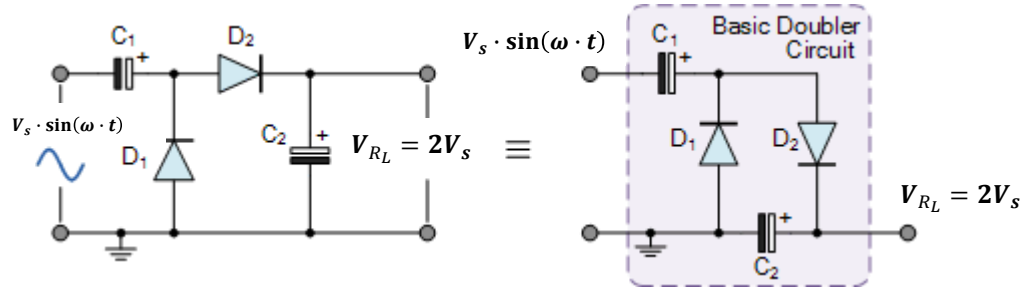


# Full-wave voltage doubler

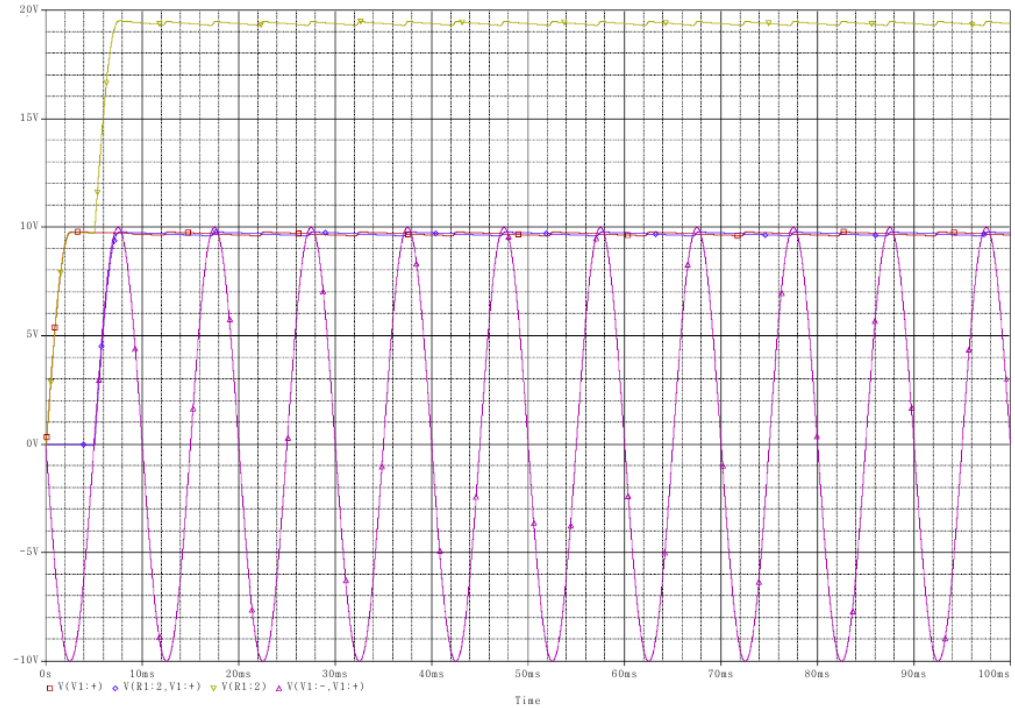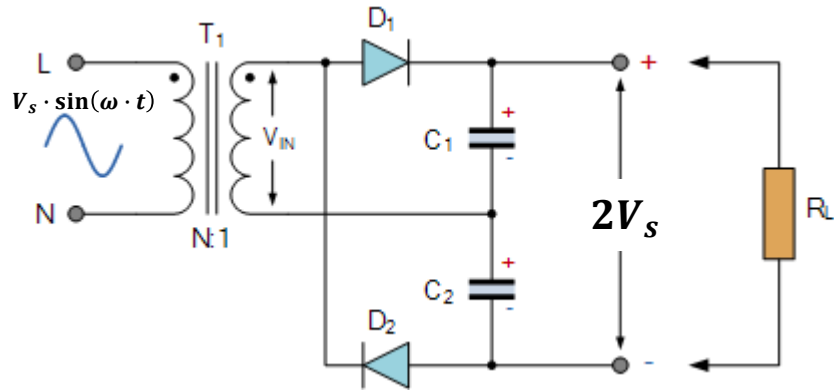



# Voltage multiplier

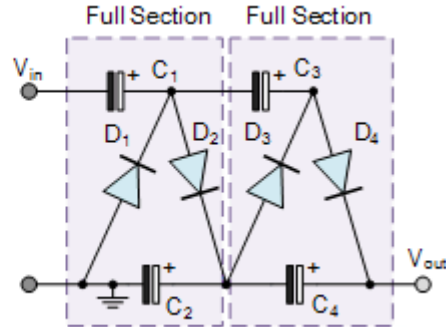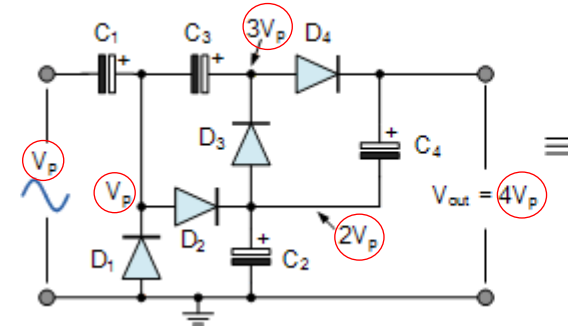

$$C = \frac{N^2 + N}{2} \frac{I_L}{f \Delta U_L}$$

$$U_L = NU_{IN_{MAX}} - \frac{I_L(N^3 + \frac{9}{4}N^2 + \frac{1}{2}N)}{12fC}$$



This Cockcroft–Walton particle accelerator was used during the development of the [atomic bomb](#). Built in 1937 by [Philips of Eindhoven](#) it is now in the [National Science Museum](#) in London, England.



750 kV Cockcroft-Walton accelerator used as the initial particle injector of the Japanese [KEK](#) accelerator, Tsukuba, Japan. The CW generator is on the right, the particle source is on the left.

Ernest Walton	Sir John Cockcroft
<b>Born</b> 6 October 1903 Abbeyside, Dungarvan, Co. Waterford, Ireland	<b>Born</b> 27 May 1897 Todmorden, West Riding of Yorkshire, England
<b>Died</b> 25 June 1995 (aged 91) Belfast, Northern Ireland	<b>Died</b> 18 September 1967 (aged 70) Cambridge, Cambridgeshire, England
<b>Nationality</b> Irish	<b>Nationality</b> British
<b>Alma mater</b> Trinity College Dublin Trinity College, Cambridge	<b>Alma mater</b> Victoria University of Manchester Manchester Municipal College of Technology St. John's College, Cambridge
<b>Known for</b> The first disintegration of an atomic nucleus by artificially accelerated protons ("splitting the atom")	<b>Known for</b> Splitting the atom
<b>Awards</b> Hughes Medal (1938) Nobel Prize in Physics (1951)	<b>Awards</b> Hughes Medal (1938) Commander of the Order of the British Empire (1944) Knight Bachelor (1948) Nobel Prize in Physics (1951) Royal Medal (1954) Faraday Medal (1955) Order of Merit (1957) Atoms for Peace Award (1961) Wilhelm Exner Medal (1961) Knight Commander of the Order of the Bath (1963) Medal of Freedom with golden palms (United States, 1947) Chevalier de la Legion d'Honneur (France, 1950) Knight Commander of the Military Order of Christ (Portugal, 1955) Grand Cross of the Order of Alfonso X (Spain, 1958)
<b>Fields</b> Physics	<b>Fields</b> Physics
<b>Institutions</b> Trinity College Dublin University of Cambridge Methodist College Belfast Dublin Institute for Advanced Studies	<b>Institutions</b> Atomic Energy Research Establishment
<b>Doctoral advisor</b> Ernest Rutherford	<b>Thesis</b> On phenomena occurring in the condensation of molecular streams on surfaces (1928)
	<b>Academic advisors</b> Ernest Rutherford
	<b>1st Master of Churchill College, Cambridge</b> In office 1959–1967
	<b>Succeeded by</b> Sir William Hawthorne

The background features a dark gray grid pattern. In the top right and bottom left corners, there are decorative wavy lines in a bright purple color, creating a modern, tech-oriented aesthetic.

**iTMO**

**Thank you for your attention!**