



iTMO

Operational amplifiers circuits design basics

Nikolay Nikolaev

(nanikolaev@itmo.ru)

Nikolai Poliakov

(polyakov_n_a@itmo.ru)




iTMO



OPERATIONAL AMPLIFIERS (OP-AMP)


Nikolay Nikolaev
Nikolai Poliakov

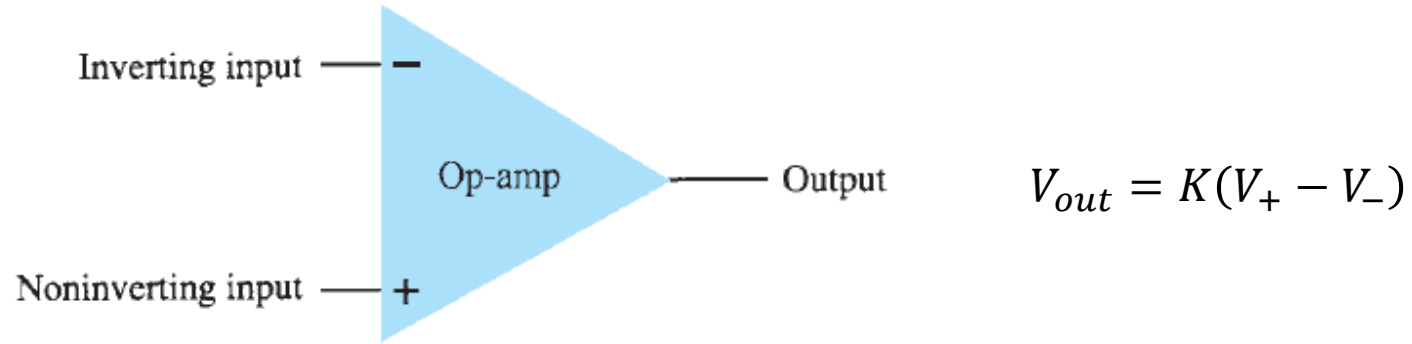(nanikolaev@itmo.ru)
(polyakov_n_a@itmo.ru)




AC equivalent of op-amp circuit

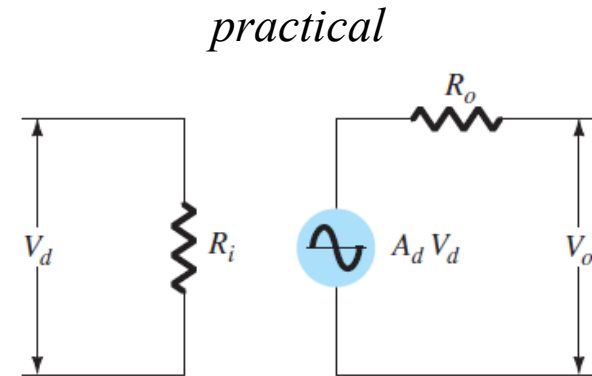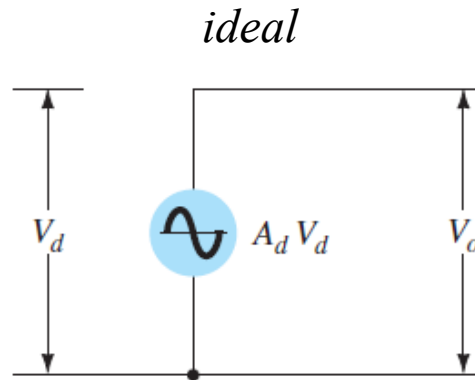

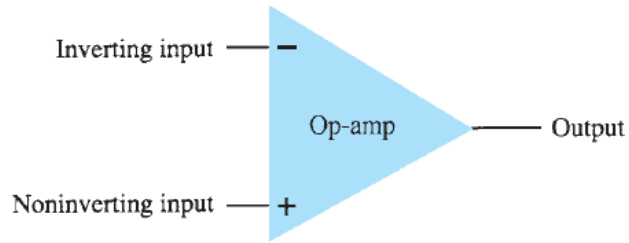

ideal

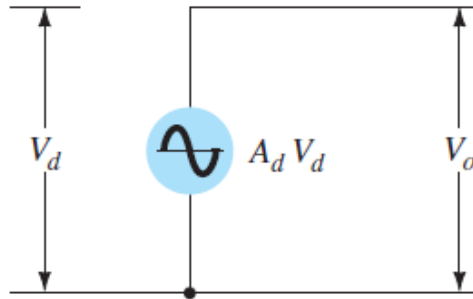

IDEAL OP AMP ATTRIBUTES


- ✓ Infinite Differential Gain
- ✓ Zero Common Mode Gain
- ✓ Zero Offset Voltage
- ✓ Zero Bias Current
- ✓ Infinite Bandwidth


OP AMP INPUT ATTRIBUTES

- ✓ Infinite Impedance
- ✓ Zero Bias Current
- ✓ Respond to Differential Voltages
- ✓ Do Not Respond to Common Mode Voltages

OP AMP OUTPUT ATTRIBUTES


- ✓ Zero Impedance

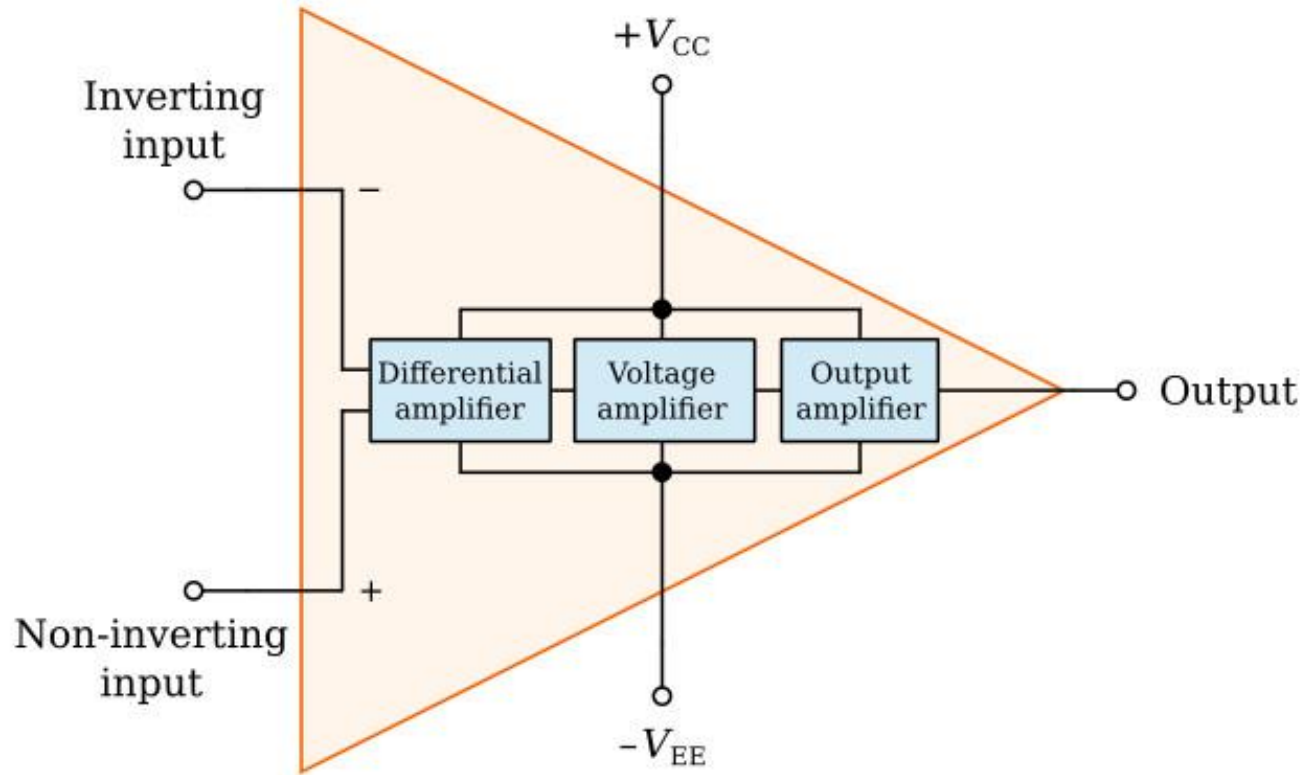

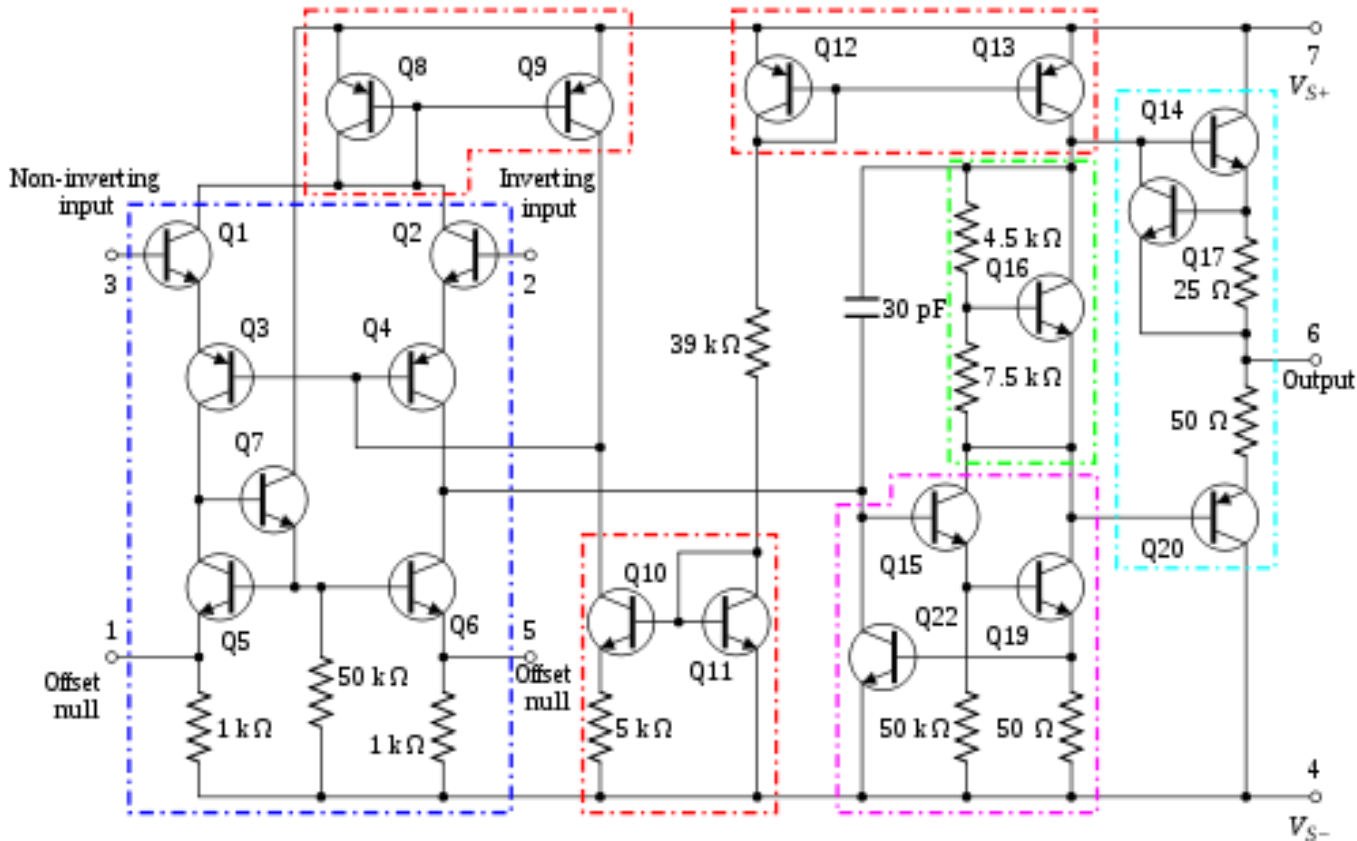

A component-level diagram of the common 741 op amp.

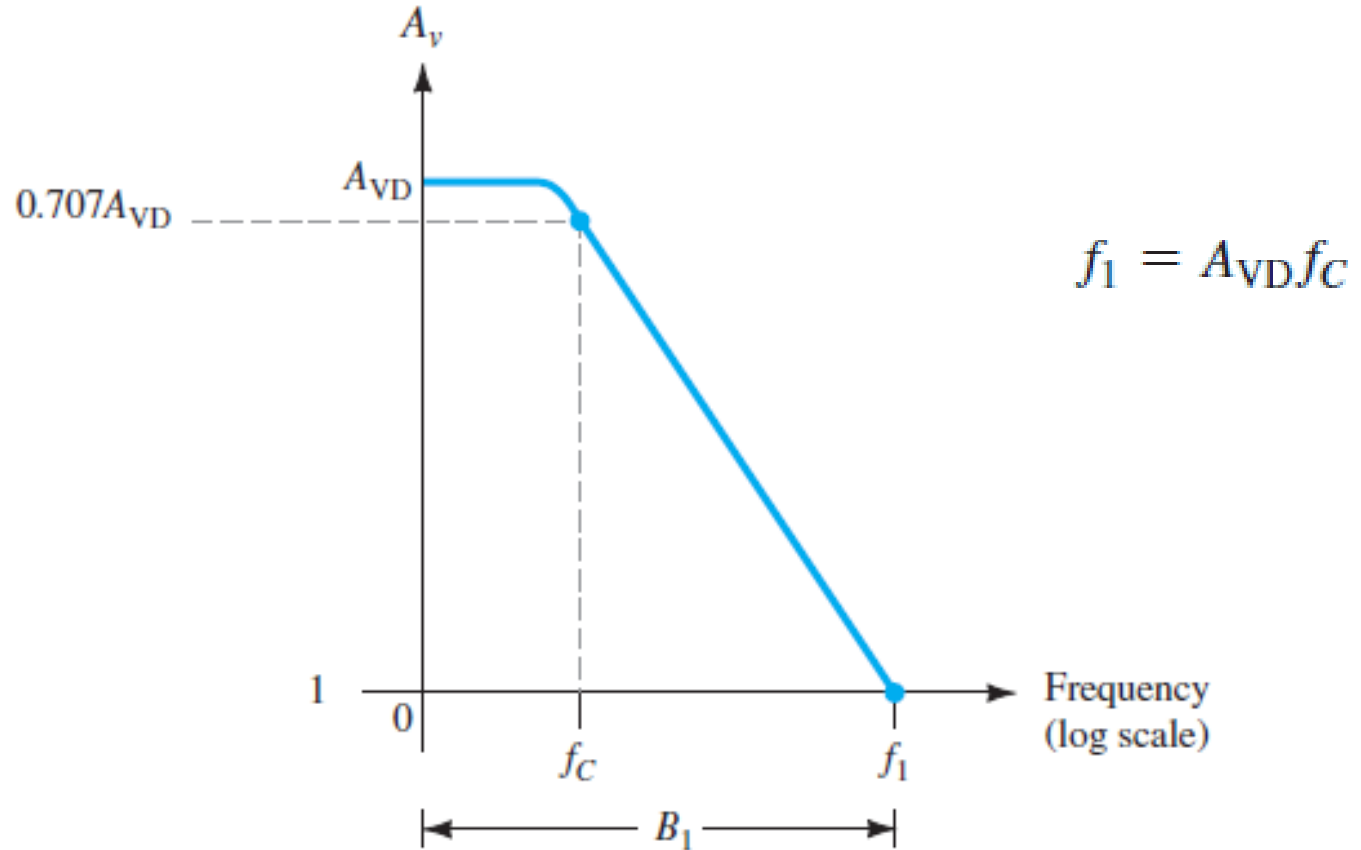Dotted lines outline:
 current mirrors;
 differential amplifier;
 class A gain stage;
 voltage level shifter;
 output stage.



Slew rate = maximum rate at which amplifier output can change in volts per microsecond ($V/\mu s$)

Slew rate calculation & formula


$$SR = \frac{\Delta V_o}{\Delta t} \text{ V}/\mu s \quad \text{or} \quad SR = 2\pi fV$$

Where

Slew Rate (SR) is measured in volts / second, although actual measurements are often given in $v/\mu s$

f – the highest signal frequency, Hz

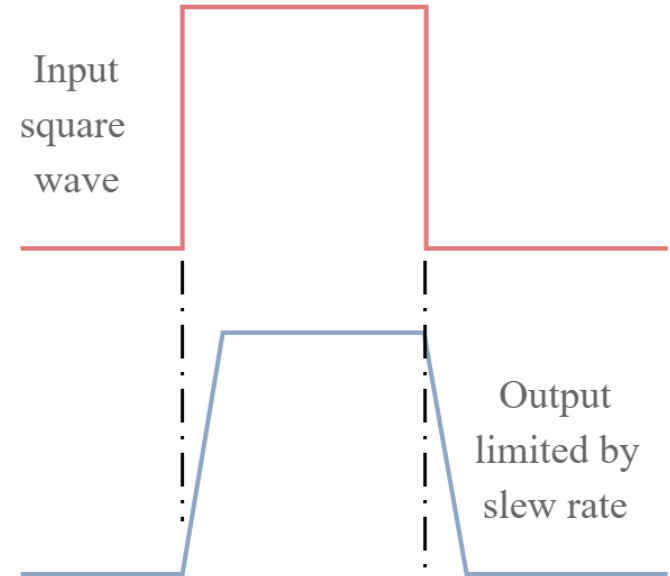V – the maximum peak voltage of the signal.



Maximum Signal Frequency

The maximum frequency at which an op-amp may operate depends on both the bandwidth (BW) and slew rate (SR) parameters of the op-amp. For a sinusoidal signal of general form

$$v_o = K \sin(2\pi ft)$$

the maximum voltage rate of change can be shown to be

$$\text{signal maximum rate of change} = 2\pi fK \text{ V/s}$$



To prevent distortion at the output, the rate of change must also be less than the slew rate, that is,

$$2\pi fK \leq \text{SR}$$

$$\omega K \leq \text{SR}$$

$$f \leq \frac{\text{SR}}{2\pi K} \quad \text{Hz}$$
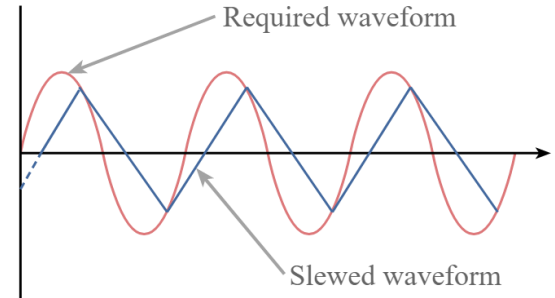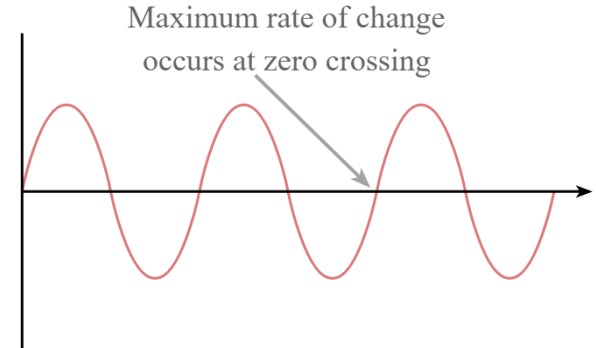
$$\omega \leq \frac{\text{SR}}{K} \quad \text{rad/s}$$



Differential Inputs $V_d = V_{i_1} - V_{i_2}$


Common Inputs $V_c = \frac{1}{2}(V_{i_1} + V_{i_2})$

Output Voltage $V_o = A_d V_d + A_c V_c$


Common-Mode Rejection Ratio $\text{CMRR} = \frac{A_d}{A_c}$

- ✓ Single-Ended Input
- ✓ Double-Ended (Differential) Input
- ✓ Double-Ended Output
- ✓ Common-Mode Operation




Double-ended input, Single-Ended output

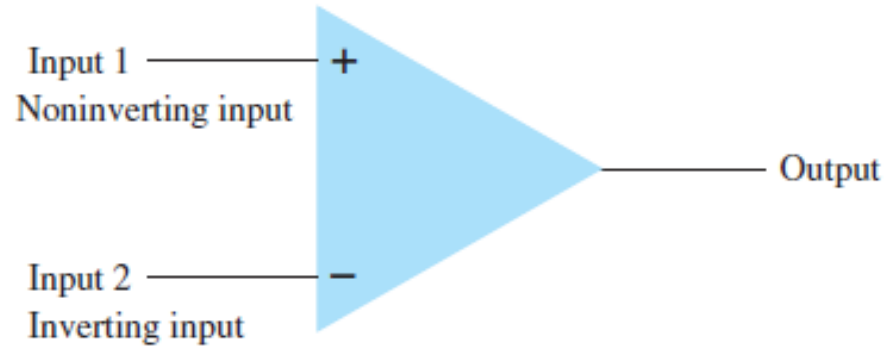



Double-ended input, double-ended output

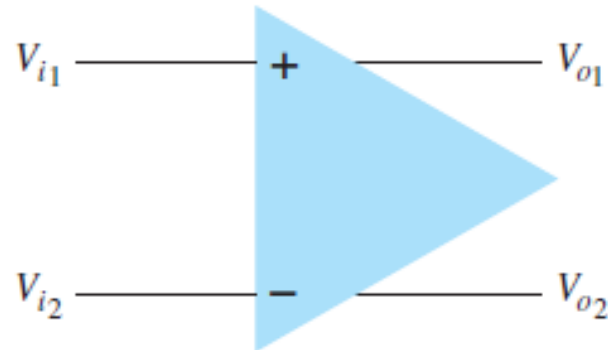


Single-Ended Input

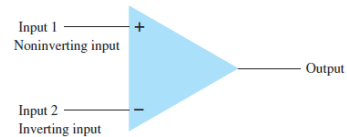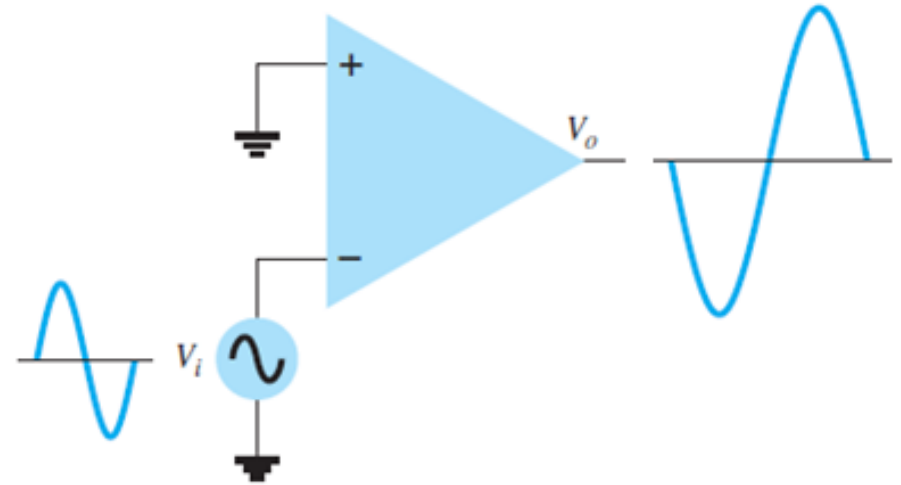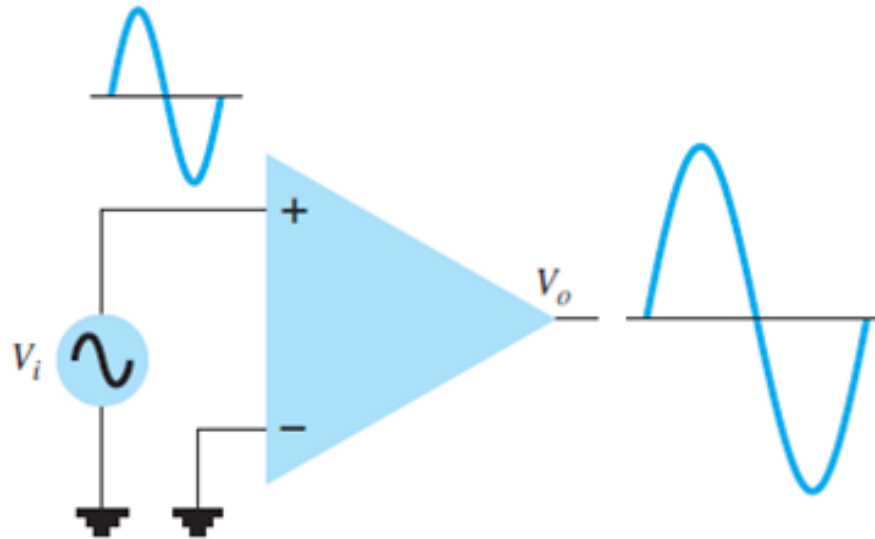


Double-Ended (Differential) Input

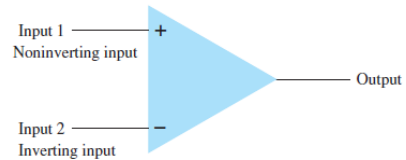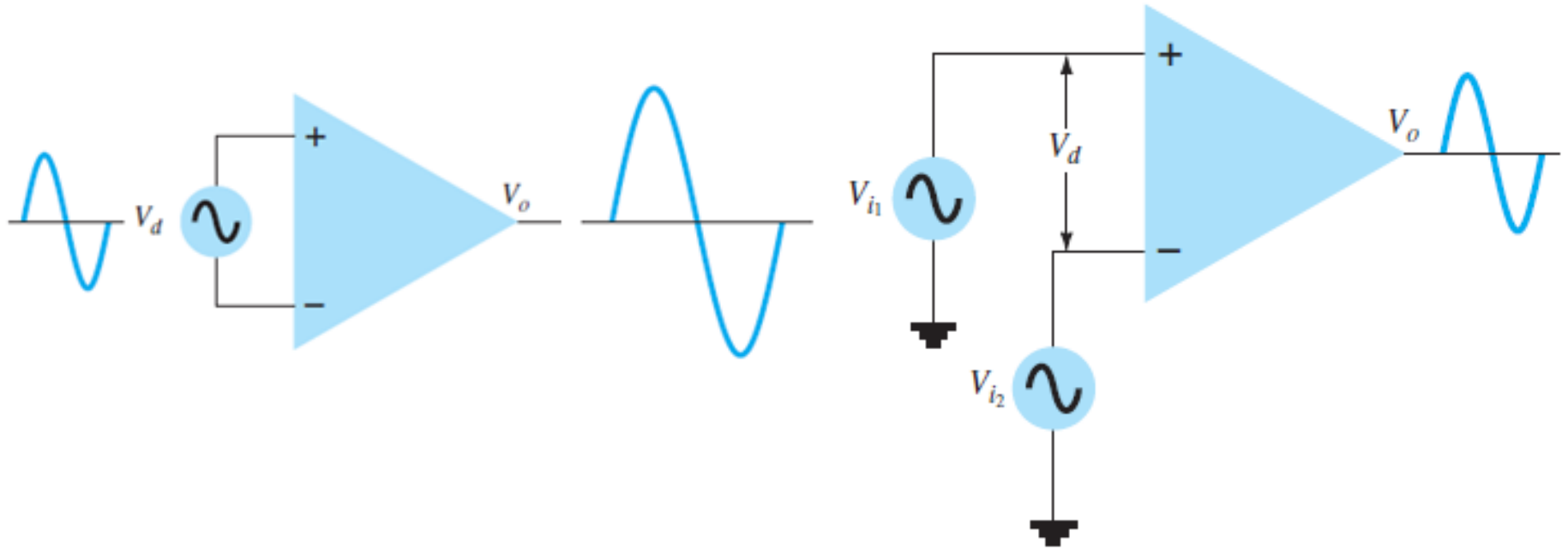

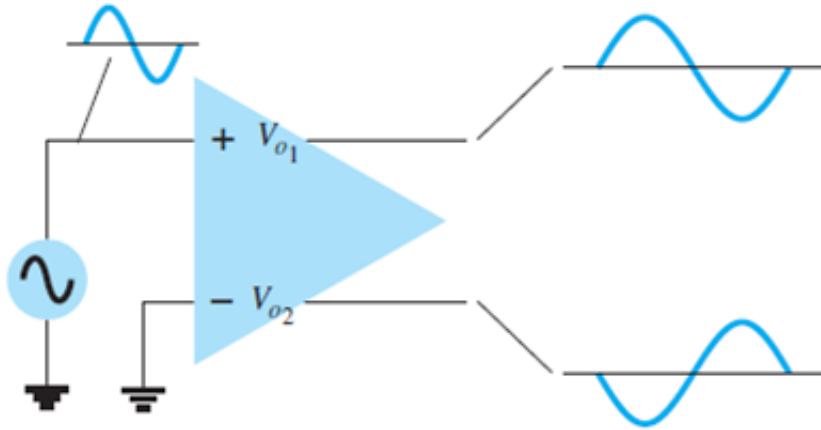
Single-ended input with double-ended output




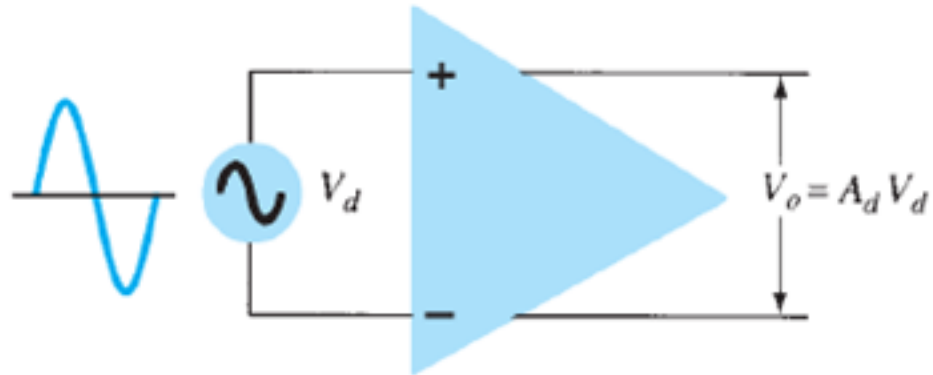Differential-input, differential-output operation



$$V_o = A_d V_d = V_{o1} - V_{o2}$$

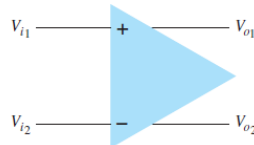


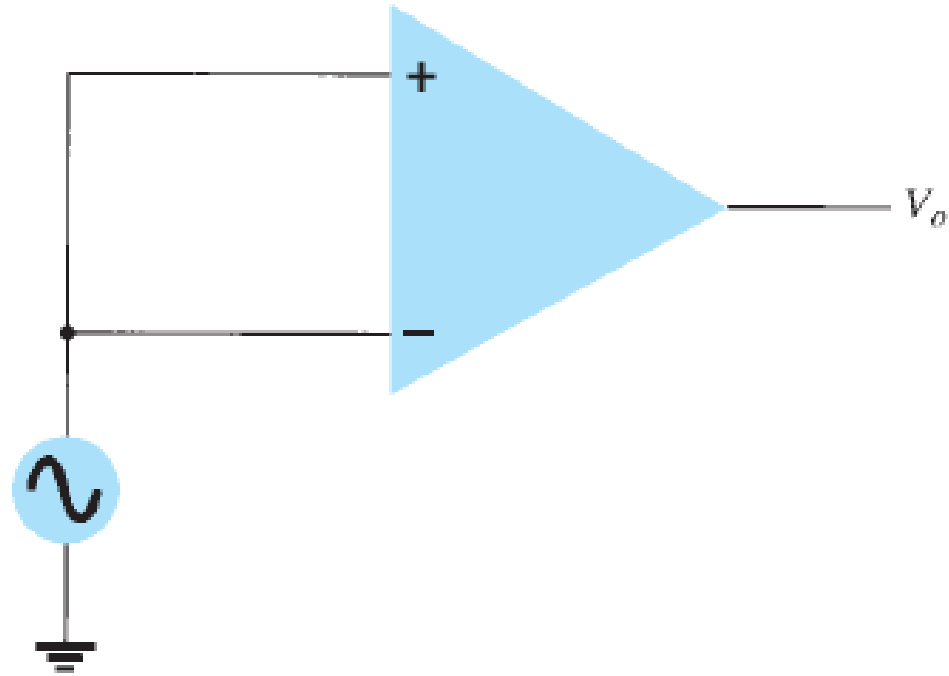


The background features a dark gray grid pattern. In the top right and bottom left corners, there are decorative wavy lines in a bright purple color, creating a modern, abstract aesthetic.

iTMO


Single stage amplifier

Inverting Amplifier

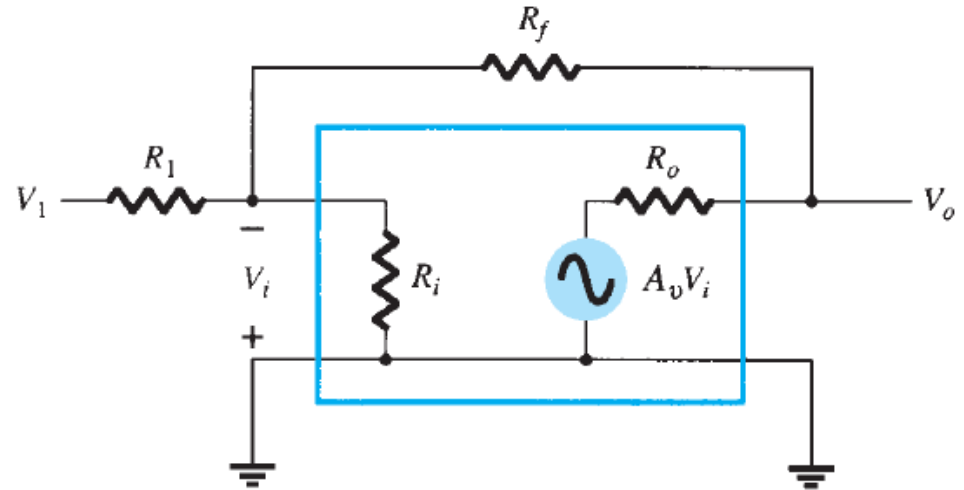
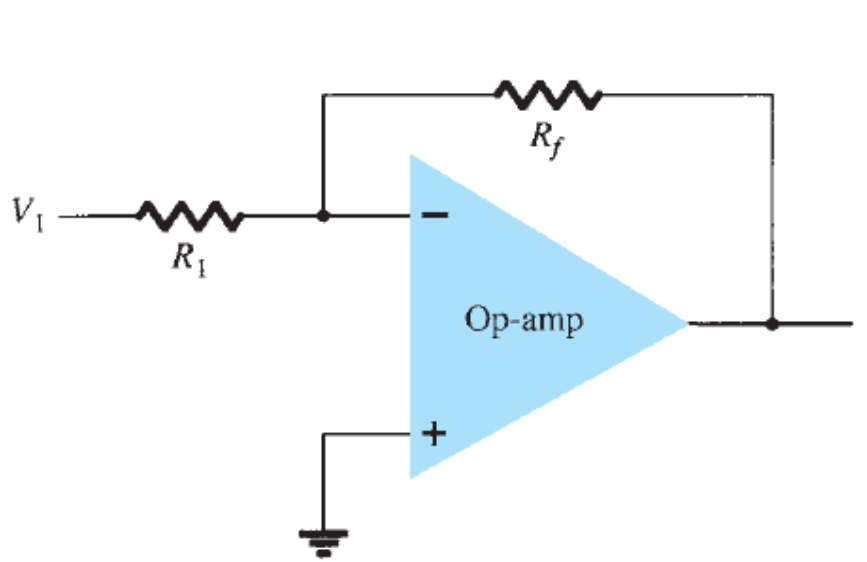


$$I_{R_1} = I_{R_f} \Rightarrow V_o = -\frac{R_f}{R_1} V_i \Rightarrow$$
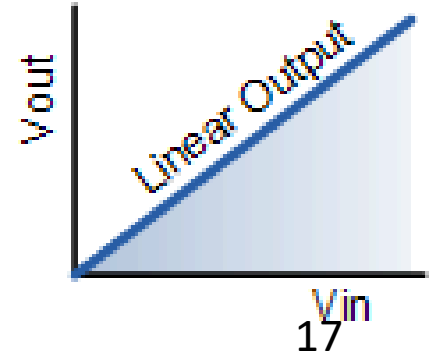
$$A_d = \frac{V_o}{V_i} = -\frac{R_f}{R_1}$$




Noninverting Amplifier

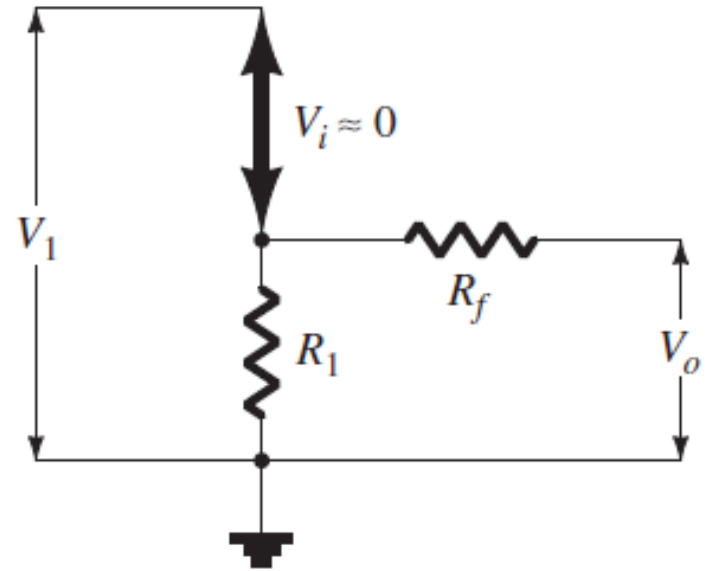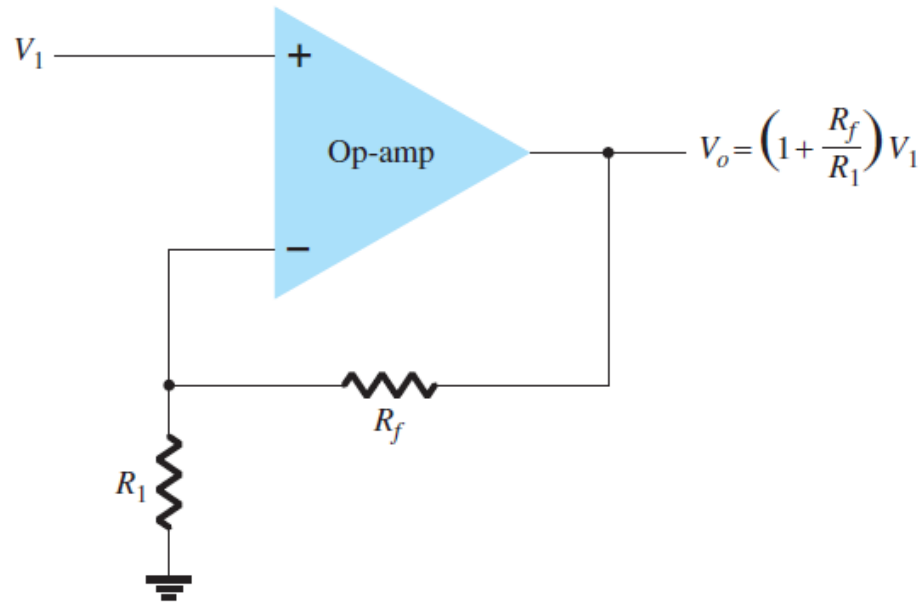

$$\frac{V_o}{V_1} = \frac{R_1 + R_f}{R_1} = 1 + \frac{R_f}{R_1}$$

Inverting Amplifier	Non-inverting Amplifier
The feedback used in amplifier is voltage shunt or negative feedback	The type of feedback used in amplifier is voltage series or negative feedback
The output of this amplifier is inverted	The output of is in phase by the input signal
the reference voltage can be given to the inverting terminal	In this amplifier, the reference voltage can be given to the non-inverting terminal
The gain is $A_d = -\frac{R_f}{R_1}$	The gain is $A_d = 1 + \frac{R_f}{R_1}$
The voltage gain is $A_d \leq \geq 1$ (less than, greater than or equal)	The voltage gain is $A_d \geq 1$
The input impedance is R_1	The input impedance is very large

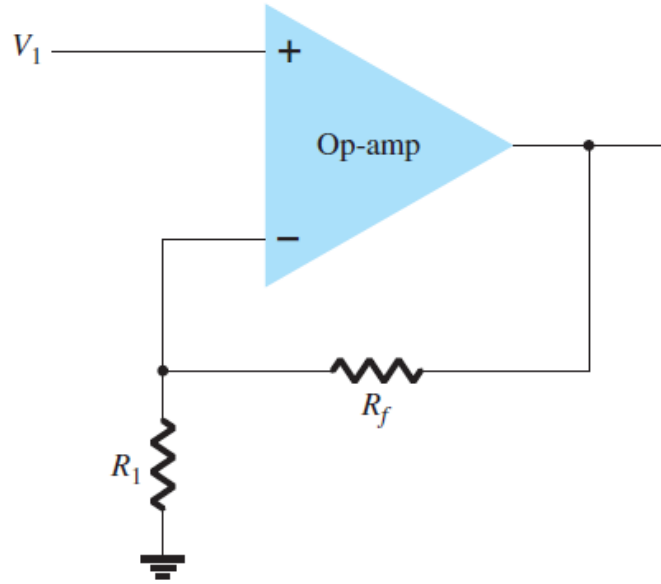


$$V_o = \left(1 + \frac{R_f}{R_1}\right) V_1$$





$$\begin{aligned} R_f &\rightarrow 0 \\ R_1 &\rightarrow \infty \end{aligned}$$





$$V_o = V_1$$

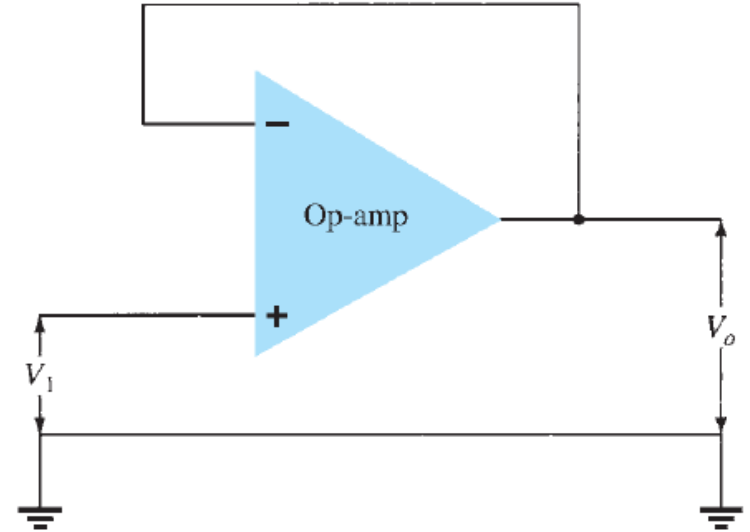


Summing Amplifier

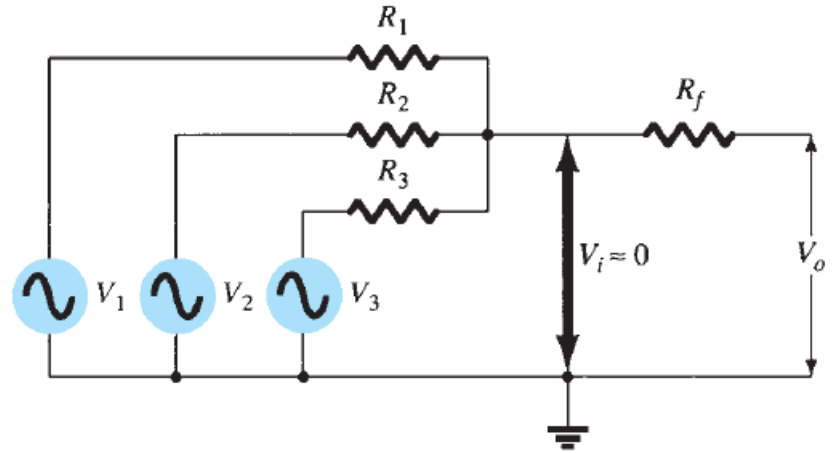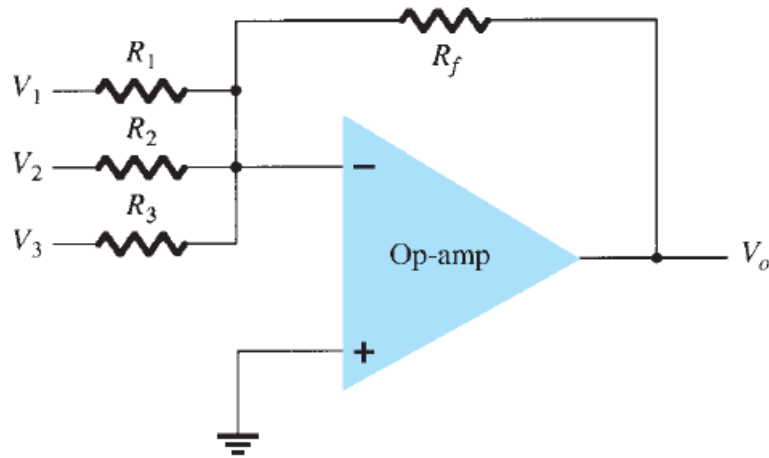
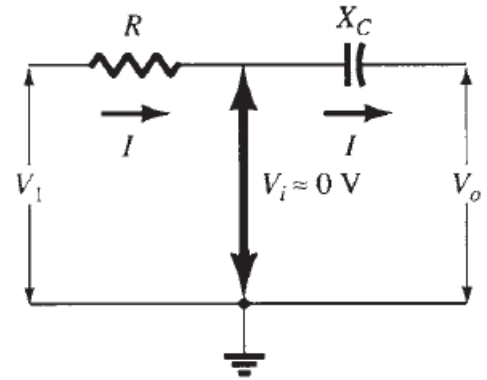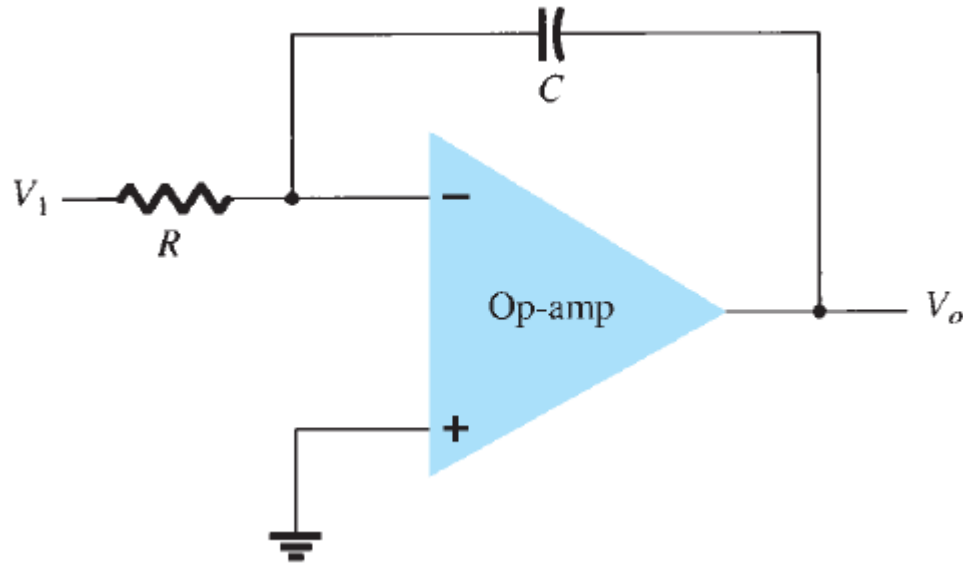
$$V_o = -\left(\frac{R_f}{R_1}V_1 + \frac{R_f}{R_2}V_2 + \frac{R_f}{R_3}V_3\right)$$



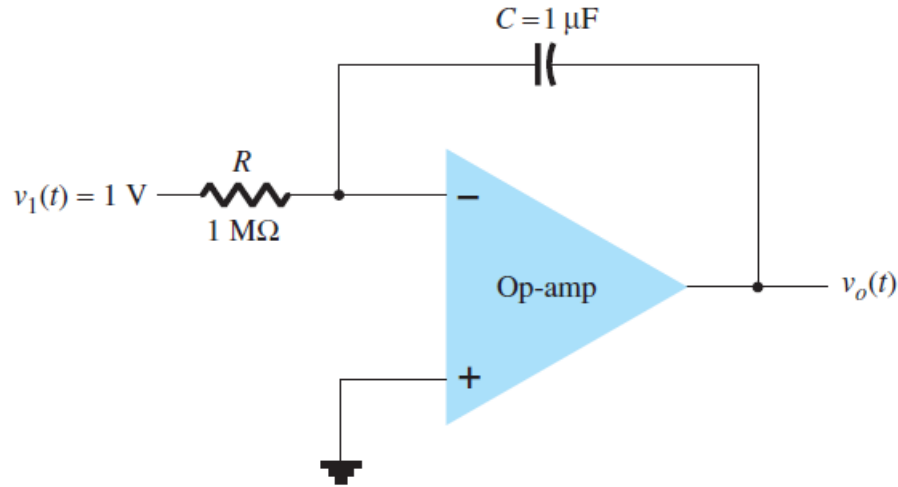
$$v_o(t) = -\frac{1}{RC} \int v_1(t) dt$$




scale factor

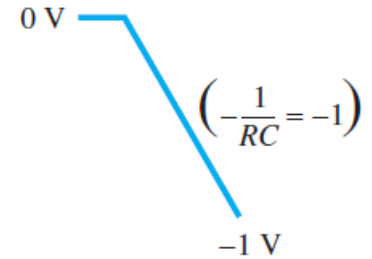
$$-\frac{1}{RC} = \frac{1}{(1 \text{ M}\Omega)(1 \mu\text{F})} = -1$$




$$v_o(t) = -\frac{1}{RC} \int v_1(t) dt$$
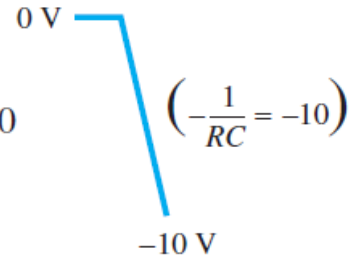
$$-\frac{1}{RC} = \frac{1}{(100 \text{ k}\Omega)(1 \mu\text{F})} = -10$$




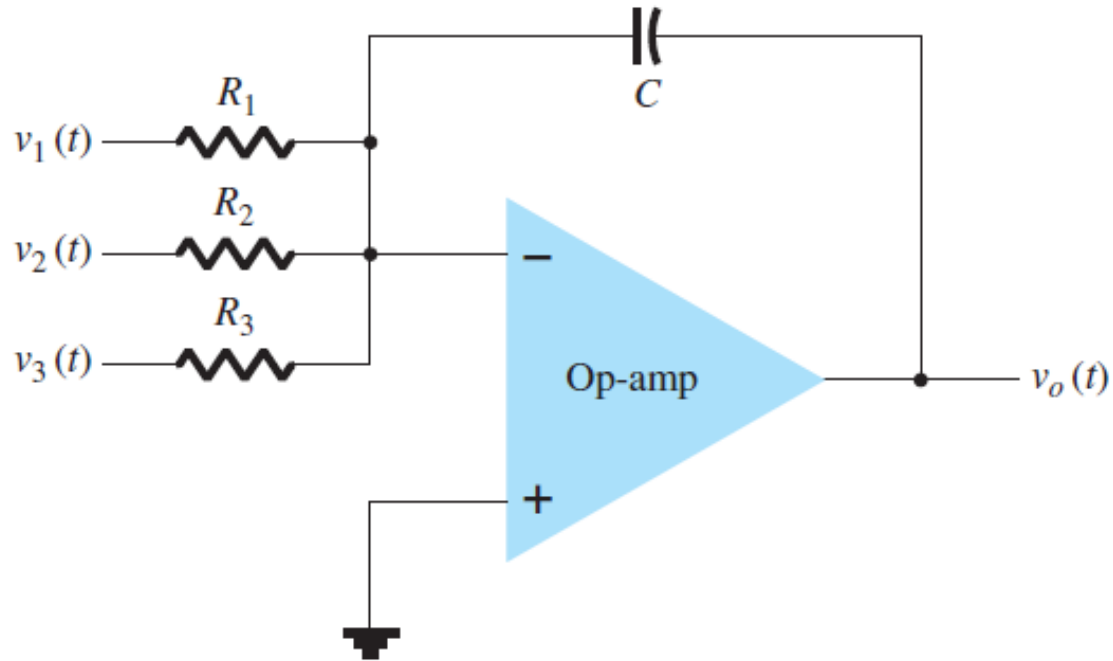


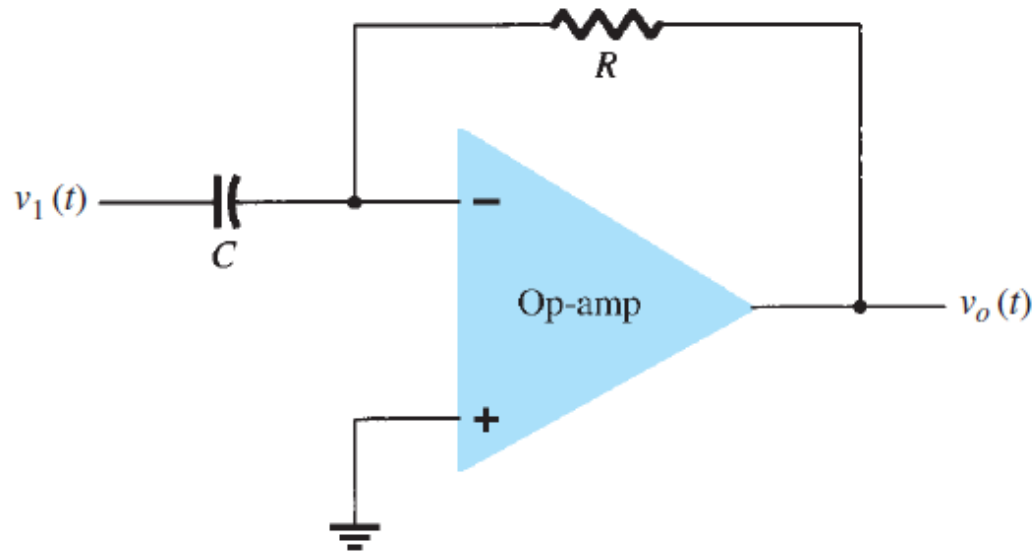
$$v_o(t) = - \left[\frac{1}{R_1 C} \int v_1(t) dt + \frac{1}{R_2 C} \int v_2(t) dt + \frac{1}{R_3 C} \int v_3(t) dt \right]$$



$$v_o(t) = -RC \frac{dv_1(t)}{dt}$$

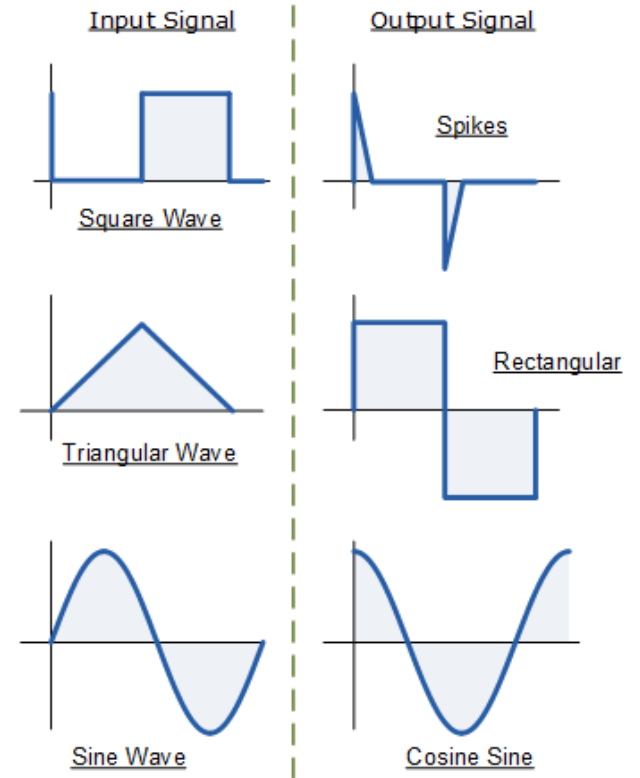


Integrator

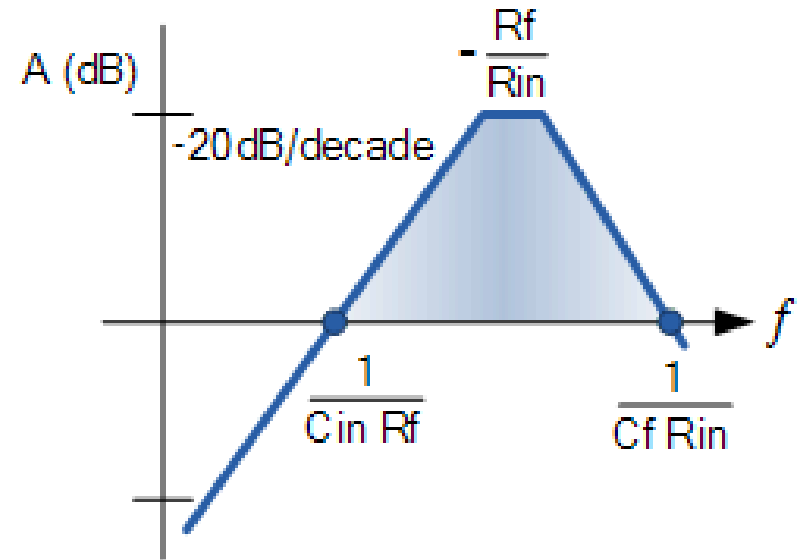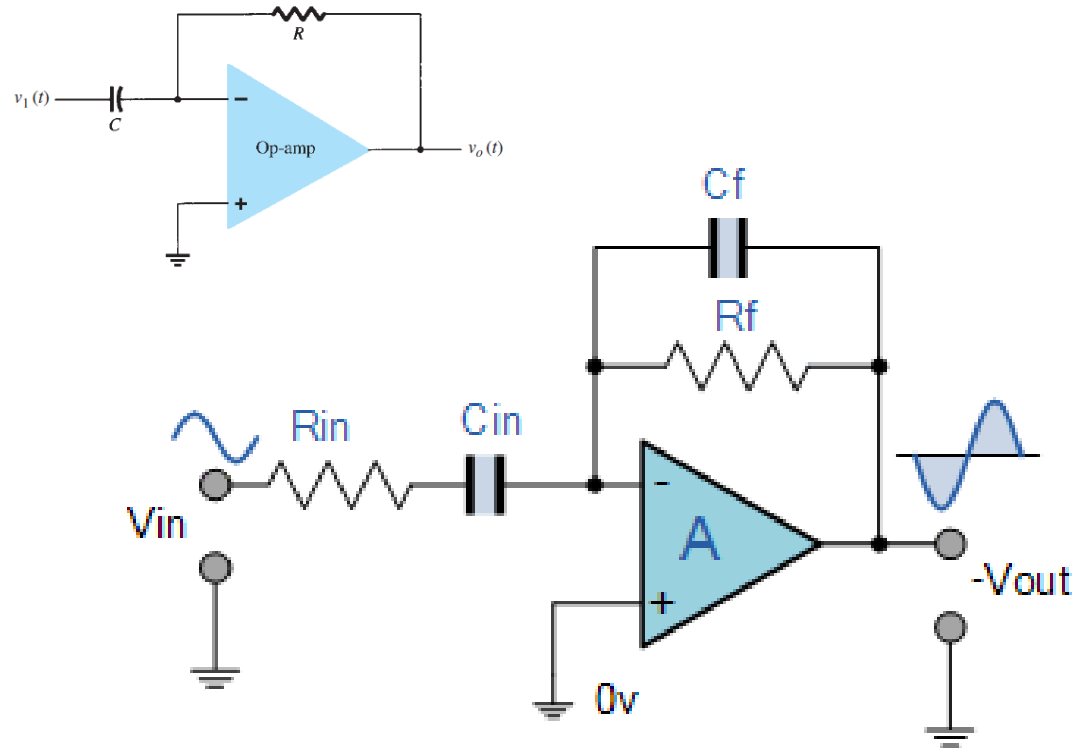



iTMO

Offset Currents and Voltages in OP Amp

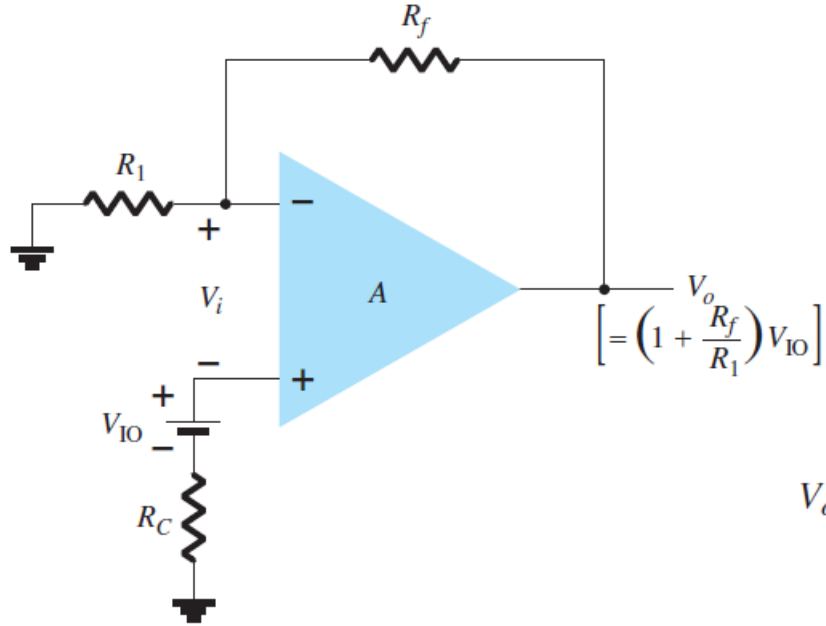

$$V_o = A * V_i$$


$$V_o = AV_i = A \left(V_{IO} - V_o \frac{R_1}{R_1 + R_f} \right)$$

Solving for V_o


$$V_o = V_{IO} \frac{A}{1 + A \left[R_1 / (R_1 + R_f) \right]} \approx V_{IO} \frac{A}{A \left[R_1 / (R_1 + R_f) \right]}$$

$$V_{o(\text{offset})} = V_{IO} \frac{R_1 + R_f}{R_1}$$

Input Offset Current

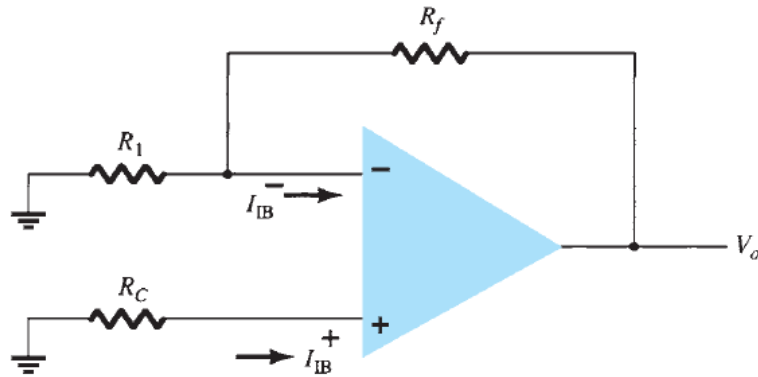

$$I_{IO} = I_{IB}^+ - I_{IB}^-$$

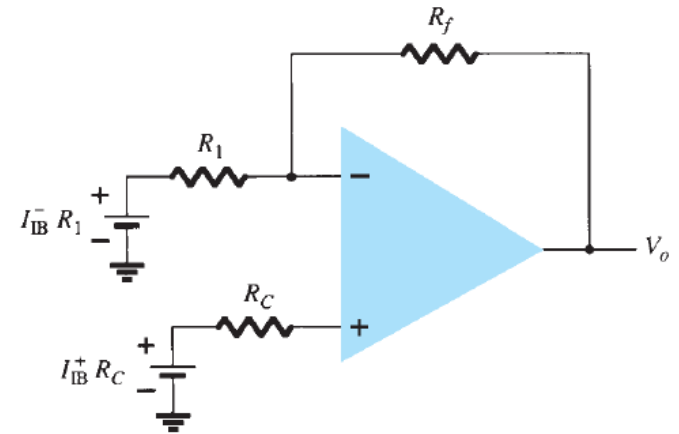





$$V_o^+ = I_{IB}^+ R_C \left(1 + \frac{R_f}{R_1} \right)$$

$$V_o(\text{offset due to } I_{IB}^+ \text{ and } I_{IB}^-) = I_{IB}^+ R_C \left(1 + \frac{R_f}{R_1} \right) - I_{IB}^- R_1 \frac{R_f}{R_1}$$

$$V_o^- = I_{IB}^- R_1 \left(-\frac{R_f}{R_1} \right)$$

$$V_o(\text{offset due to } I_{IO}) = I_{IO} R_f$$

$$|V_o(\text{offset})| = |V_o(\text{offset due to } V_{IO})| + |V_o(\text{offset due to } I_{IO})|$$

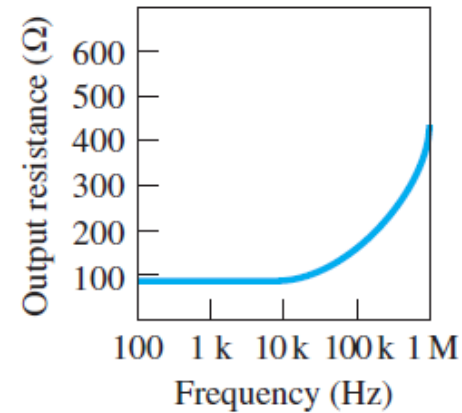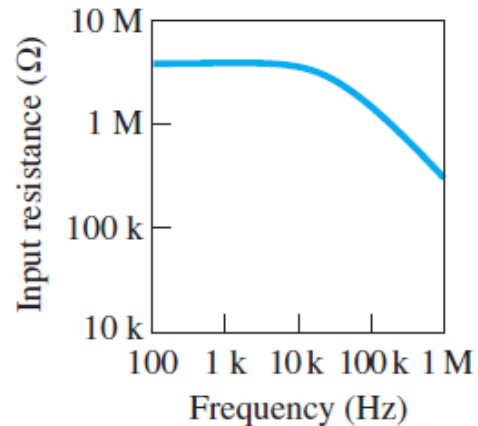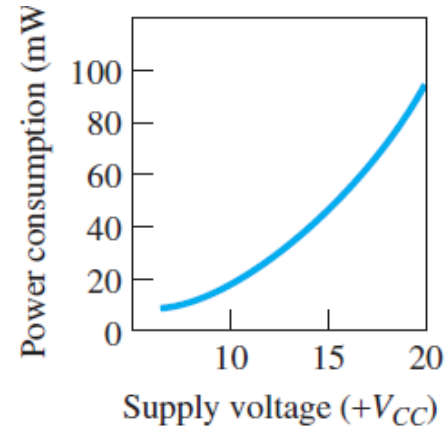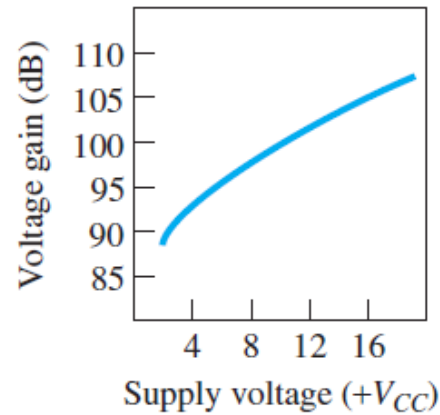


The background features a dark gray grid pattern. In the top right and bottom left corners, there are decorative wavy lines in a bright purple color, creating a modern, tech-oriented aesthetic.

iTMO

Multiple-Stage amplifier

Multiple-Stage Gains

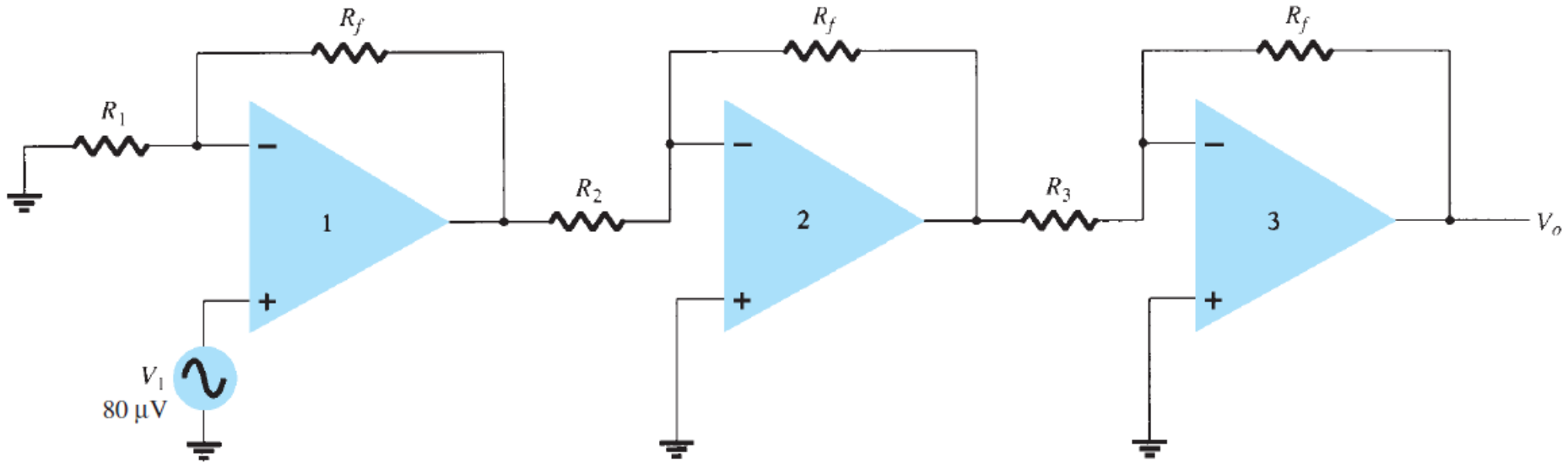



$$A_1 = 1 + \frac{R_f}{R_1}$$


$$A_2 = -\frac{R_f}{R_2}$$

$$A_3 = -\frac{R_f}{R_3}$$

$$A = A_1 A_2 A_3$$

Voltage Subtraction

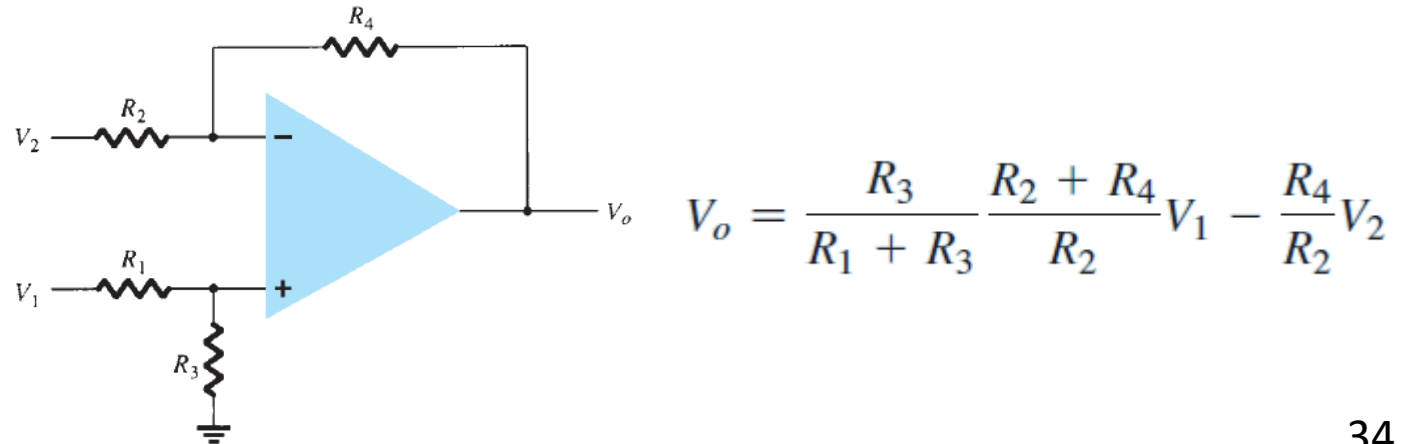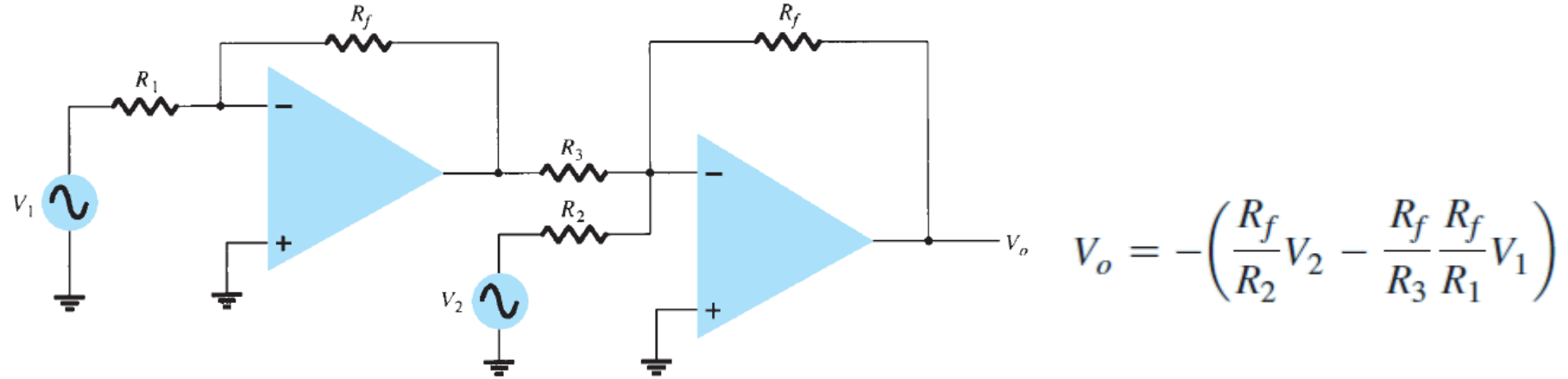

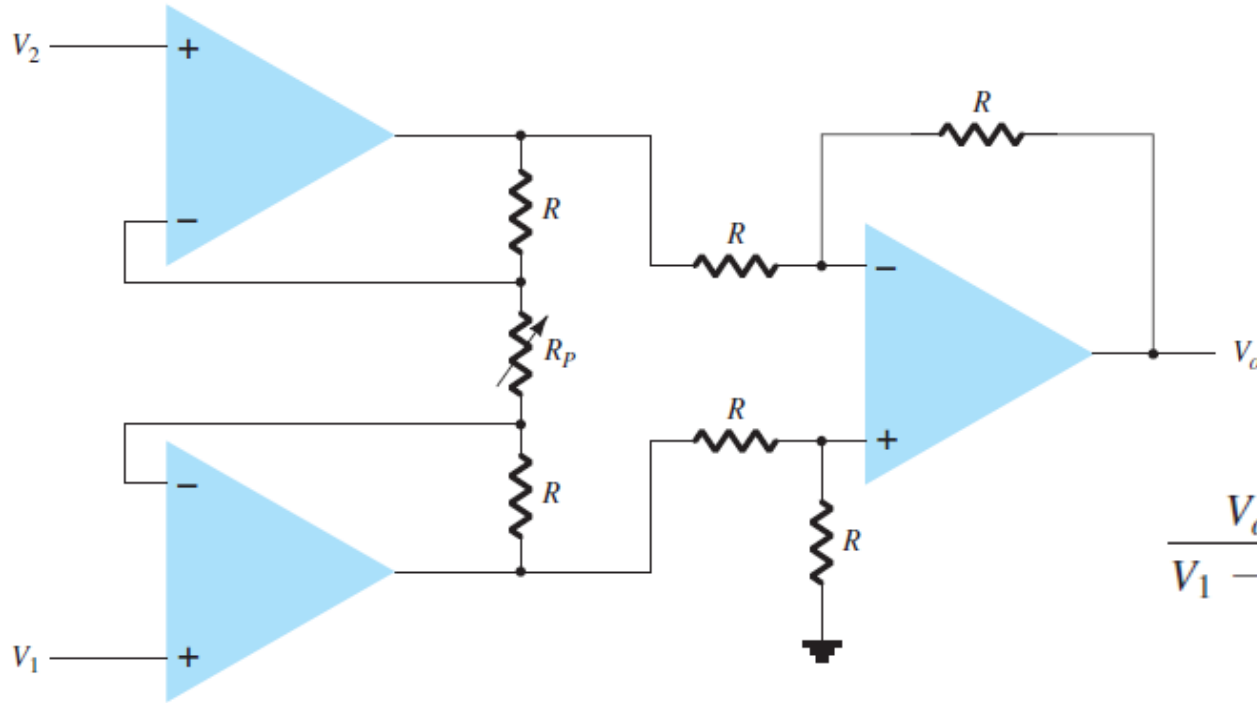


$$\frac{V_o}{V_1 - V_2} = 1 + \frac{2R}{R_p}$$



$$V_o = \left(1 + \frac{2R}{R_p}\right)(V_1 - V_2) = k(V_1 - V_2)$$

The background features a dark gray grid pattern. In the top right and bottom left corners, there are decorative wavy lines in a bright purple color, creating a modern, abstract aesthetic.


iTMO

Nonlinear Circuits

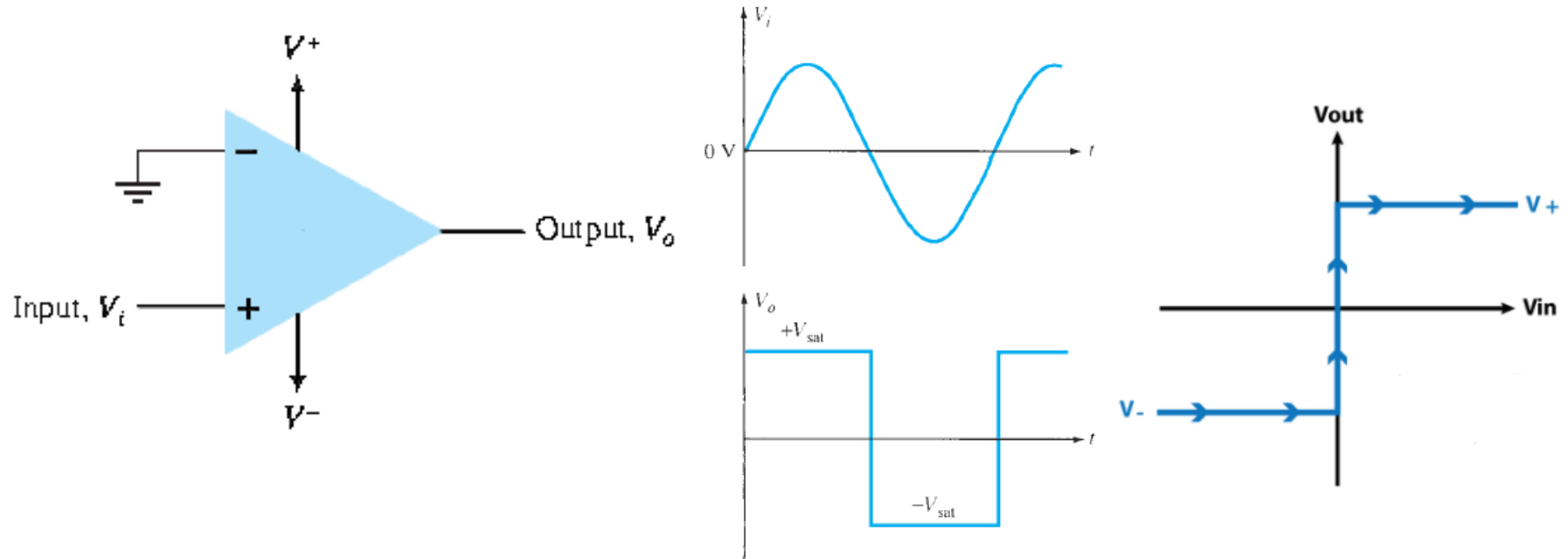

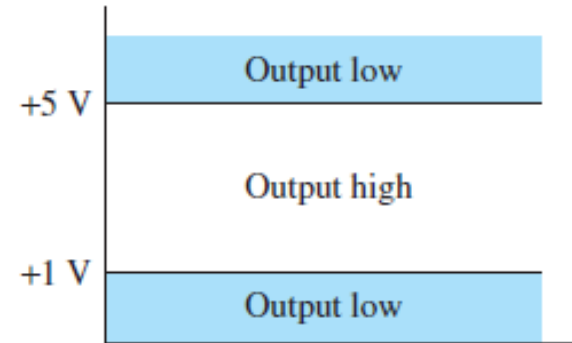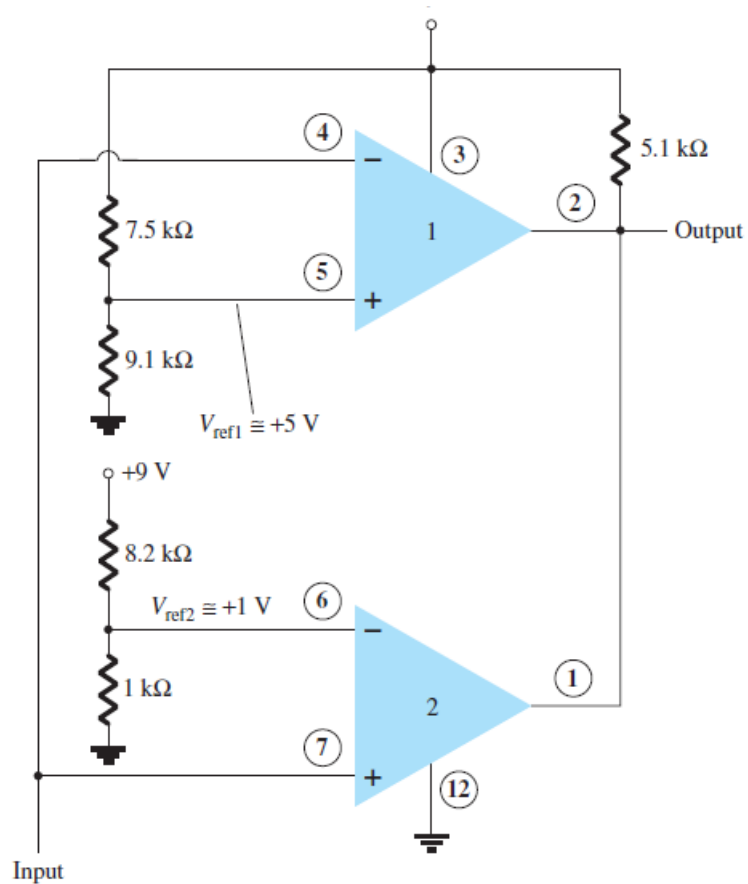

Schmitt trigger

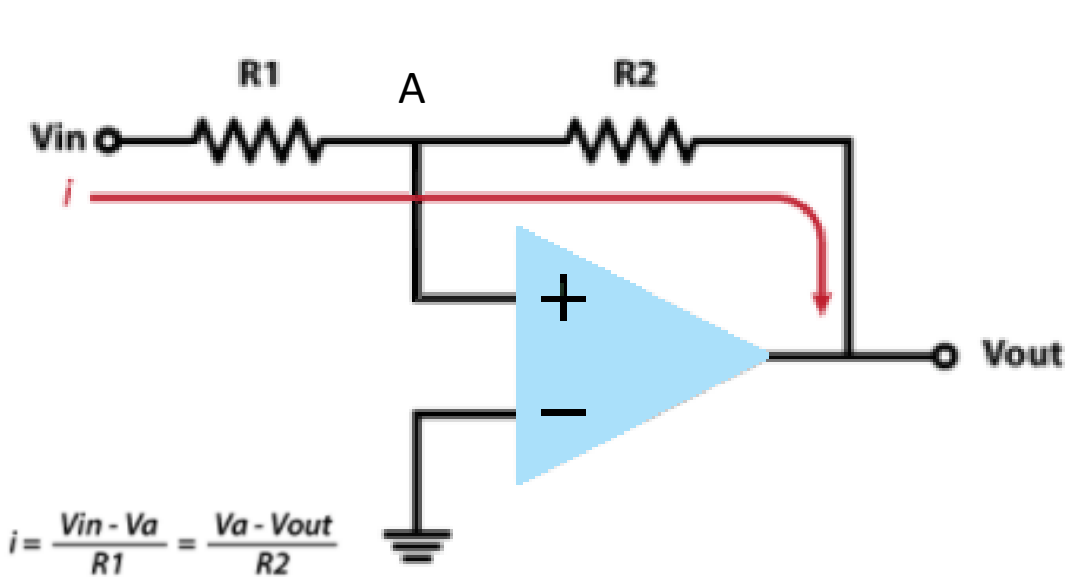


$$i = \frac{V_{in} - V_a}{R_1} = \frac{V_a - V_{out}}{R_2}$$

$$V_a = 0$$

$$\frac{V_{in}}{R_1} = -\frac{V_{out}}{R_2}$$

$$V_{in} = -\frac{R_1}{R_2} V_{out}$$


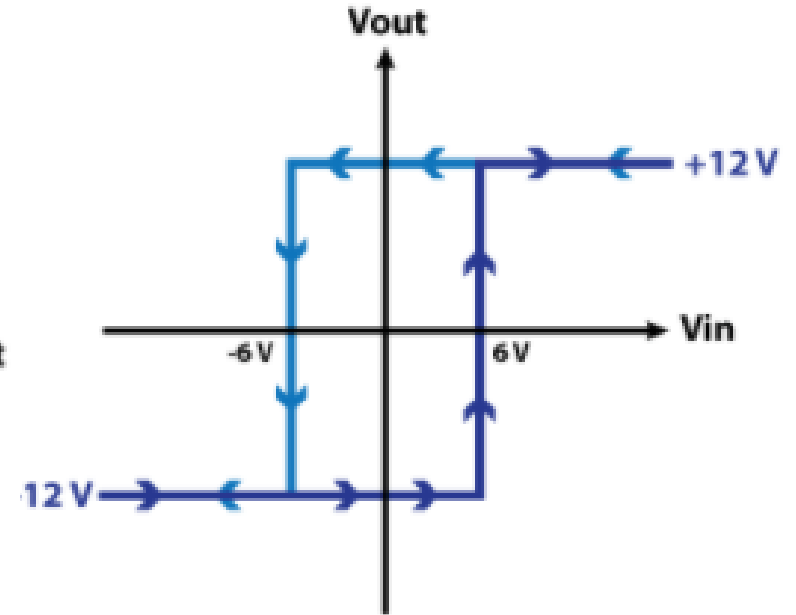


Example:

$$R_1 = 1\text{ K}; R_2 = 2\text{ K}; V_{out} = \pm 12\text{ V}$$

$$V_{in} = -\frac{1}{2} (\pm 12) = \pm 6\text{ V}$$

Non-Symmetrical Schmitt Trigger

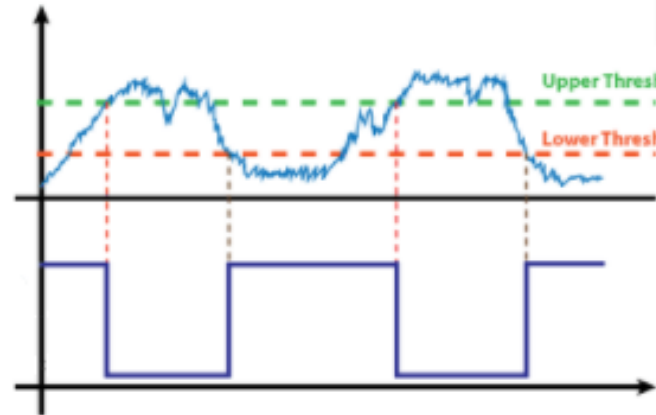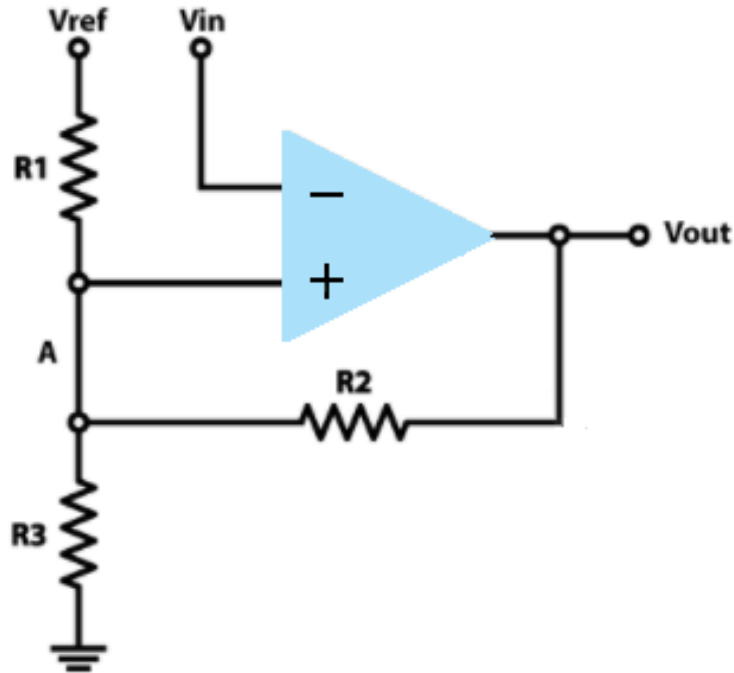

Inverted Output

Example:
 $R1, R2, R3 = 10K; V_{ref} = 5V$

$V_{out} = 0V$



$$V_a = \frac{R2 \parallel R3}{R1 + R2 \parallel R3} V_{ref}$$

$V_a = 1,66V$

$V_{out} = 5V$


$$V_a = \frac{R2}{R2 + R1 \parallel R3} V_{ref}$$

$V_a = 3,33V$

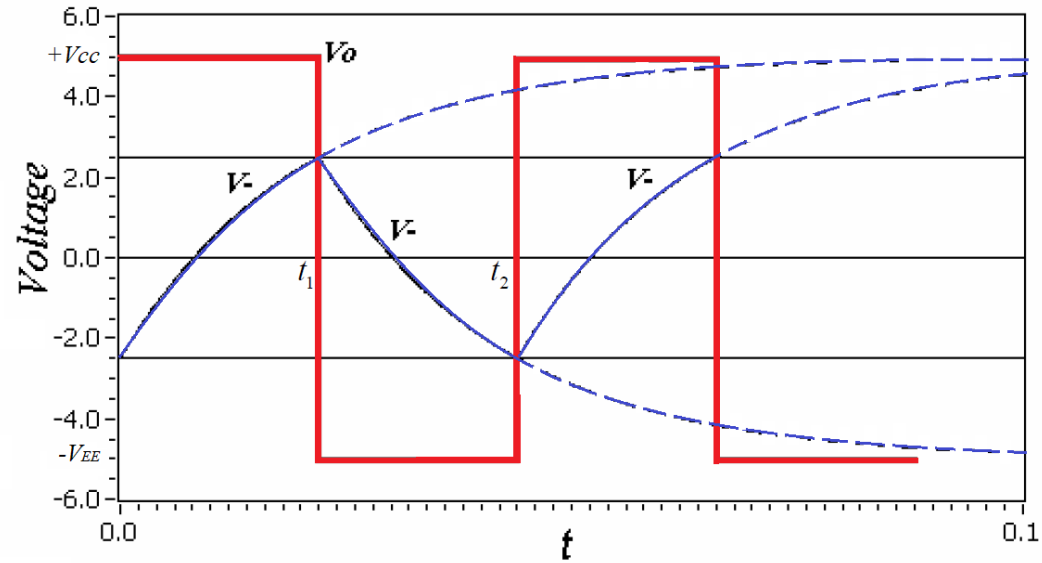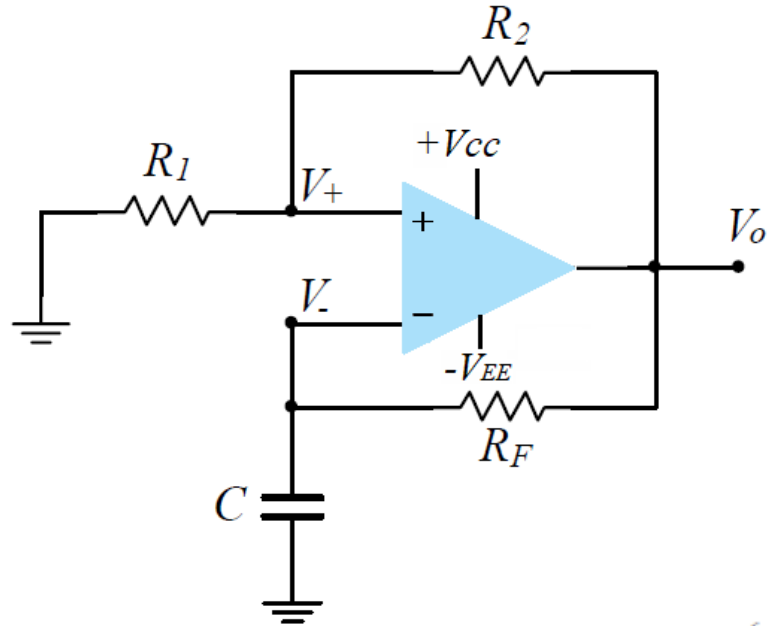

$$T = 2R_F C \ln \left(1 + 2 \frac{R_1}{R_2} \right)$$

Wien Bridge Oscillator

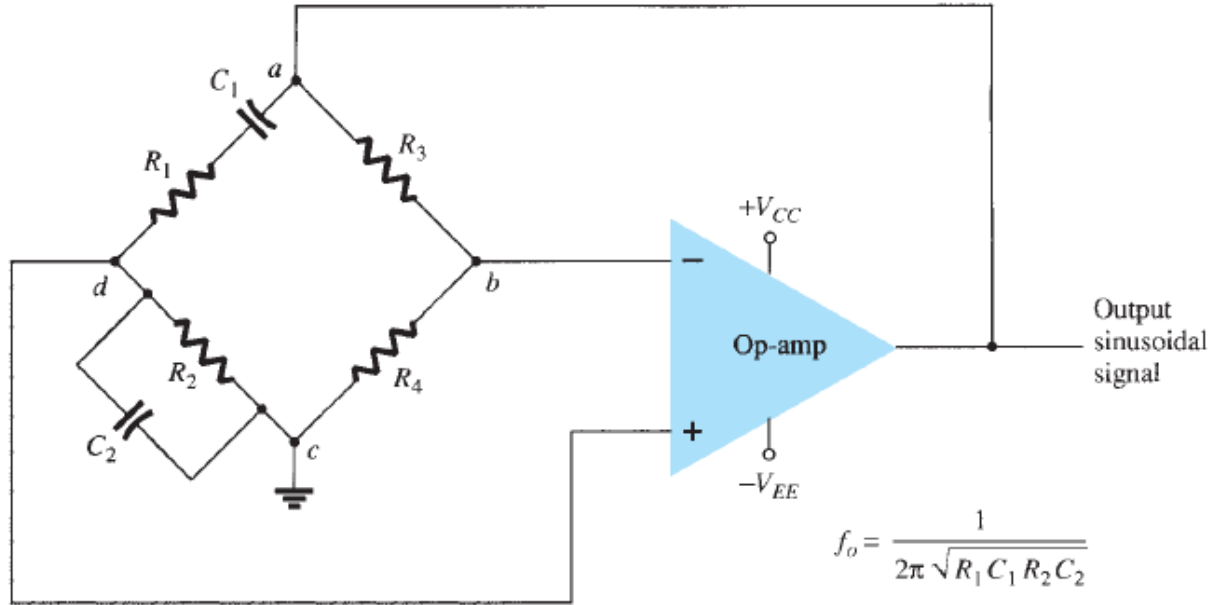

$$\frac{R_3}{R_4} = \frac{R_1}{R_2} + \frac{C_2}{C_1}$$


$$f_o = \frac{1}{2\pi\sqrt{R_1 C_1 R_2 C_2}}$$

If, in particular, the values are $R_1 = R_2 = R$ and $C_1 = C_2 = C$, the resulting oscillator frequency is

$$f_o = \frac{1}{2\pi RC}$$


$$\frac{R_3}{R_4} = 2$$
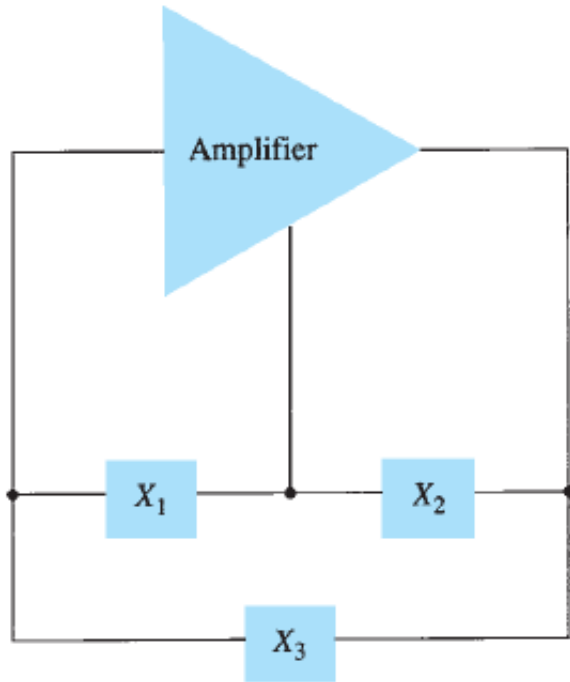
$$f_o = \frac{1}{2\pi\sqrt{R_1 C_1 R_2 C_2}}$$




<i>Oscillator Type</i>	<i>Reactance Element</i>		
	X_1	X_2	X_3
Colpitts oscillator	C	C	L
Hartley oscillator	L	L	C
Tuned input, tuned output	$ LC$	LC	—

Colpitts oscillator

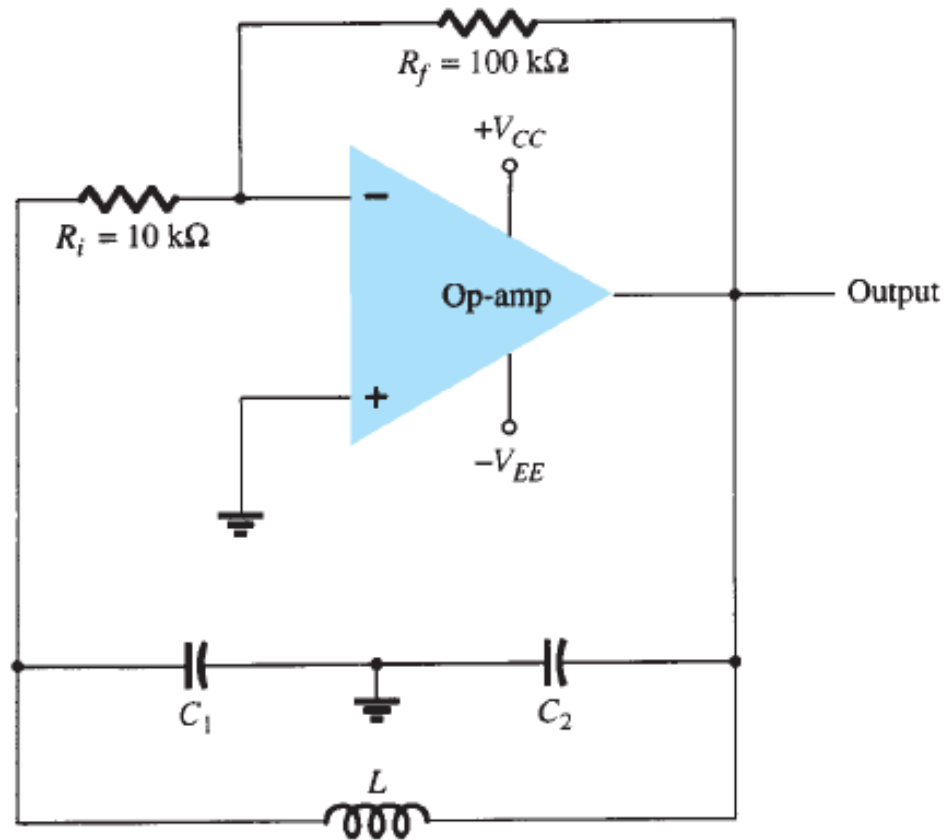

$$f_o = \frac{1}{2\pi\sqrt{LC_{eq}}}$$



$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

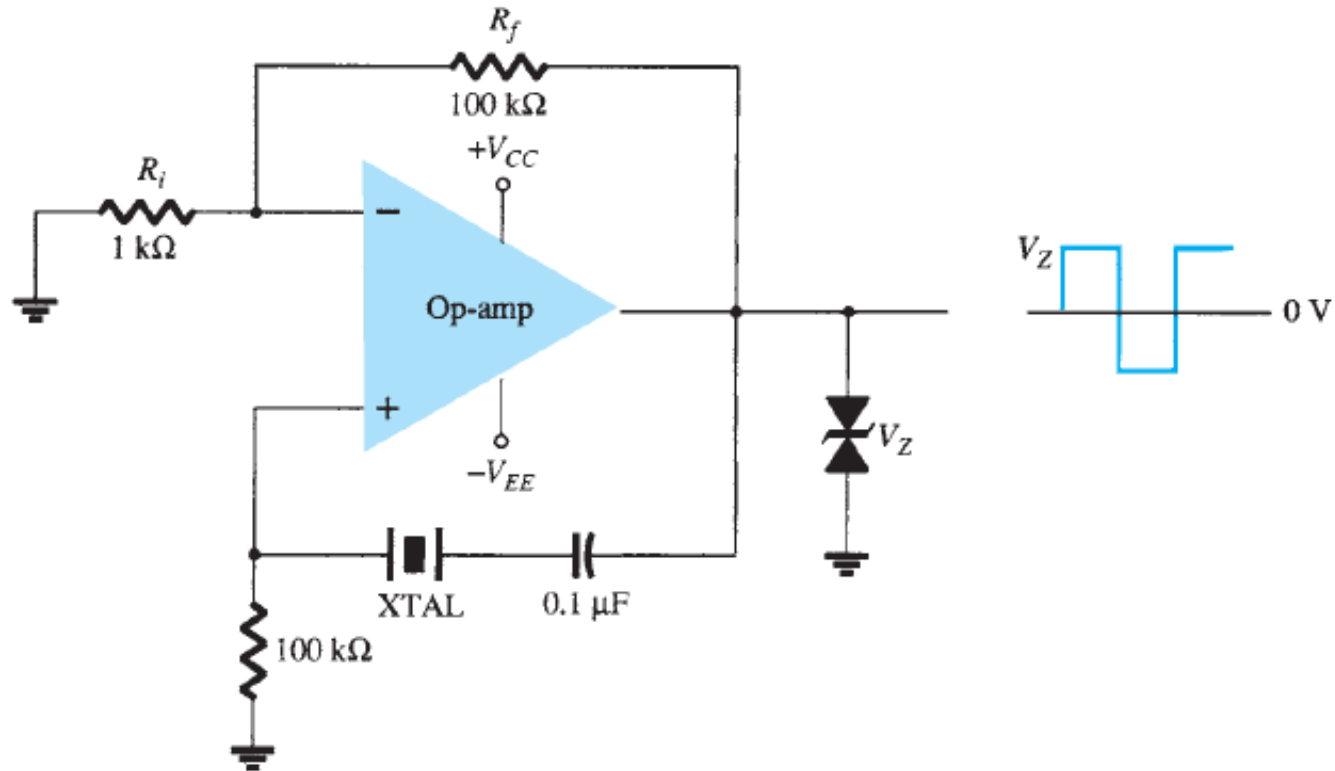




iTMO

Controlled Voltage Source

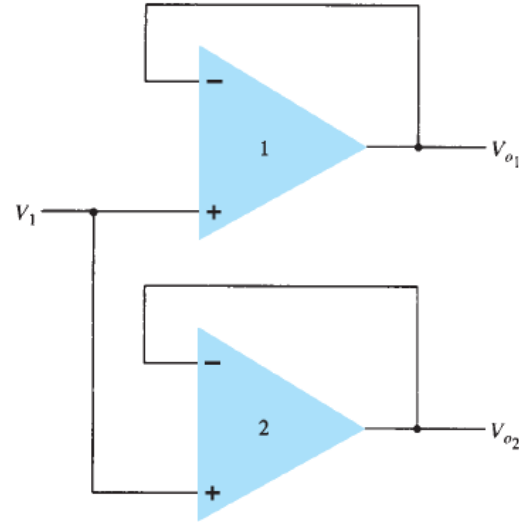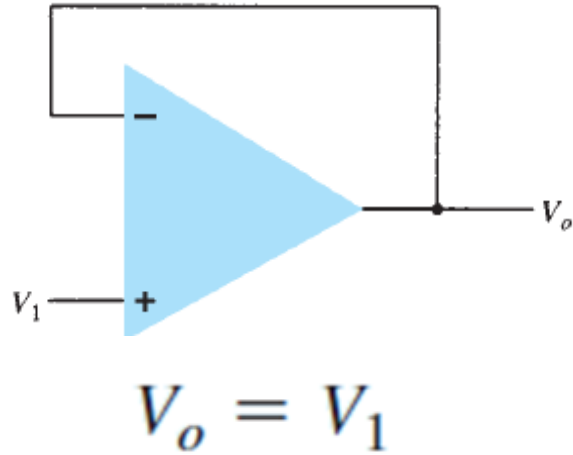


Advantages of Voltage Follower

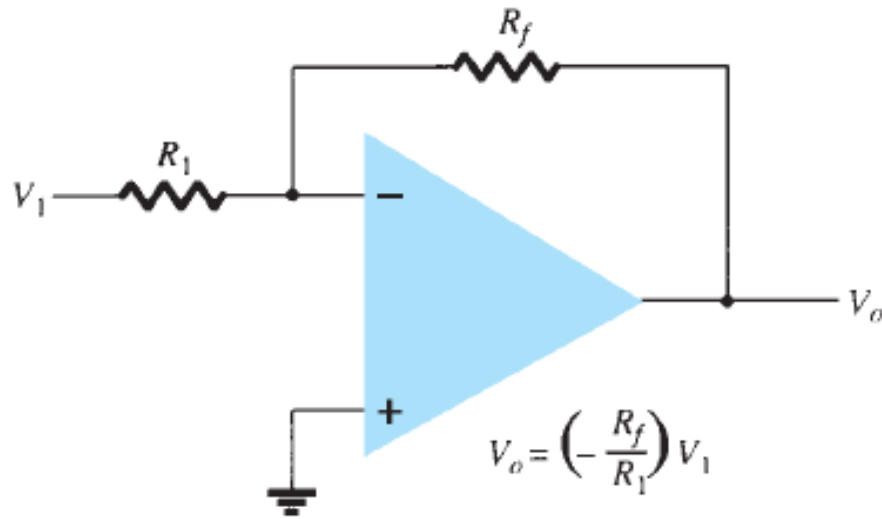1. Very large input resistance
2. Very low output resistance
3. Large bandwidth
4. The output follows the input exactly without any phase shift




$$V_o = -\frac{R_f}{R_1} V_1 = kV_1$$

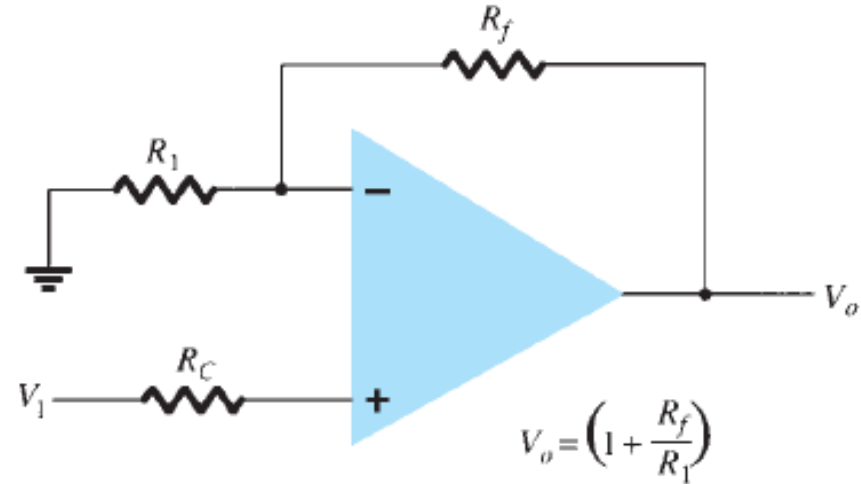


$$V_o = \left(1 + \frac{R_f}{R_1}\right) V_1 = kV_1$$


Voltage-Controlled Current Source

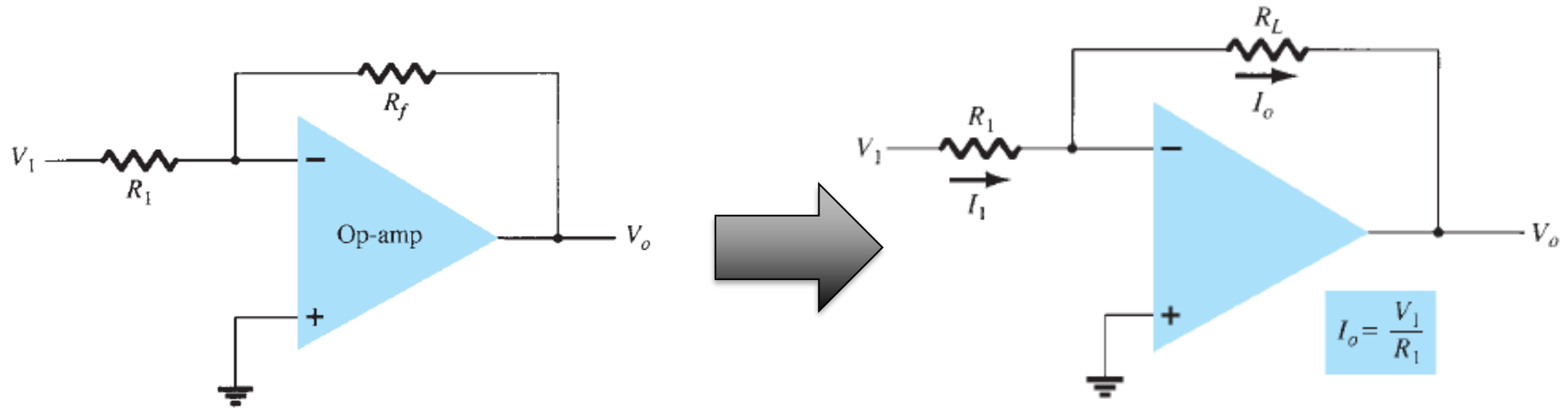

$$I_o = \frac{V_1}{R_1} = kV_1$$

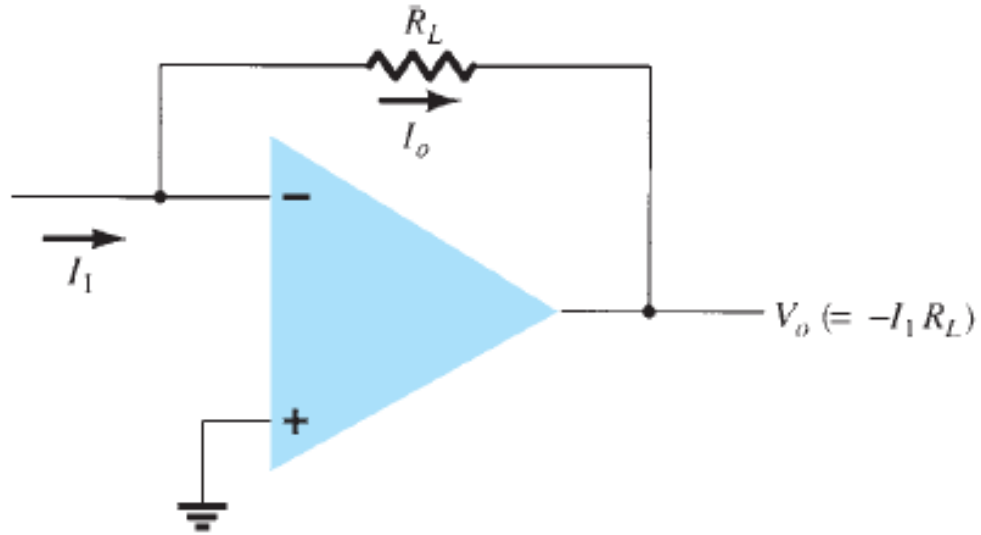

$$V_o = -I_1 R_L = kI_1$$

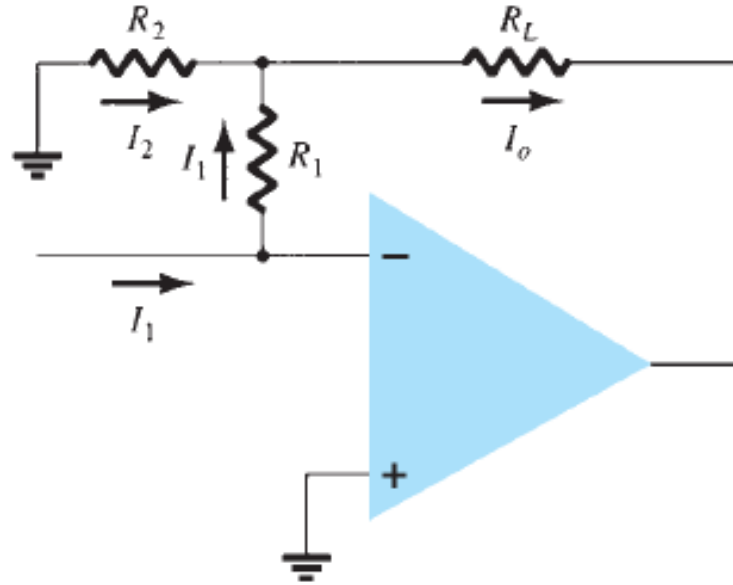

$$I_o = I_1 + I_2 = I_1 + \frac{I_1 R_1}{R_2} = \left(1 + \frac{R_1}{R_2}\right) I_1 = k I_1$$

1. Sarma M. S. Introduction to electrical engineering. – New York : Oxford University Press, 2001. – C. 715-716.
2. Boylestad, Robert L. Electronic devices and circuit theory / Robert L. Boylestad, Louis Nashelsky.—11th ed.
3. ISBN 978-0-13-262226-4 Scherz P., Monk S. Practical electronics for inventors. – McGraw-Hill Education, 2016.
4. Horowitz, Paul, and Winfield Hill. "The Art of Electronics. 3rd." *New York, NY, USA: University of Cambridge* (2015).
5. All about circuits (<https://www.allaboutcircuits.com/>)
6. <https://www.electronics-tutorials.ws/>
7. <https://en.wikipedia.org/>

The background features a dark gray grid pattern. In the top right and bottom left corners, there are decorative wavy lines in a bright purple color, creating a modern, tech-oriented aesthetic.

iTMO

Thank you for your attention!