



**ITMO**

# **Digital circuits design basics.**

## **Encoders, Decoders, Multiplexers, Flip-flops (SR, D, JK), Registers, Counters**

**Nikolay Nikolaev**

([nanikolaev@itmo.ru](mailto:nanikolaev@itmo.ru))

**Nikolai Poliakov**

([polyakov\\_n\\_a@itmo.ru](mailto:polyakov_n_a@itmo.ru))

**Arina Arbuzina**


([arbyzina99@gmail.com](mailto:arbyzina99@gmail.com))

- Combinational logic elements:
  - Multiplexers;
  - Encoders;
  - Decoders.
- Sequential logic elements:
  - Flip-flops (SR, D, JK);
  - Registers;
  - Counters.


In this section we consider some common digital system components, such as:

- decoders;
- encoders;
- multiplexers;
- demultiplexers

 A decoder is a combinational network that decodes (converts) the  $n$ -bit binary-coded input to  $m$  outputs ( $m \leq 2^n$ ). The block diagram of a 3-bit to 8-element decoder is shown in Figure, wherein the three inputs are decoded into eight outputs, one for each combination of the input variables.



# Decoder. True table.

 


$A_2$	$A_1$	$A_0$	$Q_7$	$Q_6$	$Q_5$	$Q_4$	$Q_3$	$Q_2$	$Q_1$	$Q_0$
0	0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

In the Figure you can see transformations of three binary combinations into respective output signals.

$000 \rightarrow Q_0$


$010 \rightarrow Q_2$


$101 \rightarrow Q_5$

 

Encoding is the process of forming an encoded representation of a set of inputs, and it is the converse of the decoding operation. An encoder is a combinational network that generates an  $n$ -bit binary code that uniquely identifies the one out of  $m$  activated inputs ( $0 \leq m \leq 2^n - 1$ ).

Figure shows the block diagram of an 8-element to 3-bit encoder.

 

 

$I_7$	$I_6$	$I_5$	$I_4$	$I_3$	$I_2$	$I_1$	$I_0$	$n_2$	$n_1$	$n_0$
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1




In the Figure you can see transformations of input signals to binary combinations.

$$I_1 \rightarrow 001$$



$$I_3 \rightarrow 010$$

$$I_5 \rightarrow 101$$

 


A *multiplexer* is a data selector.

  A multiplexer is a combinational network that selects one of several possible input signals and directs that signal to a single output terminal. The selection of a particular input is controlled by a set of selection variables. A multiplexer with  $n$  selection variables can usually select one out of  $2^n$  input signals.




$A_1$	$A_0$	$Out$
0	0	$I_1$
0	1	$I_2$
1	0	$I_3$
1	1	$I_4$

# Multiplexer. Example

 


 A demultiplexer (or data distributor) is the opposite of a multiplexer. It takes a single data input and routes it to one of several possible outputs. To select the output ( $Out_1$ ,  $Out_2$ ,  $Out_3$ , or  $Out_4$ ) to which you want to send the input signal, you apply logic levels to the data select inputs ( $S_0$ ,  $S_1$ )


 
# Demultiplexer. True Table.

Demultiplexer works according to the True Table.




$A_1$	$A_0$	Output
0	0	$Out_1 = In$
0	1	$Out_2 = In$
1	0	$Out_3 = In$
1	1	$Out_4 = In$

In this section we consider some common Sequential logic components, such as:


- Flip-flops (SR, D, JK);
- Registers;
- Counters.

 The symbol for the SRFF and True table are shown in Figure.



<i>Input</i>		<i>Output</i>	
$In_1$	$In_2$	$Q_{n+1}$	$\bar{Q}_{n+1}$
0	0	$Q_n$	$\bar{Q}_n$
0	1	0	1
1	0	1	0
1	1	Not allowed	

 The symbol for the SRFF and True table are shown in Figure.




<i>Input</i>		<i>Output</i>	
$In_1$	$In_2$	$Q_{n+1}$	$\bar{Q}_{n+1}$
0	0	$Q_n$	$\bar{Q}_n$
0	1	0	1
1	0	1	0
1	1	Not allowed	

Can we construct SRFF by using combinations of logic blocks?



 The symbol for the SRFF and True table are shown in Figure.




<i>Input</i>		<i>Output</i>	
$In_1$	$In_2$	$Q_{n+1}$	$\bar{Q}_{n+1}$
0	0	$Q_n$	$\bar{Q}_n$
0	1	0	1
1	0	1	0
1	1	Not allowed	

Can we construct SRFF by using combinations of logic blocks?


Yes, we can!

We can make SRFF from two types of basic elements – NAND and NOR

Cross-NAND SR flip-flop

 


Cross-NOR SR flip-flop

 



 
# Level-Triggered SR Flip-Flop

**Level-Triggered SR Flip-Flop** – this is a synchronous flip-flop—meaning making the  $S$  and  $R$  inputs either enabled or disabled by a control pulse.






$C_k$	S	R	Q	$\bar{Q}$	Mode
0	0	0	Q	$\bar{Q}$	Hold
0	0	1	Q	$\bar{Q}$	Hold SR-inputs
0	1	0	Q	$\bar{Q}$	Hold disabled
0	1	1	Q	$\bar{Q}$	Hold
1	0	0	0	0	Hold
1	0	1	0	1	RESET SR-inputs
1	1	0	1	0	SET enabled
1	1	1	Q	$\bar{Q}$	Inderterminate

   An edge-triggered flipflop samples the inputs only during either a positive or negative clock edge ( $\uparrow$  = positive edge,  $\downarrow$  = negative edge).




Positive edge-triggered

   


Negative edge-triggered


Simple SRFF

 

level triggered

 


edge-triggered

 

positive edge-triggered input



edge-triggered

 


negative edge-triggered input



D FLIP-FLOP (LATCH OR DELAY ELEMENT).

 
A D-type flip-flop is a single input device. It is basically an SR flipflop, where  $S$  is replaced with  $D$  and  $R$  is replaced  $\bar{D}$  (inverted  $D$ ).



D	Q	$\bar{Q}$	Mode
0	0	1	Reset
1	1	0	Set

D FLIP-FLOP (LATCH OR DELAY ELEMENT).

 A D-type flip-flop is a single input device. It is basically an SR flipflop, where  $S$  is replaced with  $D$  and  $R$  is replaced  $\bar{D}$  (inverted  $D$ ).




D	Q	$\bar{Q}$	Mode
0	0	1	Reset
1	1	0	Set

How can we make D-type flip-flop?



D FLIP-FLOP (LATCH OR DELAY ELEMENT).


 
A D-type flip-flop is a single input device. It is basically an SR flipflop, where  $S$  is replaced with  $D$  and  $R$  is replaced  $D$  (inverted  $D$ ).





D	Q	$\bar{Q}$	Mode
0	0	1	Reset
1	1	0	Set

How can we make D-type flip-flop?

  Of course, we can make D flip-flop from logic elements and also from SRFF.







 
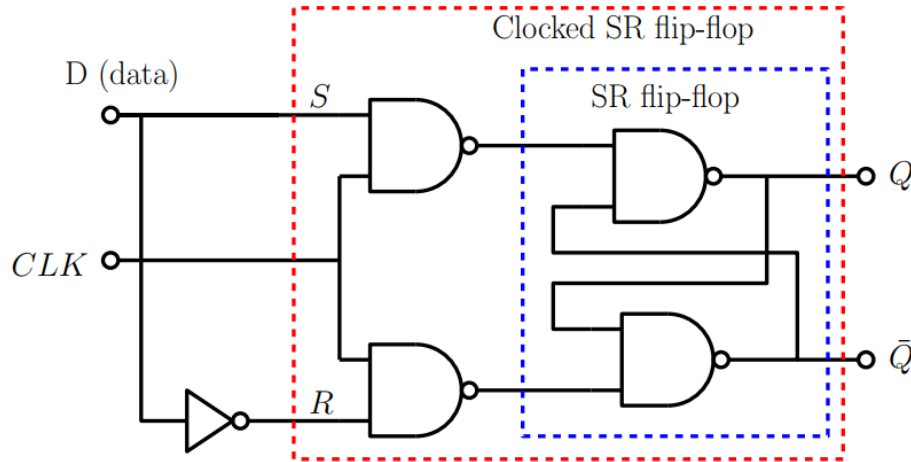
Also we can make a clocked D-type level-triggered flip-flop.




Input		Output		
CLK	D	Q	Q̄	Mode
0	X	Q	Q̄	Hold
1	0	0	1	Reset
1	1	1	0	Set

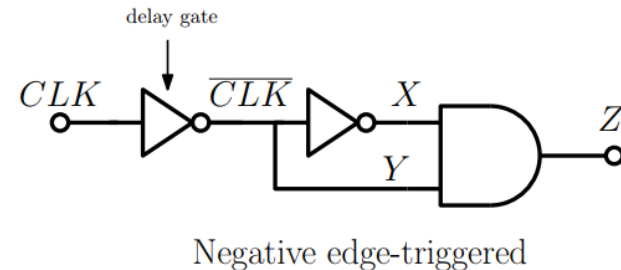  Also we can make a clocked, edge-triggered D-type flip-flop .




   


Stop-Go indicator

 




Divide-by-two counter

 

Synchronizer

 

   What would happen if D flip-flop wasn't in place





A JK flip-flop resembles an SR flip-flop, where  $J$  acts like  $S$  and  $K$  acts like  $R$ . However, unlike the SR flip-flop, which has an indeterminate mode when  $S = 1, R = 1$ , the JK flip-flop has a *toggle* mode when  $J = 1, K = 1$ . *Toggle* means that the  $Q$  and  $\bar{Q}$  outputs switch to their opposite states at each active clock edge.

As D flip-flop we can make JK flip-flop based on SRFF.


To make a JK flip-flop, modify the SR flip-flop's internal logic circuit to include two cross-coupled feedback lines between the output and input. This modification, however, means that the JK flip-flop cannot be level-triggered; it can only be edge-triggered or pulse-triggered.

## Positive edge-triggered

  



$C_k$	J	K	Q	$\bar{Q}$	Mode
0	X	X	Q	$\bar{Q}$	Hold
1	X	X	Q	$\bar{Q}$	Hold
↓	X	X	Q	$\bar{Q}$	Hold
↑	0	0	Q	$\bar{Q}$	Hold
↑	0	1	0	1	Reset
↑	1	0	1	0	Set
↑	1	1	Q	Q	Toggle

edge-triggered

 


positive edge-triggered input

## Negative edge-triggered

  

$C_k$	J	K	Q	$\bar{Q}$	Mode
0	X	X	Q	$\bar{Q}$	Hold
1	X	X	Q	$\bar{Q}$	Hold
↑	X	X	Q	$\bar{Q}$	Hold
↓	0	0	Q	$\bar{Q}$	Hold
↓	0	1	0	1	Reset
↓	1	0	1	0	Set
↓	1	1	Q	Q	Toggle

edge-triggered

 


negative edge-triggered input






Data words traveling through a digital system frequently must be temporarily held, copied, and bit-shifted to the left or to the right. A device that can be used for such applications is the *shift register*. There are three types of shift register arrangements:

 - serial-in/serial-out,
- parallel-in/parallel-out
- parallel-in/serial-out and serial-in/parallel out.



 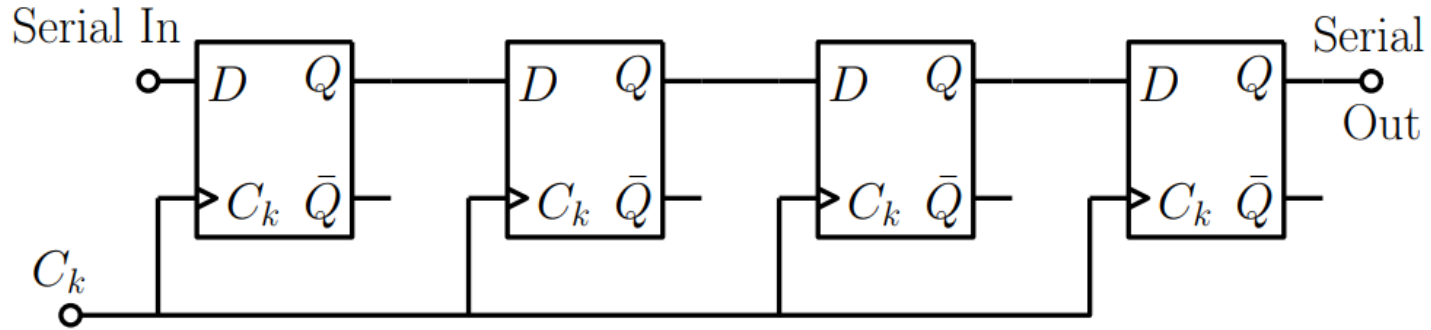
## Simple example - *Serial-In/Serial-Out Shifter Registers*




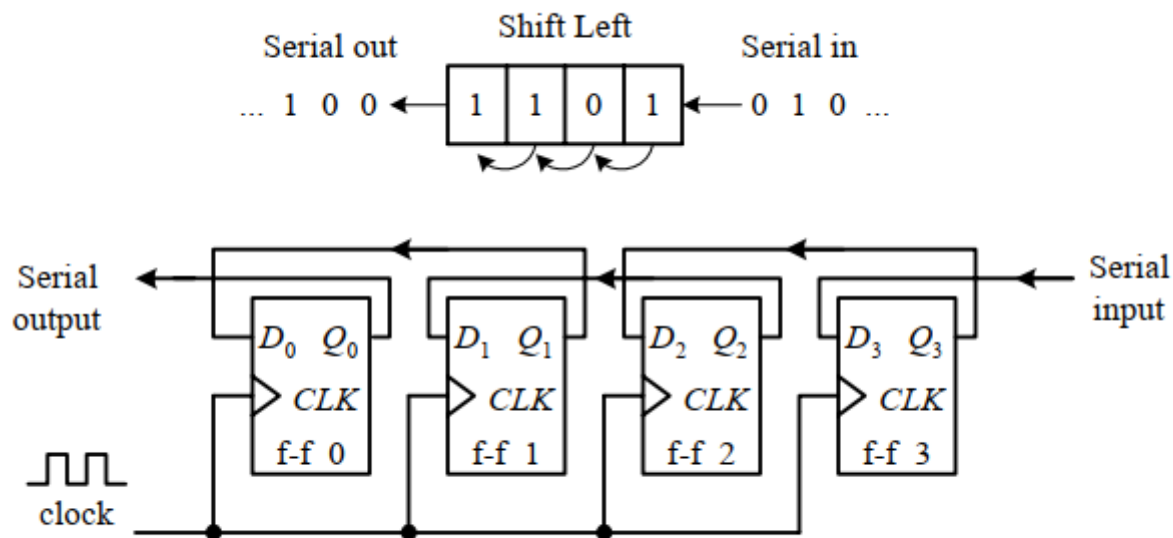

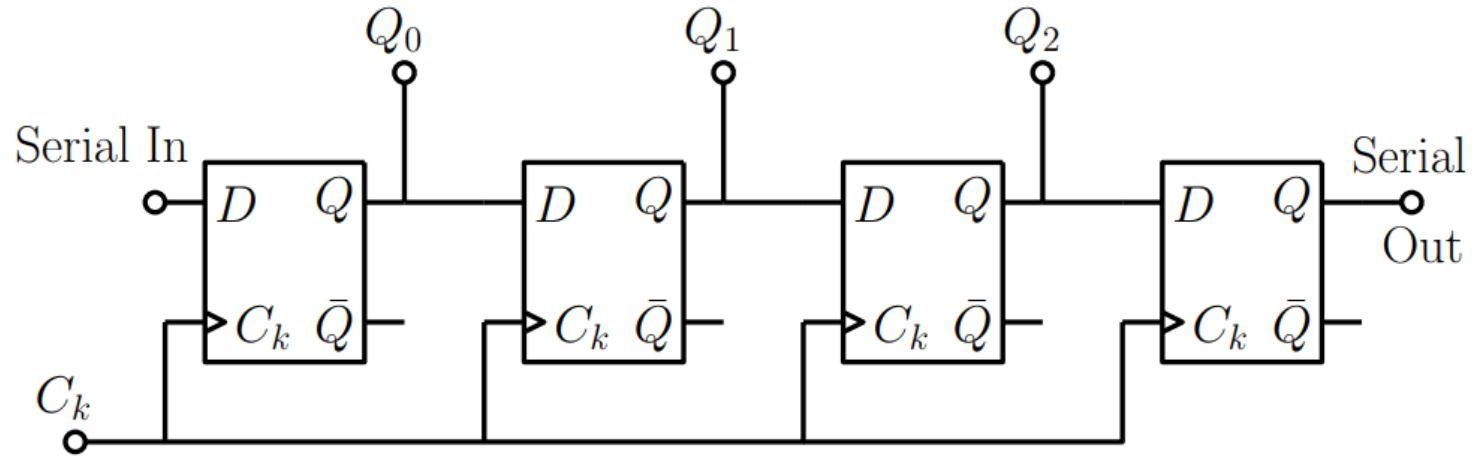Simple example - *Serial-In/Parallel-Out Shift Registers*


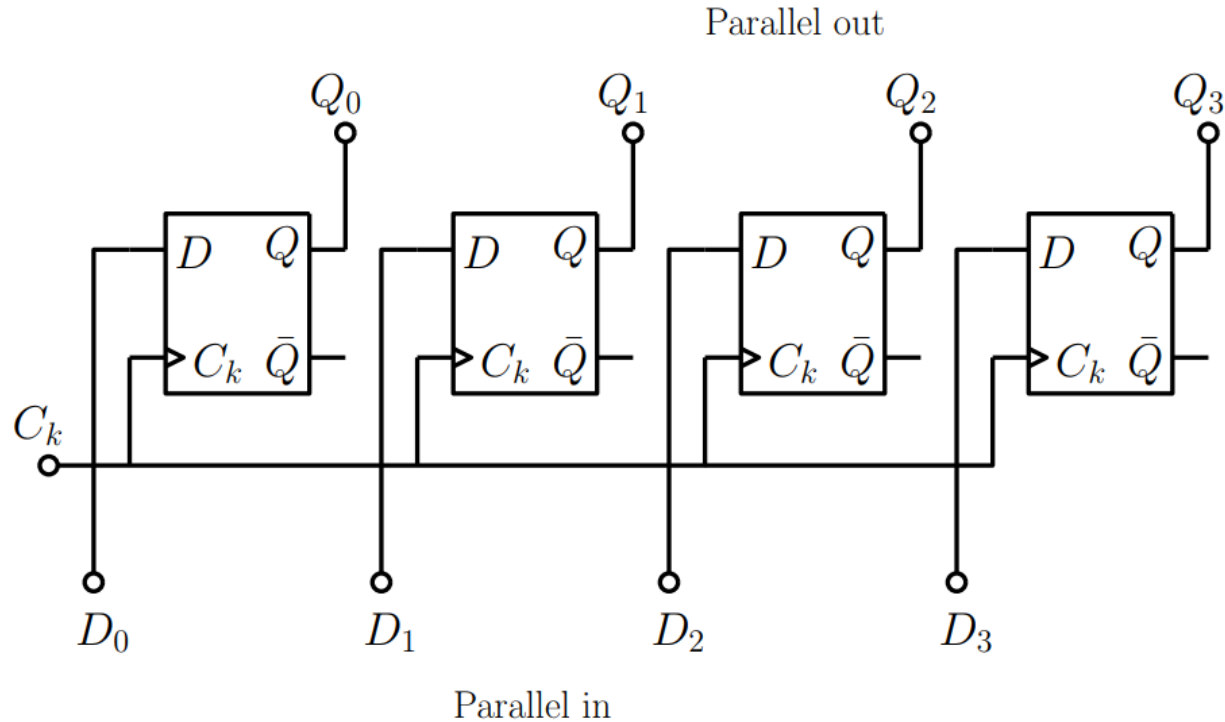
## Simple example - *Parallel-In/Parallel-Out Shift Registers*




The shift register can be used as a counter because the data are shifted for each clock pulse. A counter is a register that goes through a predetermined sequence of states when input pulses are received. Besides, computers, timers, frequency meters, and various other digital devices contain counters for counting events.


There are some types of counters:

- *ripple (asynchronous),*
- *synchronous,*
- *ring.*

## Ripple Counter (Asynchronous Counter)

 


## Synchronous Counter

 



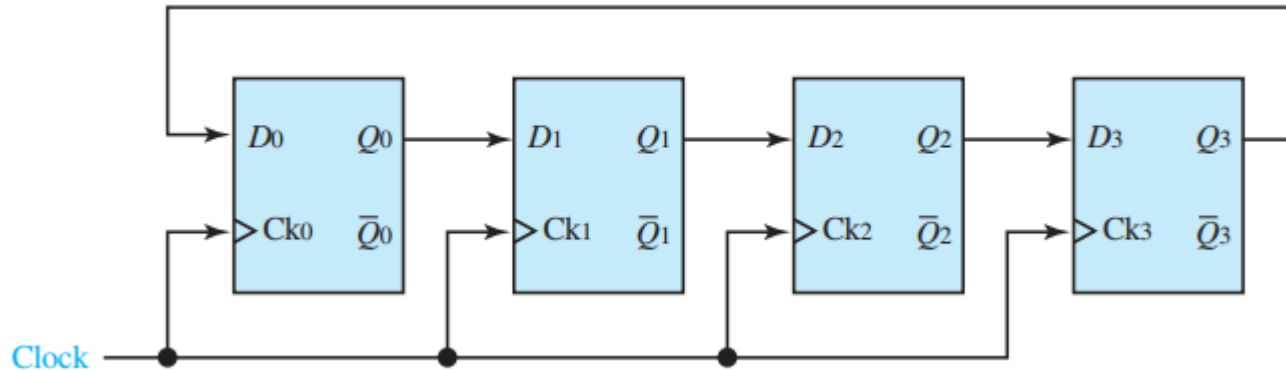
## ***Ring Counter (Shift Register Sequencer).***

The ring counter (shift register sequencer) is a unique type of shift register that incorporates feedback from the output of the last flip-flop to the input of the first flip-flop.




## Mechanics of adding

 


MSB addition			LSB addition	
$A_1$	$B_1$	$C_{in}$	$\Sigma_1$	$C_{out}$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


## Half-adder

 


## alternative representation

 


## half-adder symbol

 


## Full-adder

 


## full-adder symbol

 

## 4-bit adder

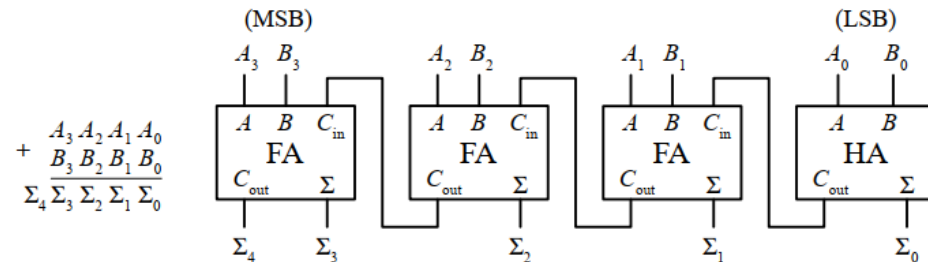

## Mechanics of adding

 


### MSB addition

$A_1$	$B_1$	$C_{in}$	$\Sigma_1$	$C_{out}$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


### LSB addition

$A_0$	$B_0$	$\Sigma_0$	$C_{out}$
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


## Half-adder

 


### alternative representation

 


### half-adder symbol

 


## Full-adder

 

### full-adder symbol

 


## 4-bit adder

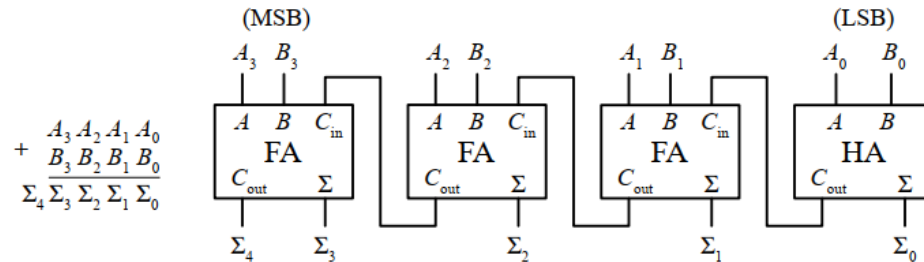


## 74HC00 Series

Quad 2-input  
NAND

 


7400, 74LS00,  
74F00, 74HC00, etc.

Quad 2-input  
NOR

 


7402, 74LS02,  
74F02, 74HC02, etc.

Hex Inverter

 


7404, 74LS04,  
74F04, 74HC04, etc.

Quad 2-input  
AND

 


7408, 74LS08,  
74F08, 74HC08, etc.

Triple 3-input  
NAND

 


7410, 74LS10,  
74F10, 74HC10, etc.

Triple 3-input  
AND

 


7411, 74LS11,  
74F11, 74HC11, etc.

Dual 4-input  
NAND

 


7420, 74LS20,  
74F20, 74HC20, etc.

Dual 4-input  
AND

 


7421, 74LS21,  
74F21, 74HC21, etc.

Triple 3-input  
NOR

 


7427, 74LS27,  
74F27, 74HC27, etc.

8-input NAND

 


7430, 74LS30,  
74F30, 74HC30, etc.

Quad 2-input  
OR

 

7432, 74LS32,  
74F32, 74HC32, etc.


Quad 2-input  
XOR

 

7486, 74LS86,  
74F86, 74HC86, etc.


## 74HC00 Series

Quad 2-input  
NAND

 


7400, 74LS00,  
74F00, 74HC00, etc.

Quad 2-input  
NOR

 


7402, 74LS02,  
74F02, 74HC02, etc.

Hex Inverter

 


7404, 74LS04,  
74F04, 74HC04, etc.

Quad 2-input  
AND

 


7408, 74LS08,  
74F08, 74HC08, etc.

Triple 3-input  
NAND

 


7410, 74LS10,  
74F10, 74HC10, etc.

Triple 3-input  
AND

 


7411, 74LS11,  
74F11, 74HC11, etc.

Dual 4-input  
NAND

 


7420, 74LS20,  
74F20, 74HC20, etc.

Dual 4-input  
AND

 


7421, 74LS21,  
74F21, 74HC21, etc.

Triple 3-input  
NOR

 


7427, 74LS27,  
74F27, 74HC27, etc.

8-input NAND

 


7430, 74LS30,  
74F30, 74HC30, etc.

Quad 2-input  
OR

 



7432, 74LS32,  
74F32, 74HC32, etc.

Quad 2-input  
XOR

 


7486, 74LS86,  
74F86, 74HC86, etc.

  Acceptable TTL Gate  
Input Signal Levels




 Acceptable TTL Gate  
Output Signal Levels





Acceptable TTL Gate  
Input Signal Levels

 Acceptable TTL Gate  
Output Signal Levels



  
# Voltage Tolerance of CMOS Gate Inputs

Acceptable CMOS Gate  
Input Signal Levels




 
Acceptable CMOS Gate  
Output Signal Levels






# CMOS Noise Margin



Acceptable CMOS Gate Input Signal Levels

  

 
Acceptable CMOS Gate Output Signal Levels



Acceptable CMOS Gate Input Signal Levels

  

 
Acceptable CMOS Gate Output Signal Levels



1. Sarma M. S. Introduction to electrical engineering. – New York : Oxford University Press, 2001. – C. 715-716.
2. Tokheim R. L. Digital Electronics: Principles and Applications, 8th Edition. – McGraw-Hill, Inc., 2014.
3. Kleitz W. Digital Electronics: A practical approach with VHDL. – Prentice Hall, 2011.
4. Harris S., Harris D. Digital design and computer architecture: arm edition. – Morgan Kaufmann, 2015.
5. Paul Scherz, Simon Monk. Practical Electronics for Inventors, Fourth Edition. - McGraw-Hill, Inc., 2016.

<https://forms.yandex.com/cloud/635481a073cee77f17e7626e/>

<https://clck.ru/32Skte>

 

The background features a dark gray grid pattern. In the top right and bottom left corners, there are decorative wavy lines in a bright purple color, creating a modern, tech-oriented aesthetic.

**iTMO**

**Thank you for your attention!**