



# Laboratory work №4

## Simple digital circuits design and simulation

Nikolay Nikolaev

([nanikolaev@itmo.ru](mailto:nanikolaev@itmo.ru))

Nikolai Poliakov

([polyakov\\_n\\_a@itmo.ru](mailto:polyakov_n_a@itmo.ru))

Arina Arbuzina

([arbyzina99@gmail.com](mailto:arbyzina99@gmail.com))

## 1. A typical inverter circuit using a bipolar transistor.

A typical inverter circuit using a bipolar transistor is shown in Figure 1.



 
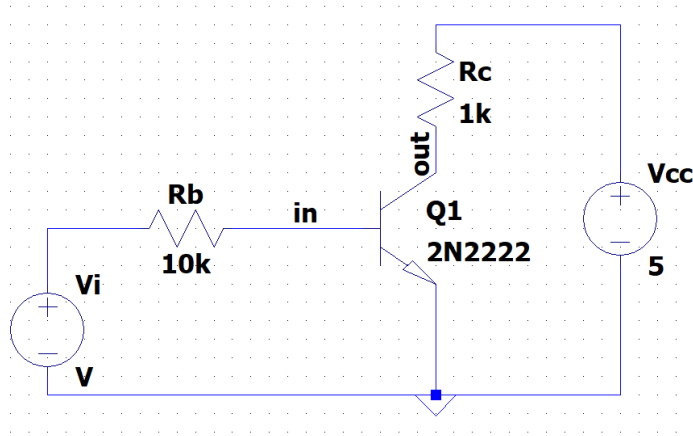
 
 
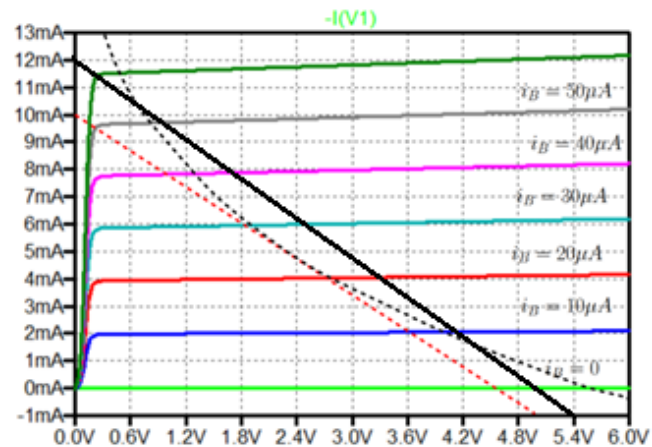


Figure 1 - A typical inverter circuit and volt-ampere characteristic

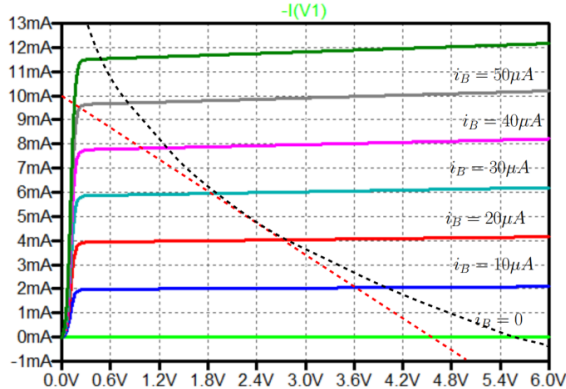

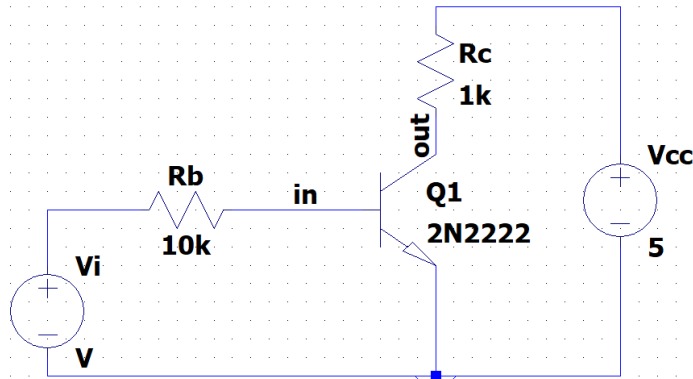

Consider main relationships for transistor switch.



For output load line drawing we need to consider Kirchhoff's voltage law for output circuit

$$V_{CE} = V_{CC} - R_C i_C$$

For input load line drawing we need to consider Kirchhoff's voltage law for input circuit

$$V_{BE} = V_i - R_B i_B$$

  Consider levels of analog input signals – as logic “0” we consider signal over 0 V and as logic “1” we consider signal over 5 V.





For logic 0 the base current is zero. Transistor is said to be cut off (off), only a very small value of collector current flows. In cut off state for output voltage we have logical 1 level

$$V_{out} = V_{CE_{cut\ off}} \cong V_{CC} - R_C i_{CE0} \cong V_{CC} = 5\text{ V}.$$

For logic 1 the base current is not zero

$$I_{B_{sat}} = \frac{V_i - V_{BE}}{R_B}$$

 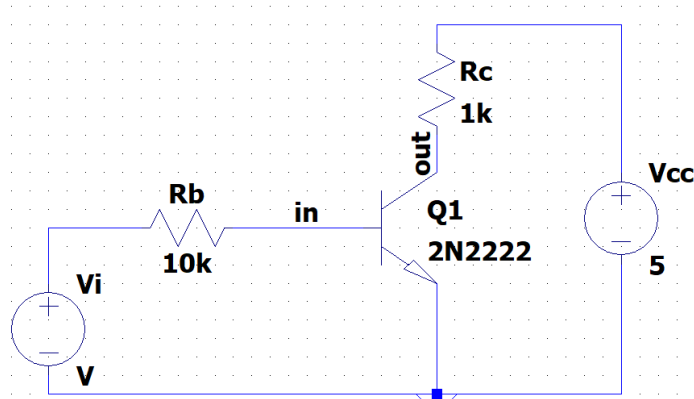where  $V_{BE} \cong 0.7\text{ V}$  which is the threshold voltage.  $R_B$  is chosen to drive the transistor into saturation.



In the saturated state  $V_{CEsat} = 0.2 \dots 0.3 \text{ V}$  (this is typically value).

$$I_{Csat} = \frac{V_{CC} - V_{CEsat}}{R_C} \cong \frac{V_{CC}}{R_C}.$$


It can be shown that saturation will occur when

$$\frac{V_i - V_{BE}}{R_B} > \frac{V_{CC} - V_{CEsat}}{\beta R_C}.$$

Since  $i_C \cong \beta i_B + I_{CE0}$ , then for saturated state we need

$$i_{Bsat} > i_{Csat} / \beta, \text{ such as}$$
 
$$I_{Csat} = \frac{V_{CC} - V_{CEsat}}{R_C}$$




then

$$I_{B_{sat}} = \frac{V_{CC} - V_{CE_{sat}}}{\beta R_C}$$



We choose current value as

$$i_B = k \frac{V_{CC} - V_{CE_{sat}}}{\beta R_C}$$

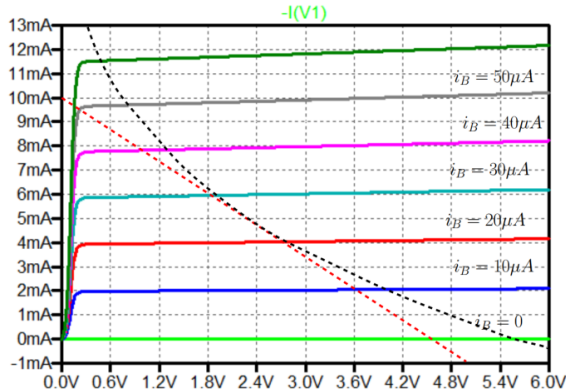where  $k$  is a coefficient of desired overdrive (usually  $k = 2 \dots 3$ ).



# Transistor switch mode

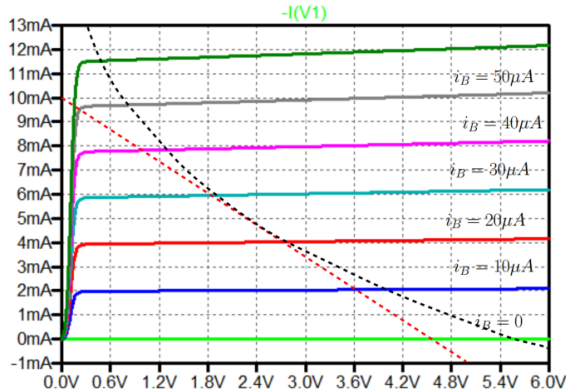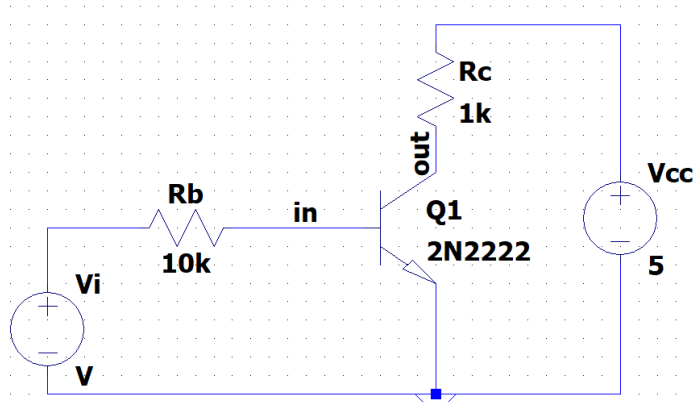

For example, we consider transistor 2N2222.

We need to choose current value  $I_C$  it must be not more than maximum value of transistor current  $I_{C_{max}}$  (for 2N2222  $I_{C_{max}} = 0.6 A$ , see table from datasheet).



We choose  $I_C = 10 mA$ . Then for  $R_C$  we have

$$R_C = \frac{V_{CC} - V_{CE_{sat}}}{I_C} \cong \frac{V_{CC}}{I_C} = \frac{5}{0.01} = 500 \Omega.$$

Now we can plot load line on the output volt–ampere characteristic (VAC) and maximum collector dissipation line.

Collector Current	$I_C$	600	mA
Power Dissipation	$P_{tot}$	625	mW



 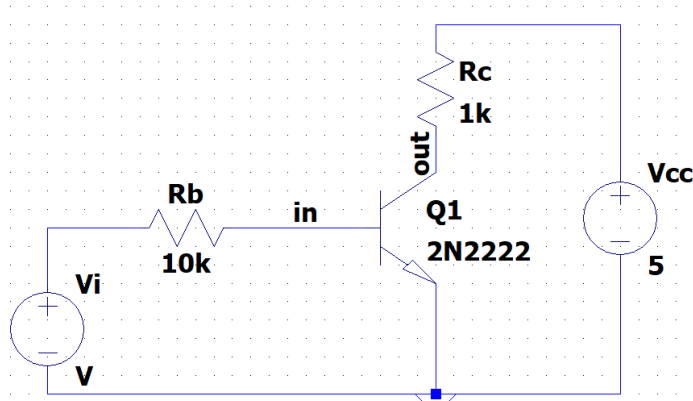

Chose value of  $i_B$


$$i_B = k \frac{V_{CC} - V_{CEsat}}{\beta R_C} \cong k \frac{V_{CC}}{\beta R_C}$$

For  $k = 3$  and  $\beta = 100$  (we found this value in transistor datasheet) we have

$$i_B = k \frac{V_{CC} - V_{CEsat}}{\beta R_C} = 3 \frac{5}{100 \cdot 500} = 0.3 \text{ mA.}$$

Now we need find value of  $R_B$


$$R_B = \frac{V_i - V_{BE}}{I_B},$$

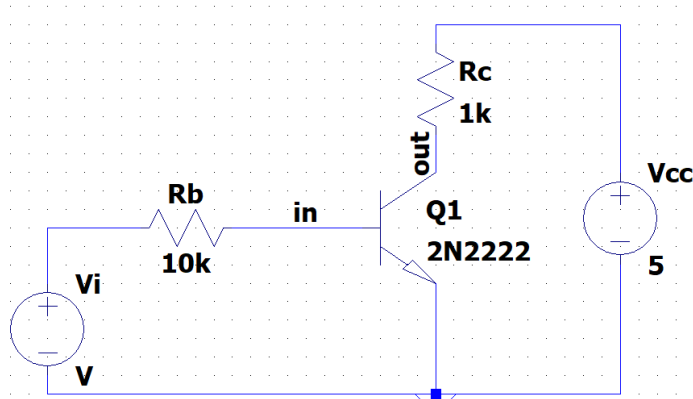


For  $V_i = 5\text{ V}$  we have

$$R_B = \frac{V_i - V_{BE}}{I_B} = \frac{5 - 0.7}{0.0003} = 14333.3\ \Omega$$

We chose  $R_B = 15\text{ k}\Omega$ .

 

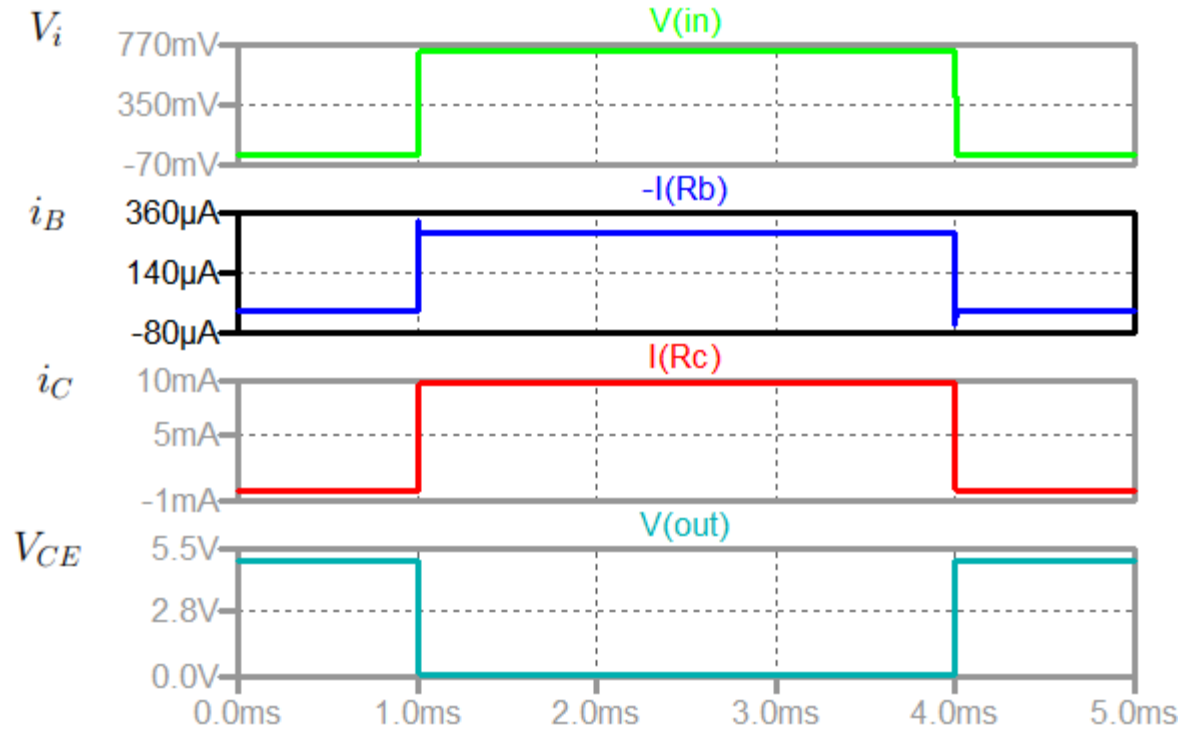

Basic level of first part of laboratory work is to simulate the typical inverter circuit using a bipolar transistor.

You should make an inverter circuit in LTspice:

- Choose transistor model;
- Make calculations parameters of resistors (without neglecting small value of  $V_{CE_{sat}} = 0.2 \dots 0.3 \text{ V}$ );
- Make simulations of inverter circuit.

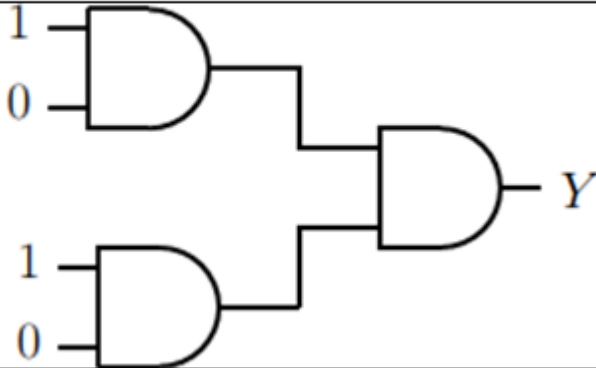

## 2. Combinational Logic Circuits

Choose your circuit variant from Table 2.


You should build circuit diagram in LtSpice and make simulations.

In the report you should draw your circuit, truth table, Boolean function and simulation results from LtSpice.


First step – you find your logic scheme from laboratory work assignment and write true table.

No	Circuit	N
1		1
2		1

No	A	B	C	D	Y
1	1	1	1	1	
2	0	1	1	1	
3	1	0	1	1	
4	0	0	1	1	
5	1	1	0	1	
6	0	1	0	1	
7	1	0	0	1	
8	0	0	0	1	
9	1	1	1	0	
10	0	1	1	0	
11	1	0	1	0	
12	0	0	1	0	
13	1	1	0	0	
14	0	1	0	0	
15	1	0	0	0	
16	0	0	0	0	

 


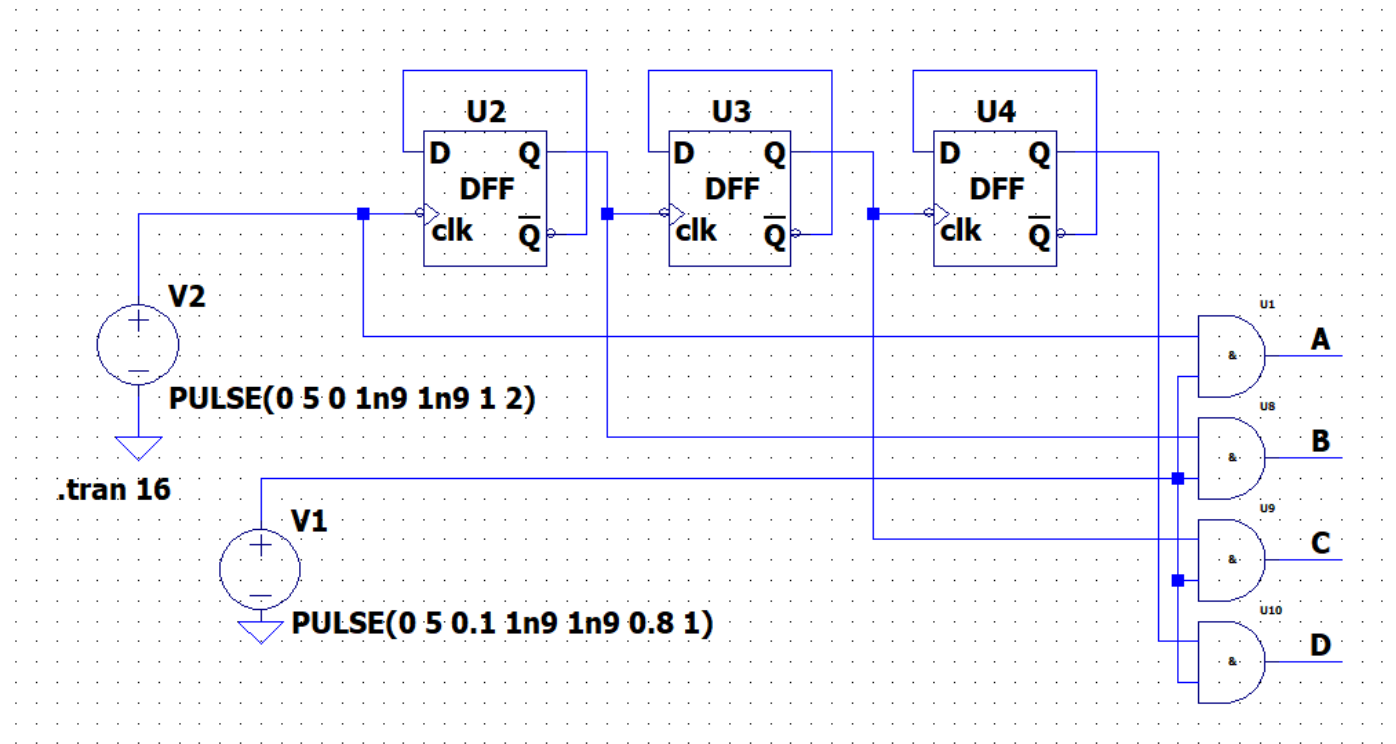Input signals you can generate by using voltage source or by using our generator.





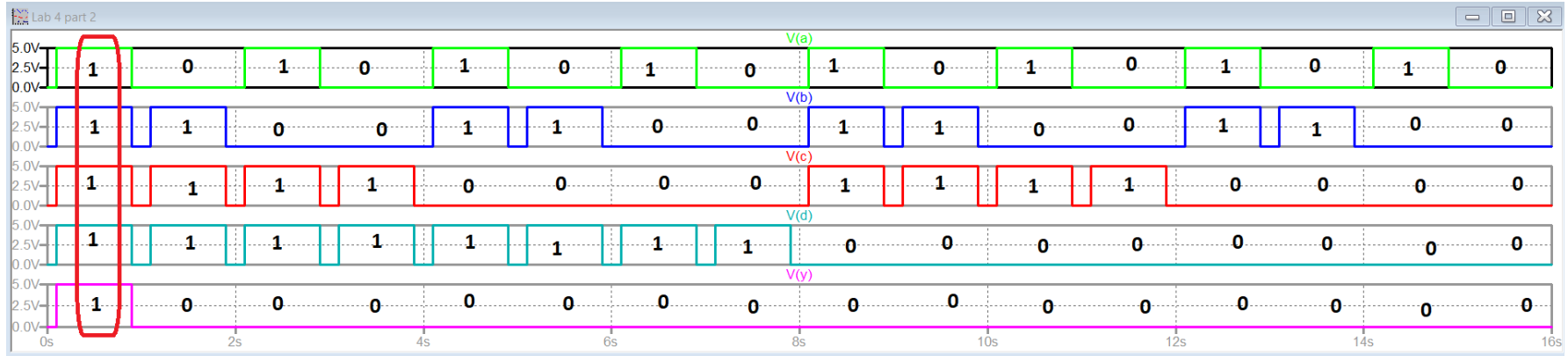
Third step – You should make simulation of your scheme.



Final step – You should make the laboratory report.
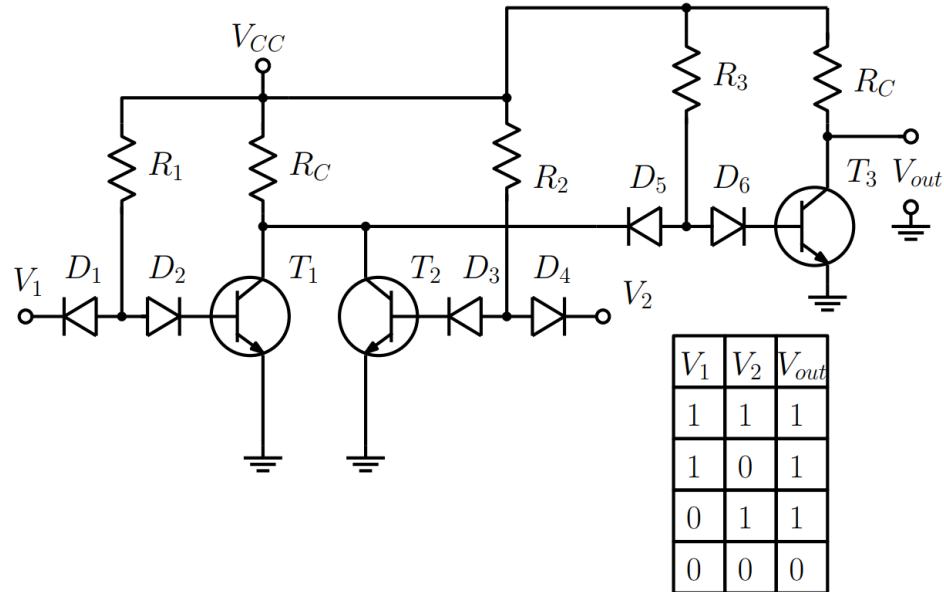
## 3 Logic families

In this part we consider the simplest schematic decisions for logic families. For example, we consider the most complicated example of DTL family.



First of all we suppose that we have power supply  $V_{CC} = 10\text{ V}$  and we need to have  $I_C = 10\text{ mA}$ .

We will use npn transistor 2N2222.

We need to find the datasheet for transistor and find common-emitter current gain.

## 2N2222 / 2N2222A

### NPN Silicon Epitaxial Planar Transistor

for switching and AF amplifier applications.

The transistor is subdivided into one group according to its DC current gain.

On special request, these transistors can be manufactured in different pin configurations.

## 2N2222 / 2N2222A

### Characteristics at $T_a = 25\text{ °C}$

Parameter	Symbol	Min.	Max.	Unit
DC Current Gain				
at $V_{CE} = 10\text{ V}$ , $I_C = 0.1\text{ mA}$	$h_{FE}$	35	-	-
at $V_{CE} = 10\text{ V}$ , $I_C = 1\text{ mA}$	$h_{FE}$	50	-	-
at $V_{CE} = 10\text{ V}$ , $I_C = 10\text{ mA}$	$h_{FE}$	75	-	-
at $V_{CE} = 10\text{ V}$ , $I_C = 150\text{ mA}$	$h_{FE}$	100	300	-
at $V_{CE} = 10\text{ V}$ , $I_C = 500\text{ mA}$	$h_{FE}$	30	-	-
2N2222	$h_{FE}$	40	-	-
2N2222A	$h_{FE}$	40	-	-
Collector Base Cutoff Current				
at $V_{CB} = 50\text{ V}$	$I_{CBO}$	-	10	nA
at $V_{CB} = 60\text{ V}$	$I_{CBO}$	-	10	nA
2N2222	$I_{CBO}$	-	10	nA
2N2222A	$I_{CBO}$	-	10	nA
Collector Base Breakdown Voltage				

$$h_{FE} = 75$$

We can find resistance of collector resistor  $R_C$ .

$$R_C = \frac{V_{CC} - V_{CE_{sat}}}{I_C}$$

$V_{CC}$  - we know and  $V_{CE_{sat}} \approx 0.2 \text{ V}$ .


$$R_C = \frac{10 - 0.2}{10 \cdot 10^{-3}} = 980 \Omega$$

Now we can find the base current, we know that in active region

$$I_C = h_{FE} I_B$$

or for  $I_B$  we have

$$I_B = \frac{I_C}{h_{FE}}$$

 

We have  $h_{FE}$  and  $I_C$

$$I_B = \frac{10 \cdot 10^{-3}}{75} = 0,13 \text{ mA}$$


This is minimal value of base current. We should choose  $I_{B_{sat}} = (2 \dots 5)I_B$ .

We choose  $I_{B_{sat}} = 0.5 \text{ mA}$ .

Now we can find resistance of base resistor

$$R_B = \frac{V_{CC} - V_{VD} - V_{BE}}{I_{B_{sat}}}$$

 where we can use  $V_{VD} \approx 0.6 \text{ V}$  and  $V_{BE} \approx 0.6 \text{ V}$




Now we have


$$R_B = \frac{10 - 0.7 - 0.7}{10 \cdot 10^{-3}} = 17.6 \text{ k}\Omega$$

As a diode we chose commonly used diode 1N4007.

 
We chose all parameters of three transistor switches are equal.



Now we can make scheme in LtSpice


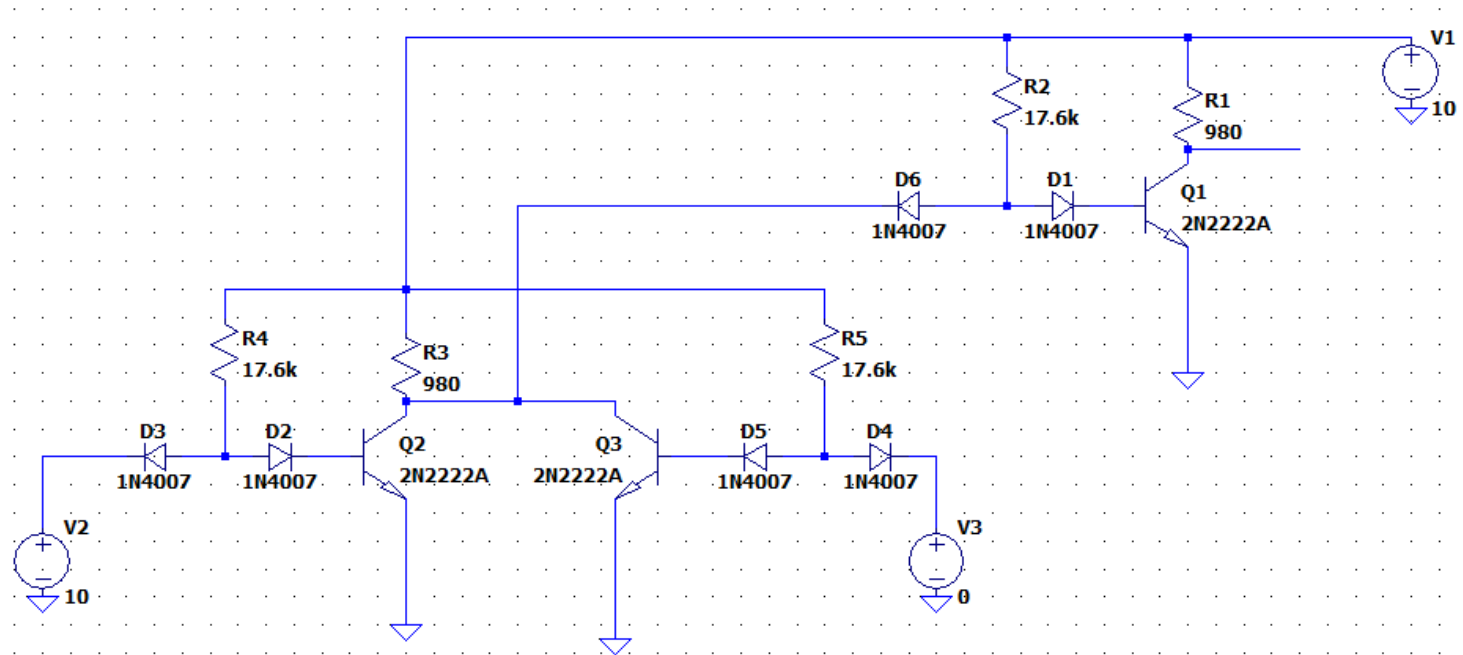


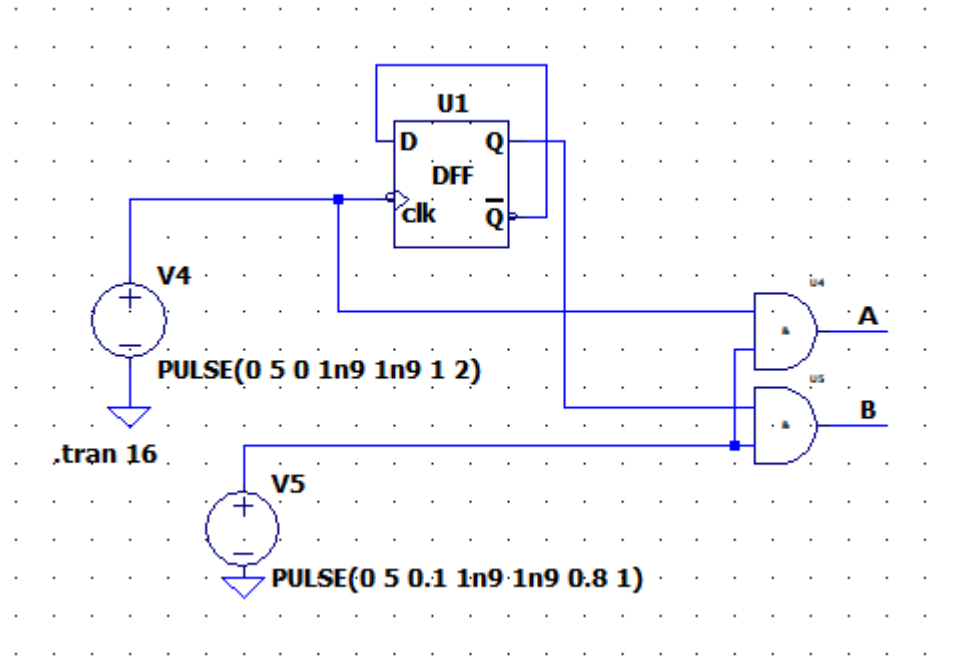You can simulate input signals by voltage sources or use our simple generator.





## Simulation results

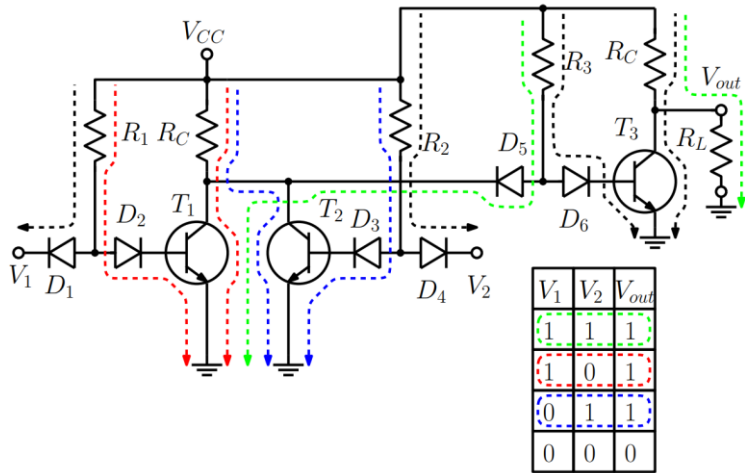 

Final step – You should prepare the laboratory report.

The background features a dark gray grid pattern. In the top right and bottom left corners, there are decorative wavy lines in a bright purple color, creating a modern, abstract aesthetic.

**iTMO**

**Thank you for your attention!**