



iTMO

Filter theory

Nikolay Nikolaev

(nanikolaev@itmo.ru)

Nikolai Poliakov

(polyakov_n_a@itmo.ru)



frequency responses

magnitude $G(\omega) = |H(j\omega)| = \left| \frac{V_2(j\omega)}{E(j\omega)} \right|$

phase $\phi(\omega) = \text{argument}(H(j\omega))$

logarithmic gain


$$G_{dB}(\omega) = 20 \log(G(\omega)) = 20 \log\left(\frac{|V_2(j\omega)|}{|E(j\omega)|}\right) \text{ (dB)}$$

attenuation

$$A(\omega) = 20 \log\left(\frac{|E(j\omega)|}{|V_2(j\omega)|}\right) = 20 \log\left(\frac{1}{G(\omega)}\right) = -G_{dB}(\omega) \text{ (dB)}$$


Ideal Transmission

$$G(\omega) = |H(j\omega)| = A$$

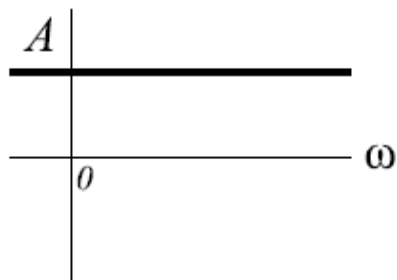


$$G(\omega) = |H(j\omega)| = A$$

$$\varphi(\omega) = -\omega t_0$$

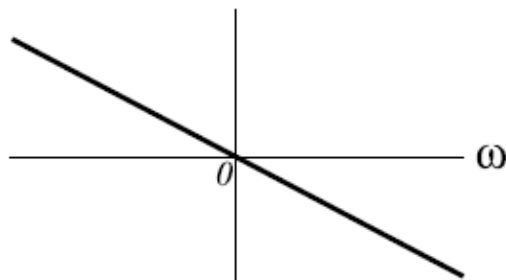

$$\varphi(\omega) = t_0 \omega$$

$$D(\omega)$$

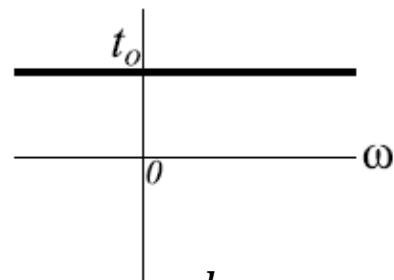

$$D(\omega) = -\frac{d}{d\omega} \phi(\omega) = t_0$$


Real Transmission

$$G(\omega) = |H(j\omega)| = f_1(\omega) \neq \text{const} \quad \varphi(\omega) = f_2(\omega) \neq t_0 \omega$$


$$D(\omega) = -\frac{d}{d\omega} \phi(\omega) \neq t_0$$

ideal lowpass filter transfer function


$$H(j\omega) = \begin{cases} e^{-j\omega t_0} & \text{for } |\omega| \leq \omega_c \\ 0 & \text{for } |\omega| \geq \omega_c \end{cases}$$

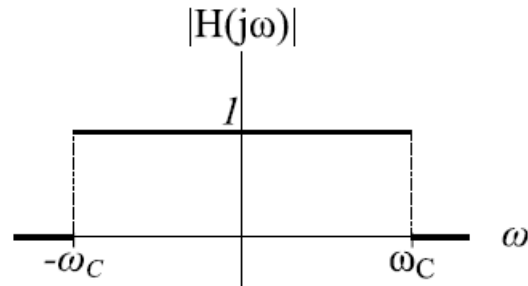


$$|H(j\omega)| = \begin{cases} 1 & \text{for } |\omega| \leq \omega_c \\ 0 & \text{for } |\omega| \geq \omega_c \end{cases}$$

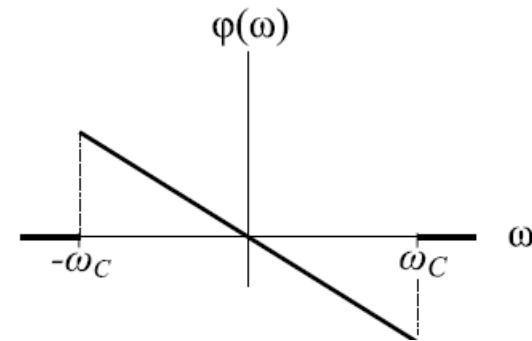


$$\varphi(\omega) = t_0 \omega$$



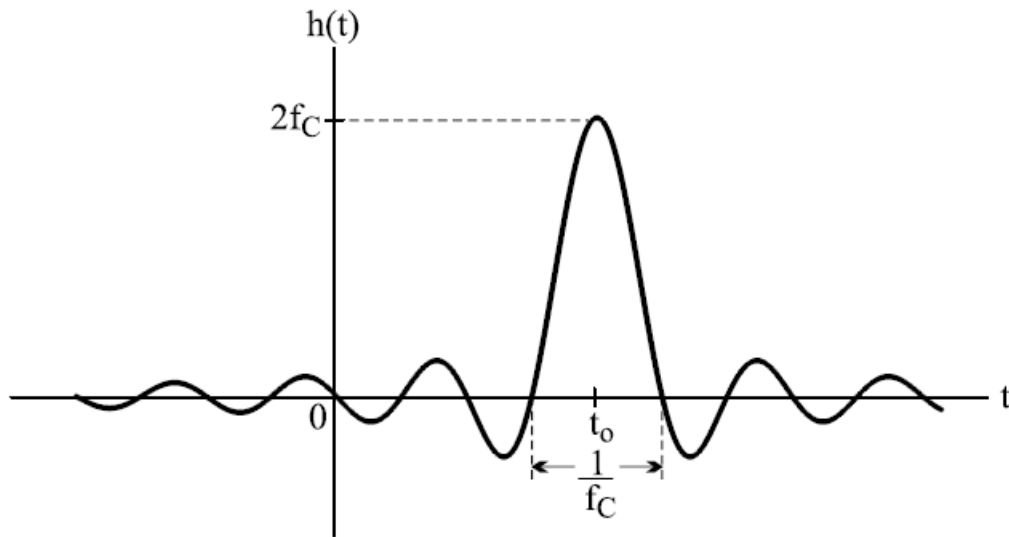


$$\begin{aligned} h(t) &= \frac{1}{2\pi} \int_{-\infty}^{\infty} H(j\omega) e^{j\omega t} d\omega = \\ &= \frac{1}{2\pi} \int_{-\infty}^{\infty} |H(j\omega)| e^{-j\omega t_0} e^{j\omega t} d\omega = \\ &= \frac{1}{2\pi} \int_{-\infty}^{\infty} e^{j\omega(t-t_0)} d\omega = \\ &= \frac{\omega_C}{2\pi} \frac{\sin(\omega_C(t-t_0))}{\omega_C(t-t_0)} \end{aligned}$$

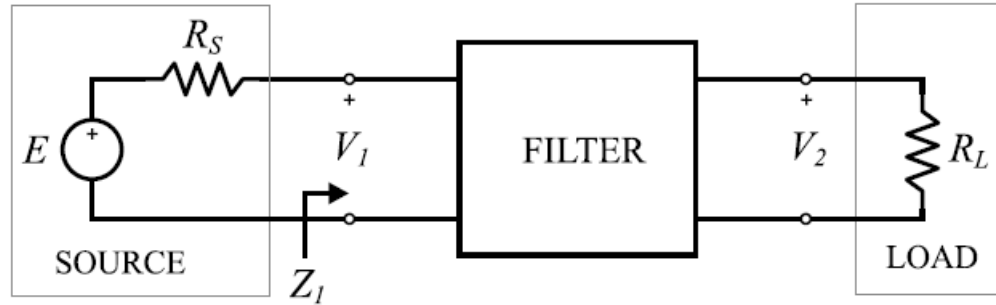

$$\begin{aligned} h(t) &= \frac{1}{2\pi} \int_{-\infty}^{\infty} H(j\omega) e^{j\omega t} d\omega = \frac{1}{2\pi} \int_{-\infty}^{\infty} |H(j\omega)| e^{-j\omega t_0} e^{j\omega t} d\omega = \\ &= \frac{1}{2\pi} \int_{-\infty}^{\infty} e^{j\omega(t-t_0)} d\omega = \frac{\omega_c}{2\pi} \frac{\sin(\omega_c(t-t_0))}{\omega_c(t-t_0)} \end{aligned}$$

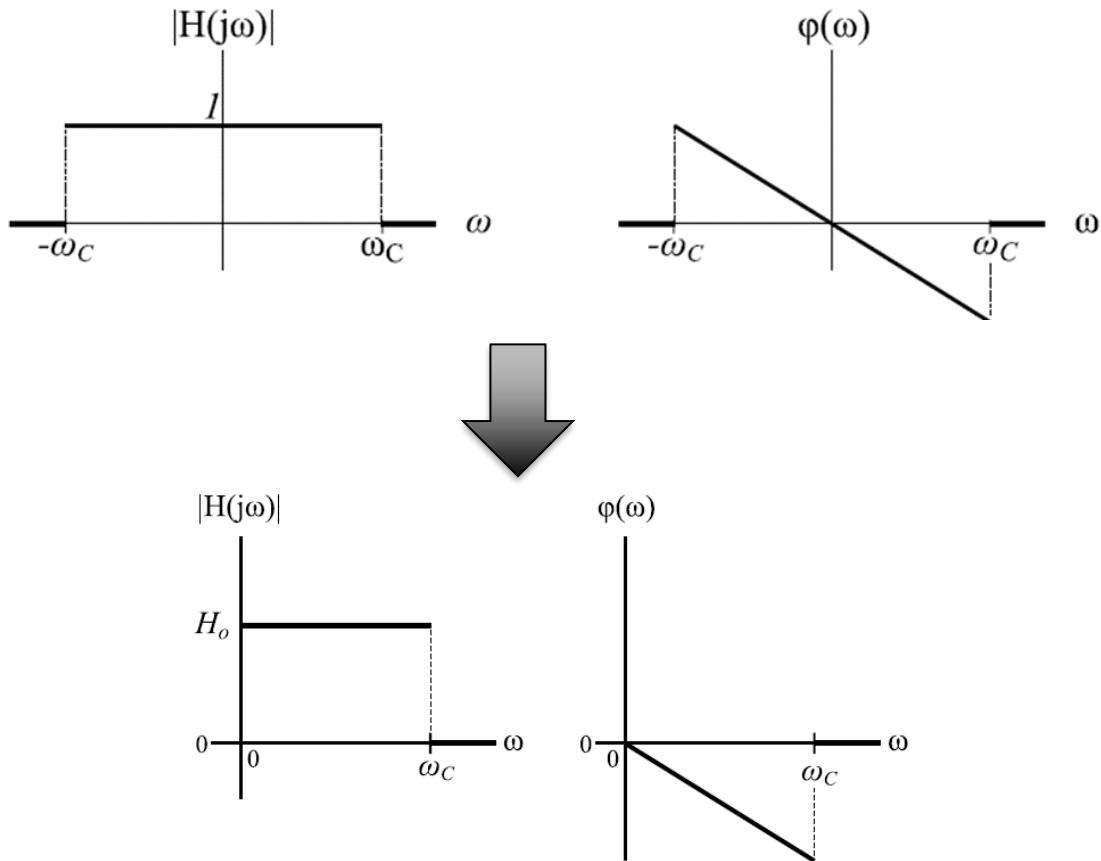

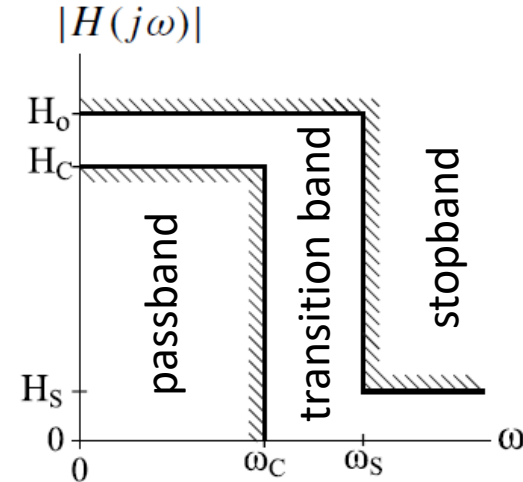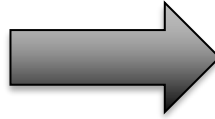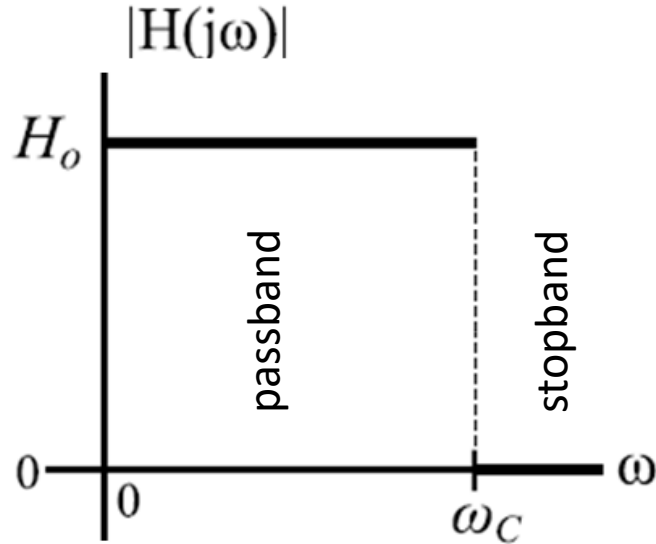

H_C - minimum allowed gain in the passband





ω_C - cut-off frequency

H_S - maximum allowed value of the gain in the stopband

ω_S - stopband edge frequency

The five quantities H_o , H_C , H_S , ω_C and ω_S constitute the magnitude specifications of the realizable lowpass filter and are dictated by the requirements of the system

Realizable Lowpass Filters

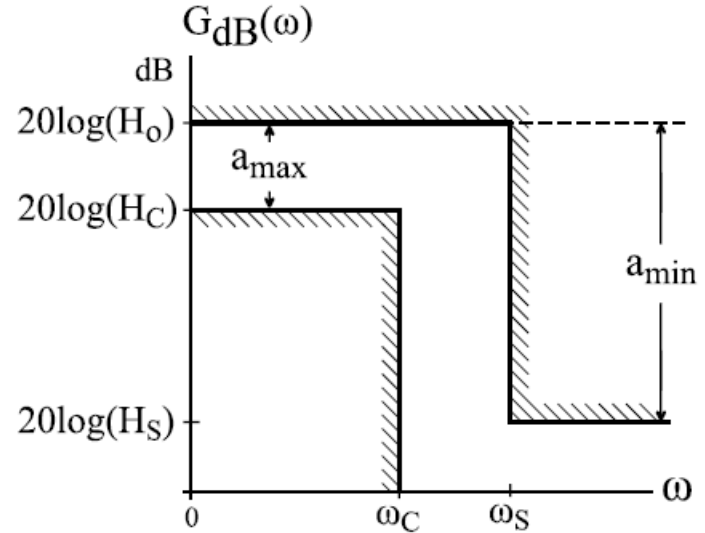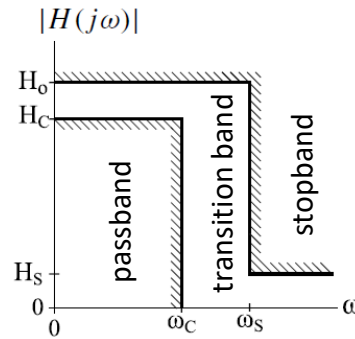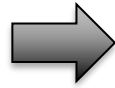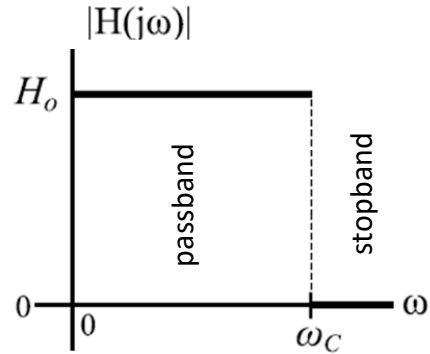




$$G_0 = 20\log(H_0) \quad H_0 = 10^{\frac{G_0}{20}}$$




$$G_C = 20\log(H_C) \quad H_C = 10^{\frac{G_C}{20}}$$

$$G_S = 20\log(H_S) \quad H_S = 10^{\frac{G_S}{20}}$$

$$\alpha_{max} = 20\log\left(\frac{H_0}{H_C}\right) \quad \frac{H_0}{H_C} = 10^{\frac{\alpha_{max}}{20}}$$

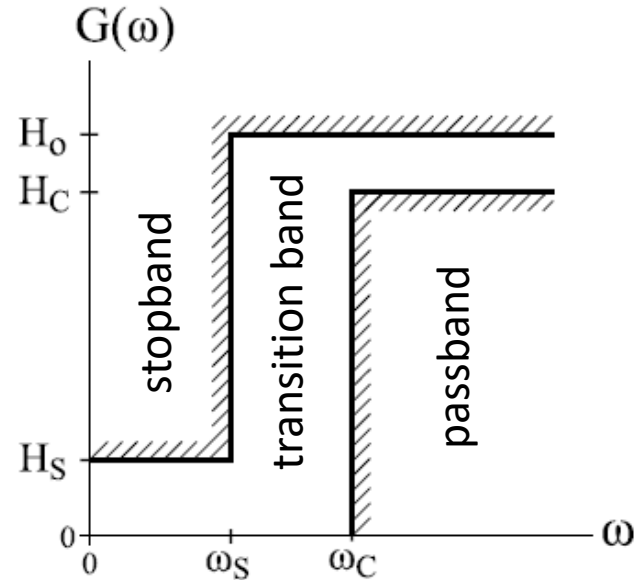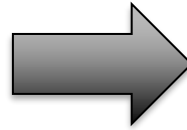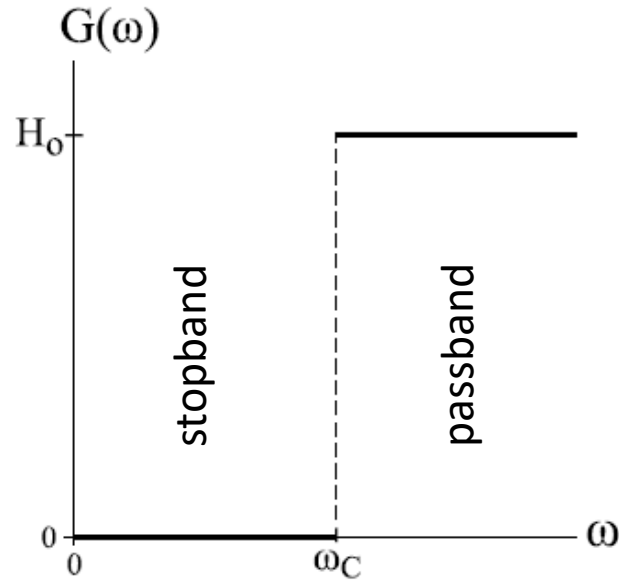
$$\alpha_{min} = 20\log\left(\frac{H_0}{H_S}\right) \quad \frac{H_0}{H_S} = 10^{\frac{\alpha_{min}}{20}}$$



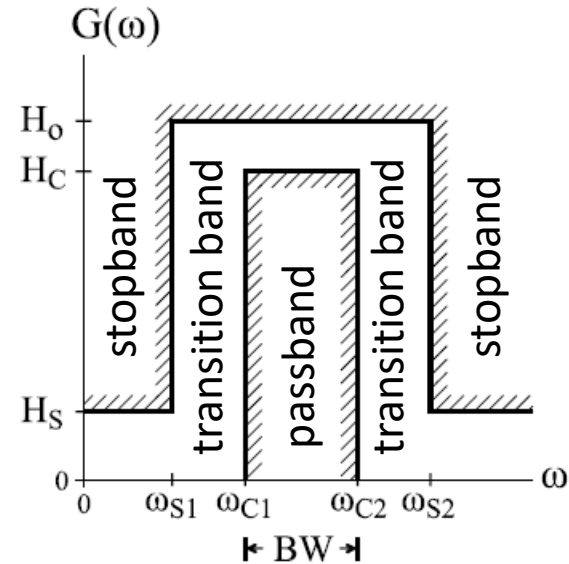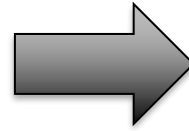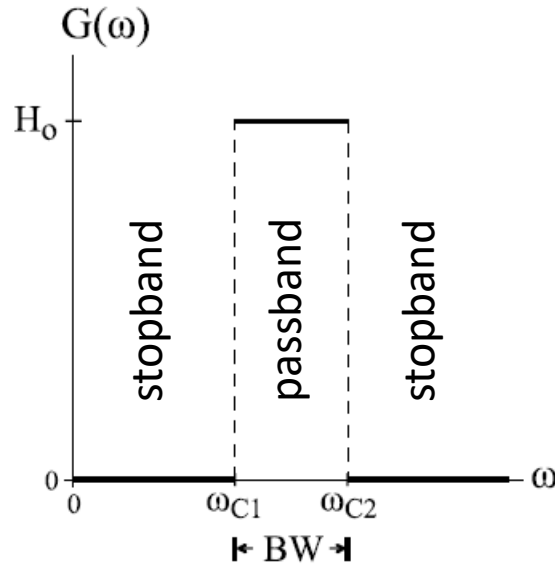

$$\text{Bandwidth } BW = \Delta f = \omega_{C2} - \omega_{C1}$$

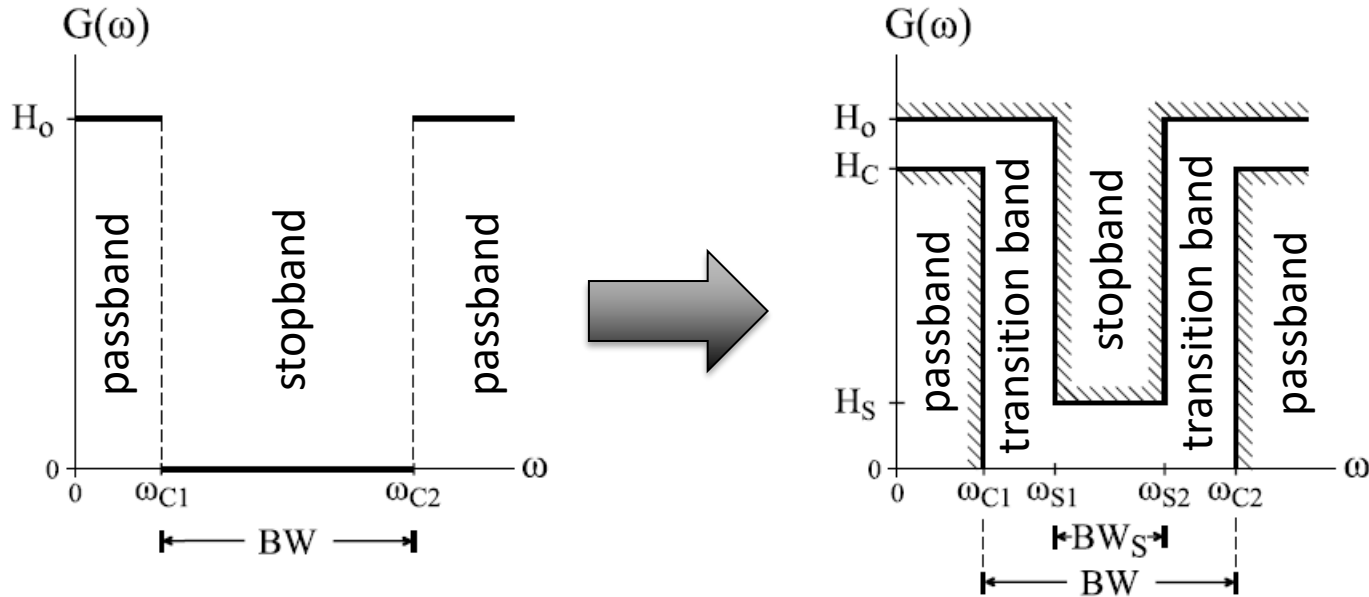
$$\text{center frequency } \omega_0 = \sqrt{\omega_{C2} * \omega_{C1}}$$




$$\text{BandWidth } BW = \omega_{C2} - \omega_{C1}$$

$$\text{Stopband BandWidth } BWS = \omega_{S2} - \omega_{S1}$$
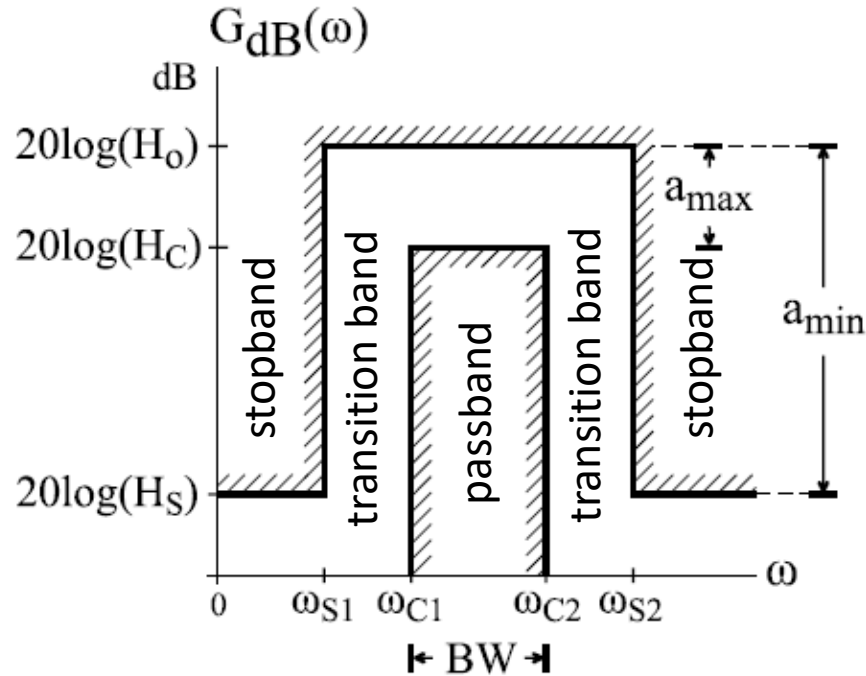
$$\text{Center Frequency } \omega_0 = \sqrt{\omega_{S2} * \omega_{S1}}$$



Bandpass filter

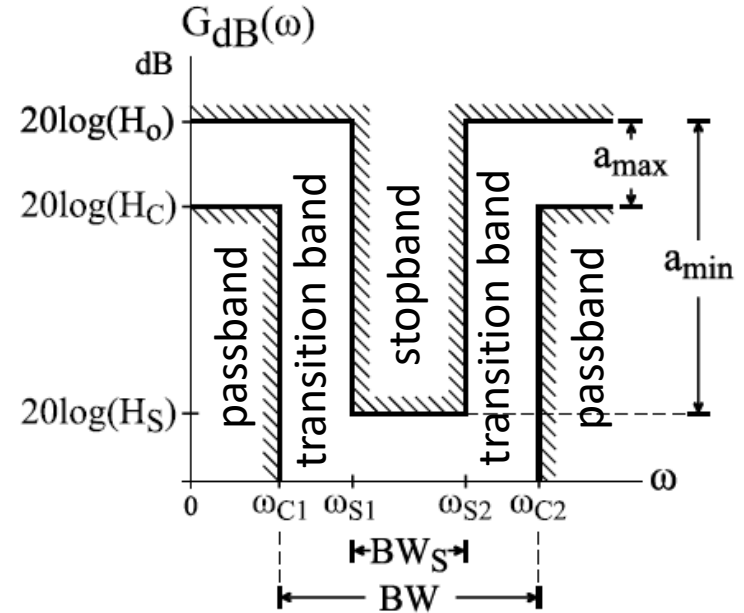

Band-reject filter

Classification filter by input signal, their internal signals and the output signals

i. Continuous-time (CT)

$f(t)$ at any t

ii. Sampled-data

$$f_s(t) = \sum_{n=-\infty}^{+\infty} f(nT) * \delta(t - nT)$$

$f(t)$ - continuous time signal

T - sampling period

$$f_s(t) = 0 \text{ for } nT \leq t < (n+1)T$$

iii. Discrete-time

$$f(nT) \\ \text{For } -\infty < n_1 \leq n \leq n_2 < +\infty$$

$$\text{And } f(nT) = 0 \\ \text{if } nT \leq t < (n+1)T$$

Classification filter by input signal, their internal signals and the output signals

i. Continuous-time (CT)

$f(t)$ at any t

ii. Sampled-data

$$f_s(t) = \sum_{n=-\infty}^{+\infty} f(nT) * \delta(t - nT)$$

$f(t)$ - continuous time signal

T - sampling period

$$f_s(t) = 0 \text{ for } nT \leq t < (n + 1)T$$


iii. Discrete-time


$$f(nT) \\ \text{For } -\infty < n_1 \leq n \leq n_2 < +\infty$$

$$\text{And } f(nT) = 0 \\ \text{if } nT \leq t < (n + 1)T$$


General classification of analogue electronic filters:

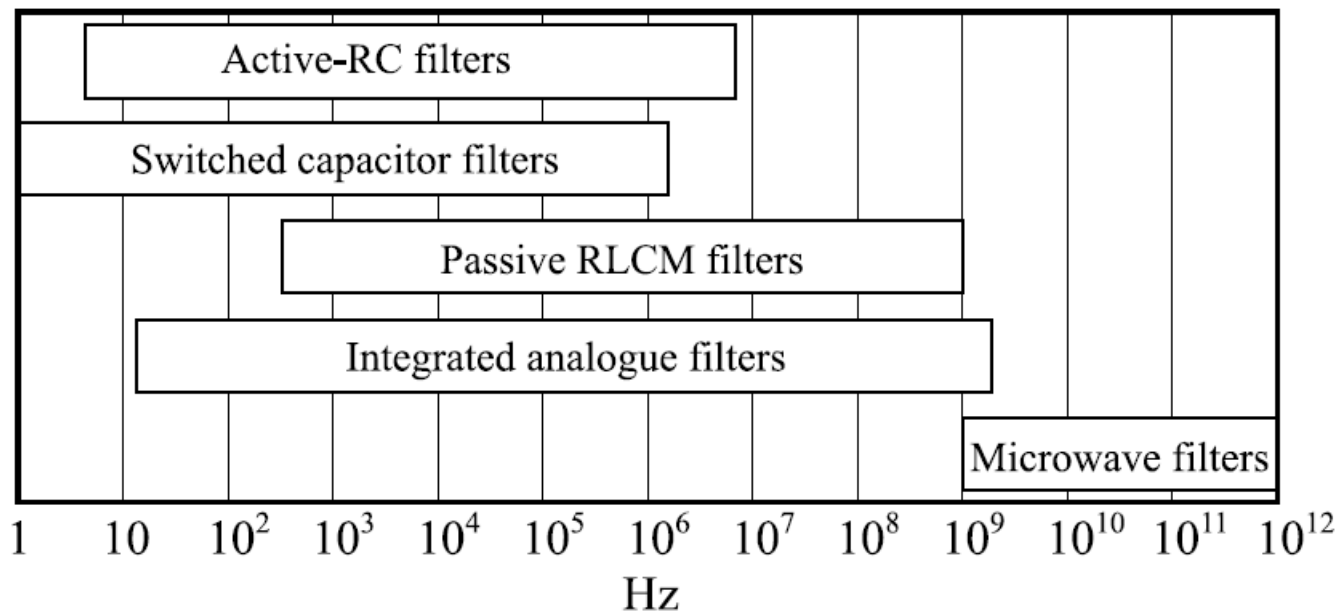1. Passive RLCM filters
2. Active-RC filters
3. Integrated MOS-C filters
4. Integrated OTA-C or $g_m - C$ filters
5. Current-mode integrated filters.
6. Active switched capacitor filters designed for discrete-time signals
7. Microwave filters with distributed parameters (waveguides) and microwave filters based on microwave resonators and cavities.
8. Crystal filters
9. Mechanical and electromechanical filters




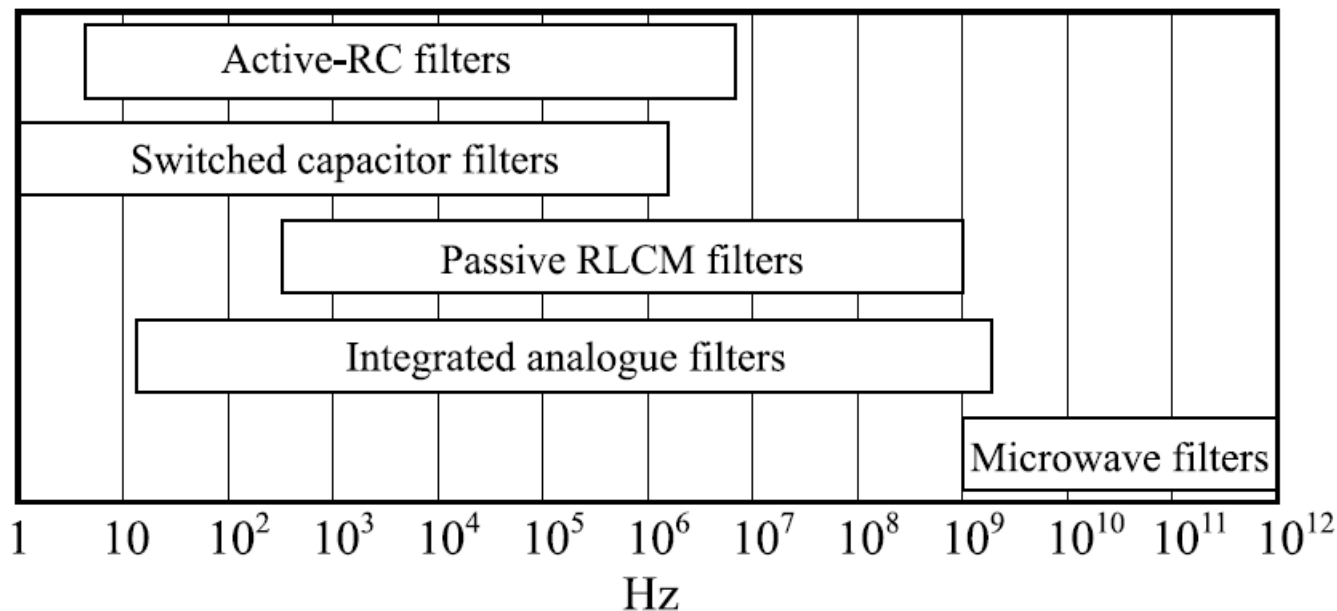

Lattice structure

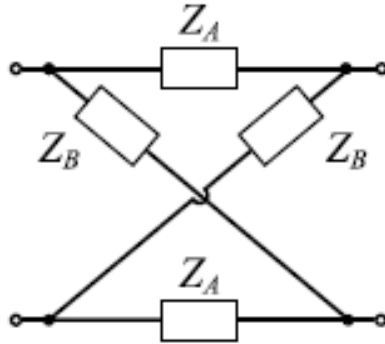


Ladder structure

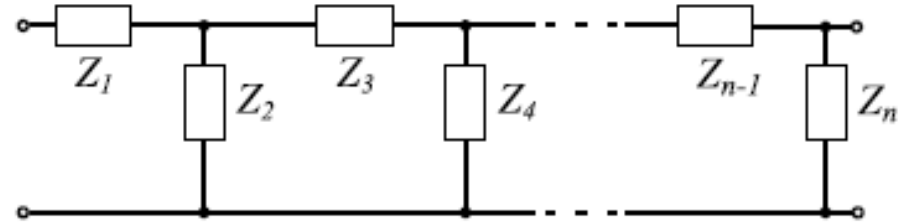

Benefits LC circuits

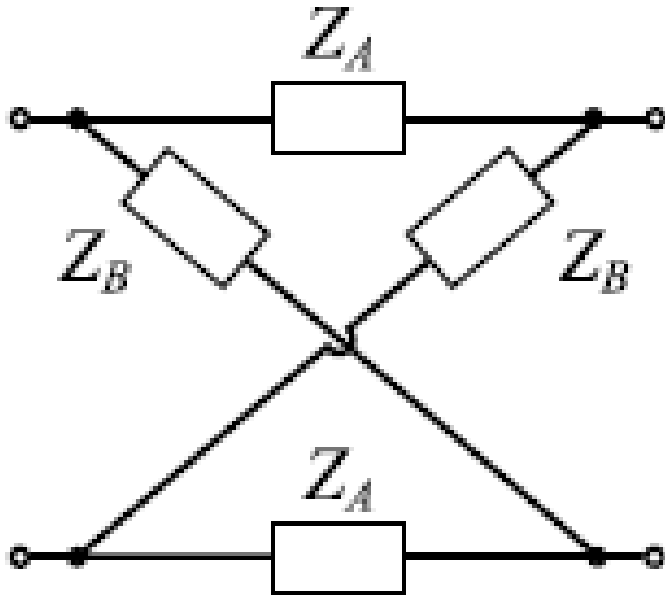- (a) can satisfy any practical filter specifications
- (b) need a minimum number of components
- (c) can be designed so that they can maximize the power transferred from source to load in some frequencies in their passband.




disadvantages when compared to the ladder topology:

1. for a given set of requirements, it needs more lossless elements than the corresponding ladder
2. it presents high sensitivity to component changes

To realize a transmission zero in passband, a bridge equilibrium is required:


$$|Z_A(j\omega)| = |Z_B(j\omega)|$$

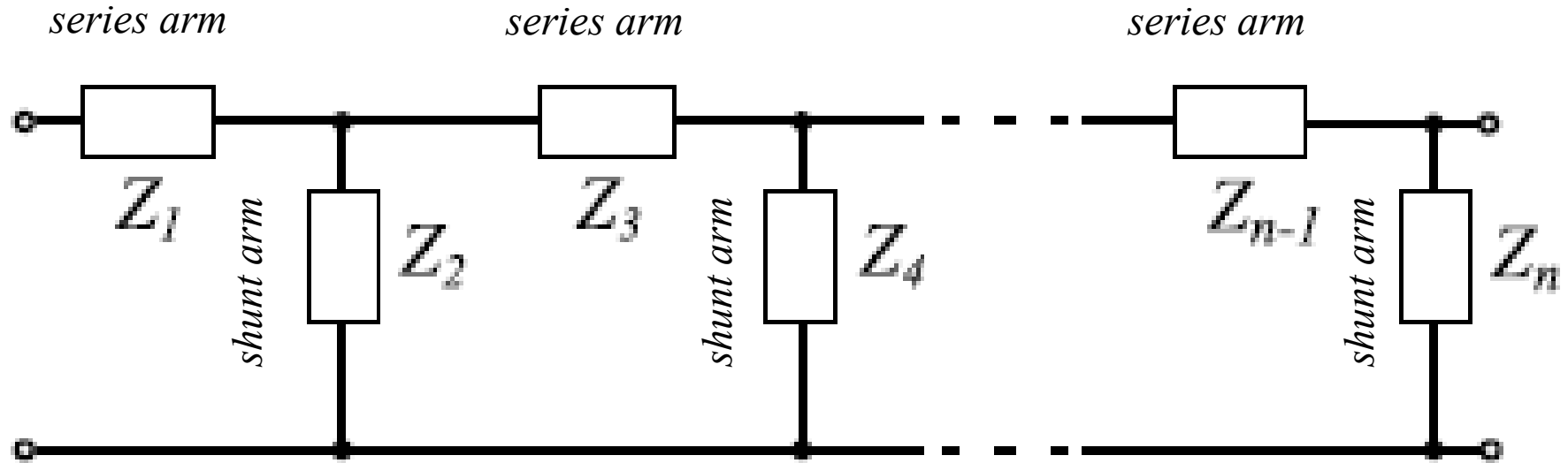

We need lowpass filter with the following specifications

(a) For $0 \leq f \leq 1 \text{ kHz}$ the gain is $G(f) = 4$

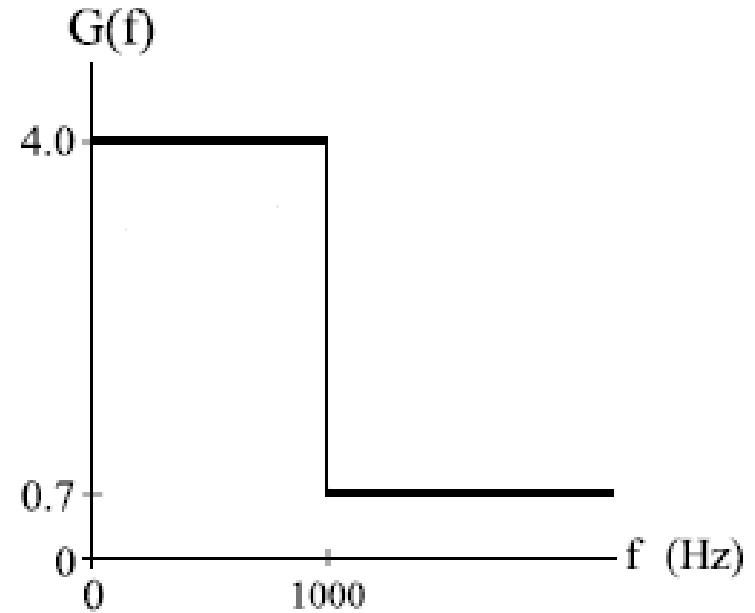
(b) For $f > 1 \text{ kHz}$ the gain is $G(f) = 0.7$



Designing a Filter. Example

For the filter to be realizable, some tolerance should be given:

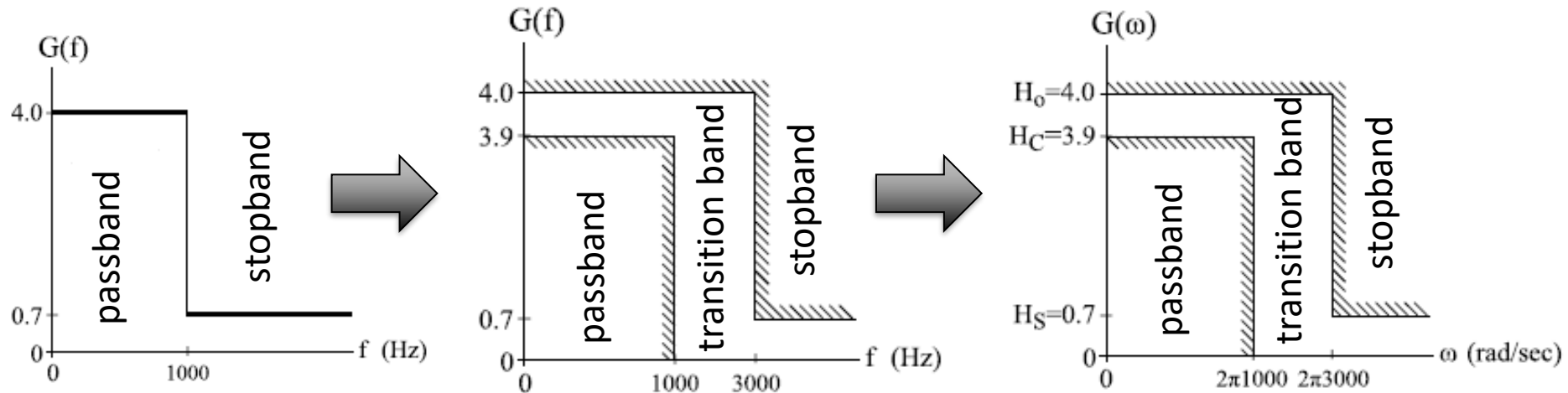- (a) For $0 \leq f \leq 1 \text{ kHz}$ the gain may vary $3.9 \leq G(f) \leq 4$
- (b) For $1 \text{ kHz} \leq f \leq 3 \text{ kHz}$ the gain must be $G(f) \leq 3.9$
- (c) For $f > 3 \text{ kHz}$ the gain must be $G(f) \leq 0.7$



let ω_0 be characteristic frequency at ω_0 , wish to move it to another frequency ω_X

$$\omega_0 \Rightarrow \omega_X$$

So *scale* the frequency by $\gamma = \frac{\omega_0}{\omega_X}$


functions will be frequency-scaled by the factor γ .

$$H(s) \Rightarrow H(\gamma s), G(\omega) \Rightarrow G(\gamma \omega)$$


When using $\omega_X = 1$, want the characteristic frequency to move from $\omega = \omega_0$ to $\omega = 1$
this particular frequency scaling is called *frequency normalization*.

The new scaled frequency $\frac{\omega}{\omega_0} = \Omega$ is the *normalized frequency*.

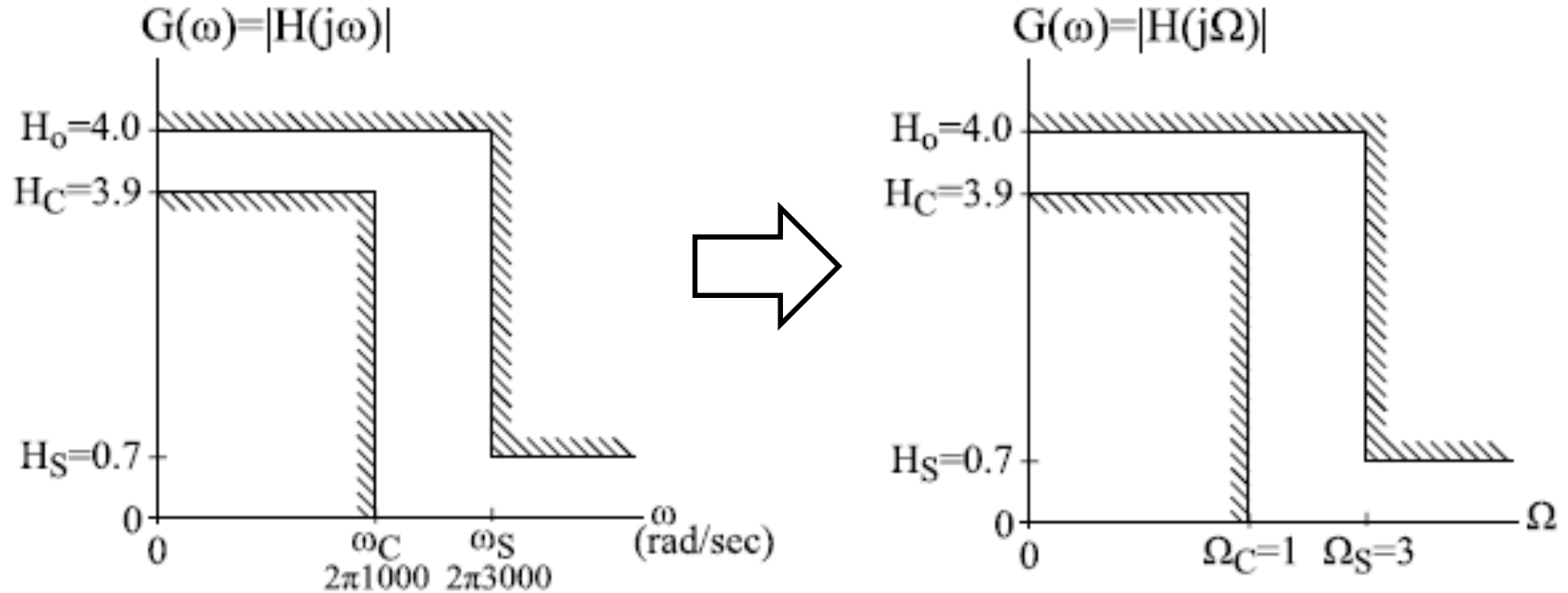A frequency-normalized filter is a filter which satisfies normalized specifications. It can be easily denormalized so that the cutoff frequency takes any desirable value, without affecting gain and attenuation characteristics.



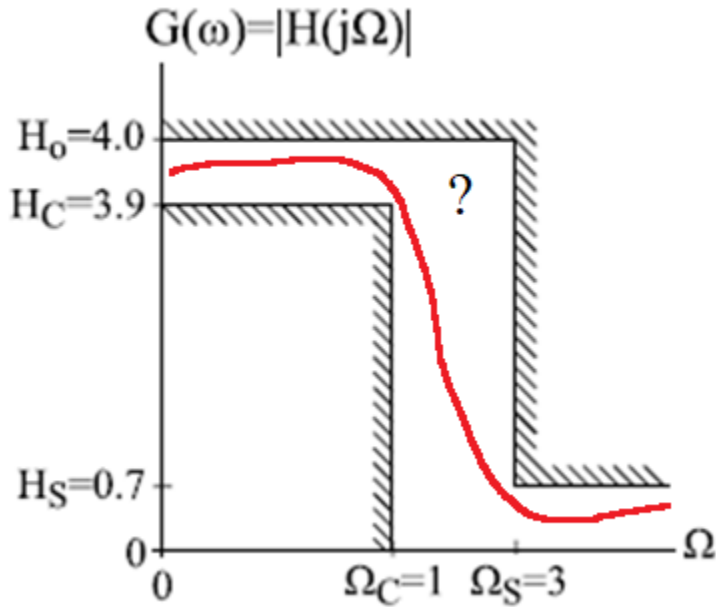A frequency-normalized filter is a filter which satisfies normalized specifications. It can be easily denormalized so that the cutoff frequency takes any desirable value, without affecting gain and attenuation characteristics.



approximation - finding the normalized gain function $G(\omega)$

and theoretically has an *infinite number of solutions*


To minimize the number of solutions, the function should satisfy some realizability conditions

- $G(\Omega)$ – even function of Ω
- $G^2(\Omega)$ – even rational function

Solution that satisfies the conditions in question







$$G(\Omega) = \frac{A}{\sqrt{1 + k^2 P^2(\Omega)}}$$

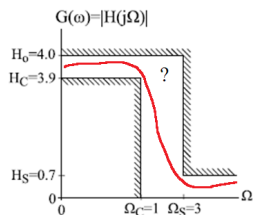
where k is a constant and $P(\Omega)$ is a polynomial or a rational function of Ω .



Approximation:

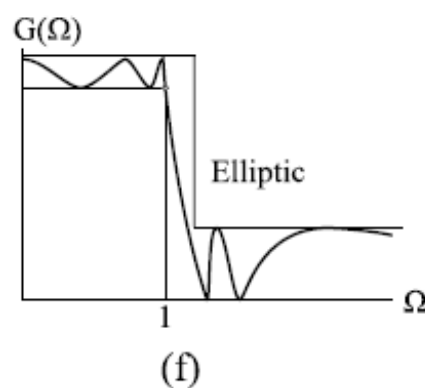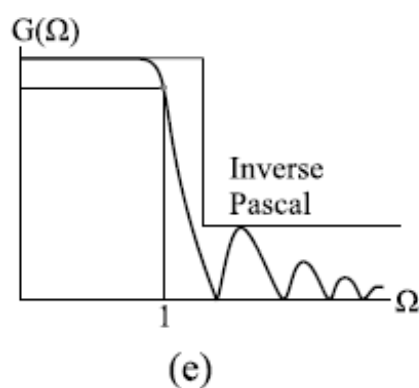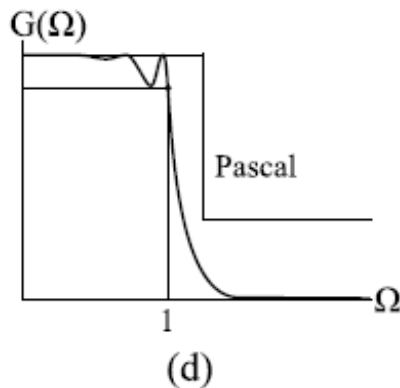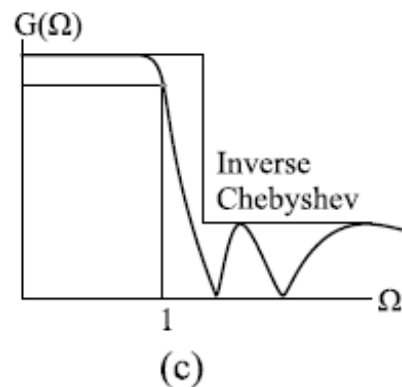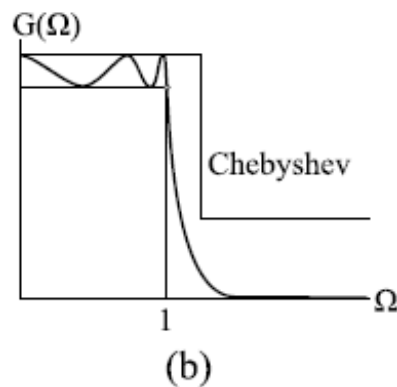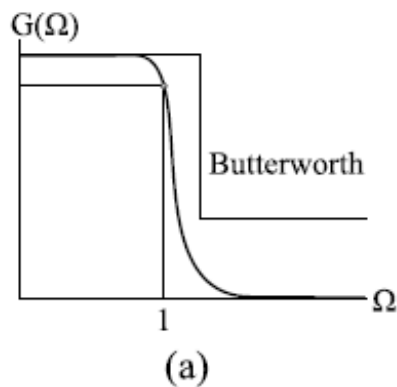
- ❖ Butterworth
- ❖ Chebyshev
- ❖ Inverse Chebyshev
- ❖ Bessel
- ❖ Pascal
- ❖ Inverse Pascal
- ❖ Elliptic
- ❖ And so on...



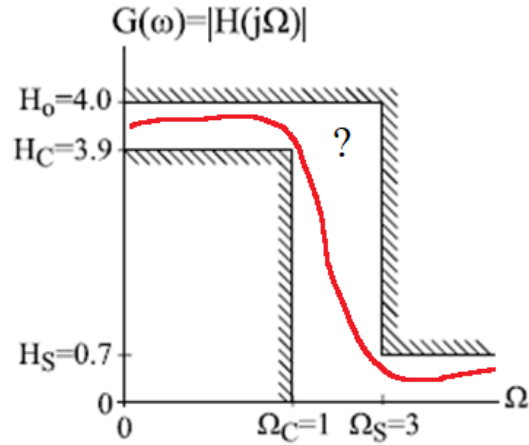

design procedure:


1. Frequency is scaled using ω_C so that the normalized cutoff frequency becomes 1 and the stopband edge frequency $\Omega_S = \frac{\omega_S}{\omega_C}$
2. Using one of the known approximations, the corresponding transfer function $H(s)$ is calculated, whose frequency response $|H(j\Omega)| = G(\Omega)$ satisfies the specifications.
3. The normalized filter circuit is synthesized from $H(s)$.
4. The filter is denormalized to the desired frequency and impedance level.

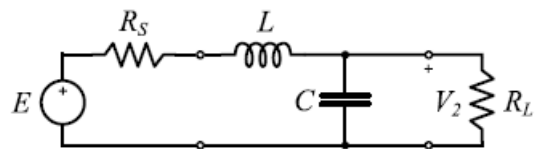

$$H(s) = \frac{1/LC}{s^2 + (\frac{R_S}{L} + \frac{1}{R_L C})s + \frac{1+R_S/R_L}{LC}}$$


$$Z(s) = \frac{s^2 + (\frac{R_S}{L} + \frac{1}{R_L C})s + \frac{1+R_S/R_L}{LC}}{s + \frac{1}{R_L C}} L$$

impedances divided
(scaled) by k

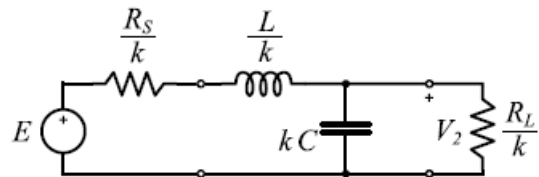


$$H(s) = \frac{1/LC}{s^2 + (\frac{R_S}{L} + \frac{1}{R_L C})s + \frac{1+R_S/R_L}{LC}}$$

$$Z_n(s) = \frac{Z(s)}{k}$$

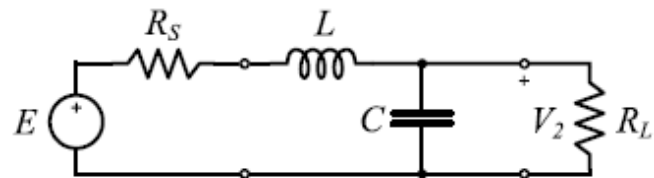

impedances divided
(scaled) by k

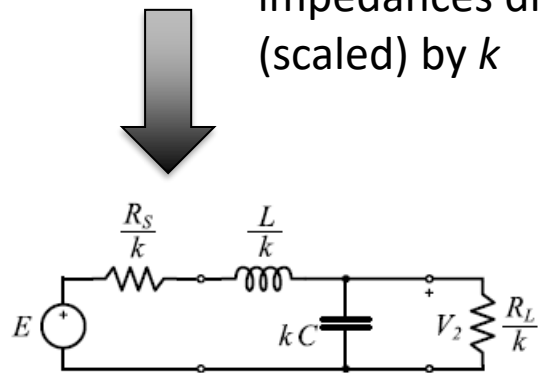

If $k = R_0$



the scaled resistors will be
dimensionless quantities

$$R_{Sn} = \frac{R_S}{R_0}$$

$$R_{Ln} = \frac{L}{R_0}$$



dimensionless

$$L_n = \frac{L}{R_0}$$

measured in seconds

$$\frac{1}{sC} = \frac{1}{sC} \frac{1}{R_0}$$


Frequency Scaling

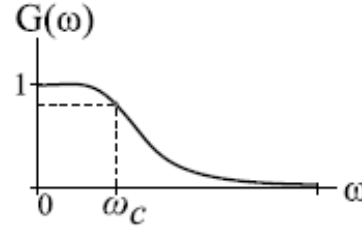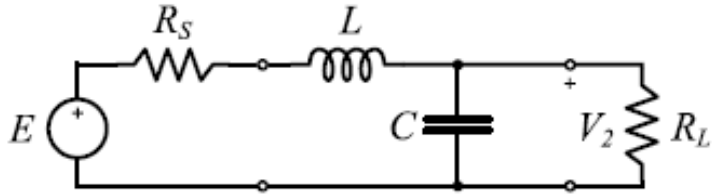

Defined

$$L = \omega_0 L,$$



$$C = \omega_0 C$$

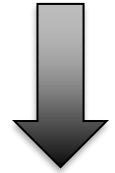


inductances and
capacitances are
multiplied by ω_0


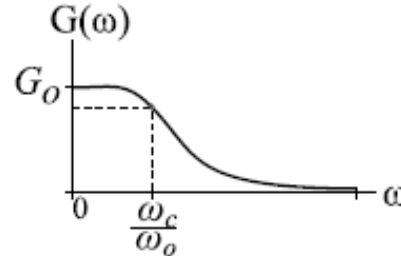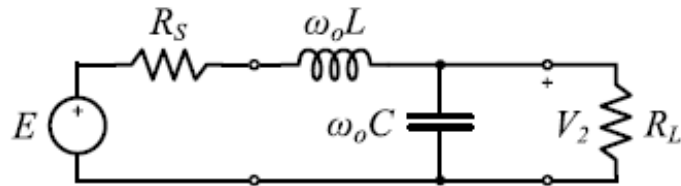
$$H_n(s) = \frac{1}{LC(\omega_0 s)^2 + (R_S C + \frac{L}{R_L})\omega_0 s + 1 + \frac{R_S}{R_L}} = H(\omega_0 s)$$



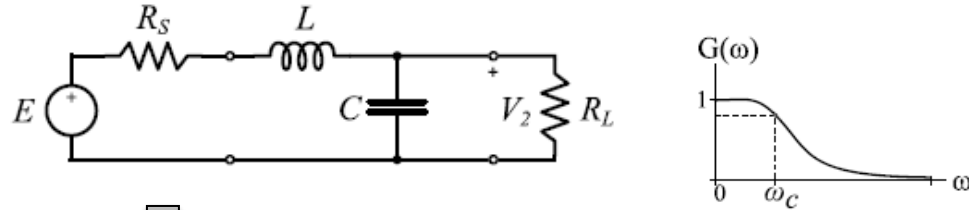
$$L, C \Rightarrow L_n = \omega_0 L, C_n = \omega_0 C,$$



Impedance
Frequency
Scaling

$$R_0 = R_L$$

$$\omega_0 = \omega_c$$

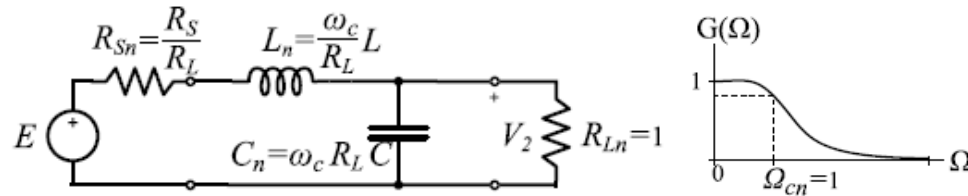

dimensionless normalized values

$$R_{Sn} = \frac{R_S}{R_L}, R_{Ln} = \frac{R_L}{R_L} = 1,$$




$$L_n = \frac{\omega_0}{R_L} L, C_n = \omega_c R_L C$$

normalized dimensionless angular
frequency, time and frequency

$$\Omega = \frac{\omega}{\omega_c}, t_n = \frac{\omega_c}{2\pi} t, F_n = \frac{2\pi}{\omega_c} f$$

Denormalized value

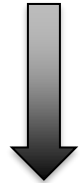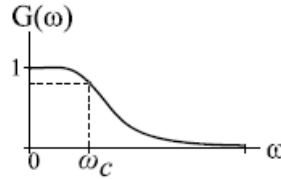
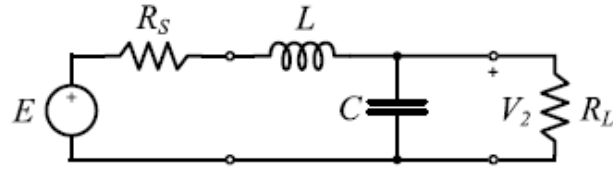
$$R_n = R_L R_{Sn}, L = \frac{R_L}{\omega_0} L_n, C = \frac{1}{\omega_c R_L} C_n$$



Impedance
Frequency
Scaling

$$R_0 = R_L$$

$$\omega_0 = \omega_C$$

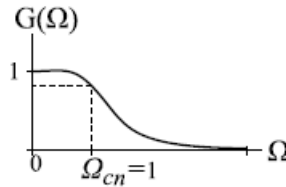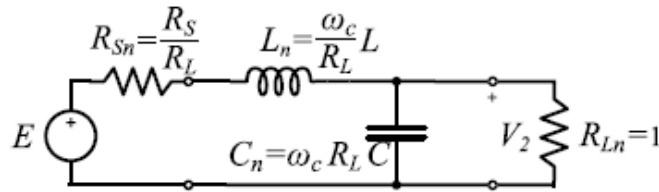

dimensionless normalized values

$$R_{Sn} = \frac{R_S}{R_L}, R_{Ln} = \frac{R_L}{R_L} = 1,$$


$$L_n = \frac{\omega_0}{R_L} L, C_n = \omega_C R_L C$$

normalized dimensionless angular
frequency, time and frequency


$$\Omega = \frac{\omega}{\omega_C}, t_n = \frac{\omega_C}{2\pi} t, F_n = \frac{2\pi}{\omega_C} f$$

Denormalized value
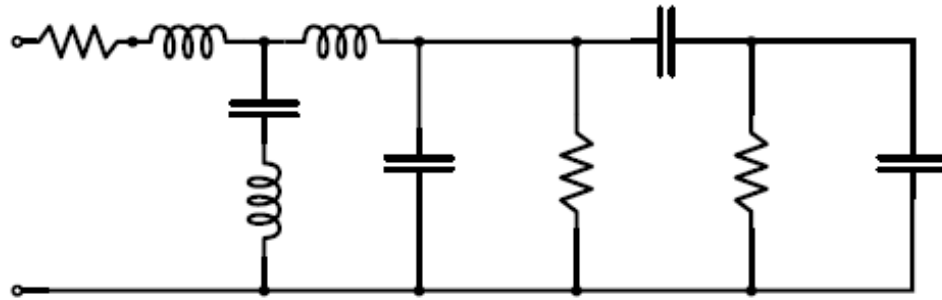
$$R_n = R_L R_{Sn}, L = \frac{R_L}{\omega_0} L_n, C = \frac{1}{\omega_C R_L} C_n$$



Rearranged

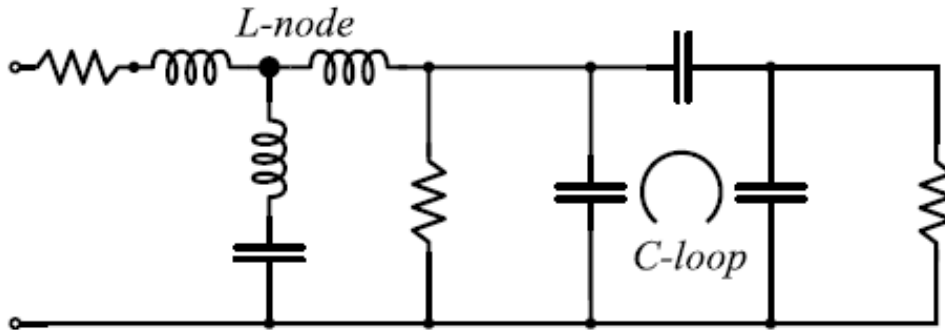


number of reactive elements: 7
inductors: 3
capacitors: 4
maximum order (as expected): 7

each L-node, C-node, L-loop or
C-loop reduces the Circuit order
by 1


number of reactive elements: 7
inductors: 3
capacitors: 4
L and C-node: 1
L and C-loop: 1
maximum order: 5

All functions of the circuit will have a polynomial of maximum degree 5.

Circuit Order. Example

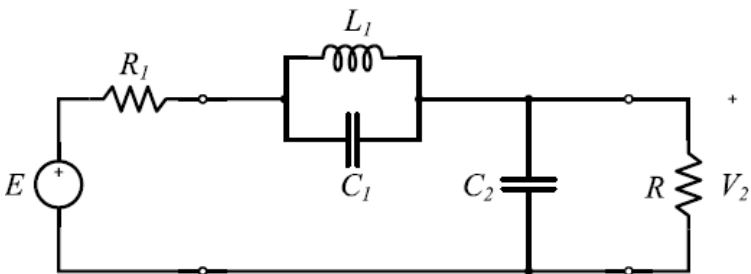

Removing resistor R1

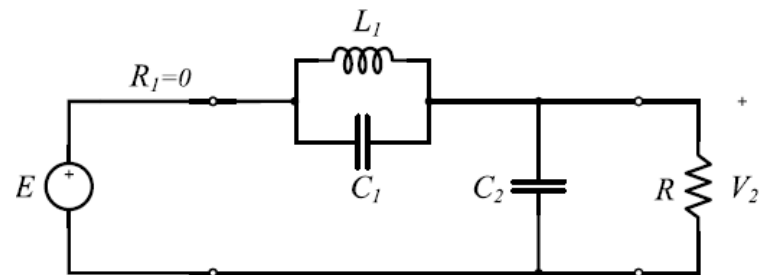

number of reactive elements: 3
Inductors and capacitors : 1+2
maximum order (as expected): 3

$$H(s) = \frac{L_1 C_1 s^2 + 1}{L_1 C_1 C_2 R_1 s^3 + [L_1 C_1 + L_1 C_1 (1 + \frac{R_1}{R})] s^2 + (R_1 C_2 + \frac{L_1}{R}) s + 1 + \frac{R_1}{R}}$$




$$R_1 = 0$$


$$H(s) = \frac{L_1 C_1 s^2 + 1}{s^2 + L_1 (C_1 + C_2) s + \frac{L_1}{R} + 1}$$

number of reactive elements: 3
Inductors and capacitors : 1+2
node and loop: 1
maximum order: 2

not canonic circuits

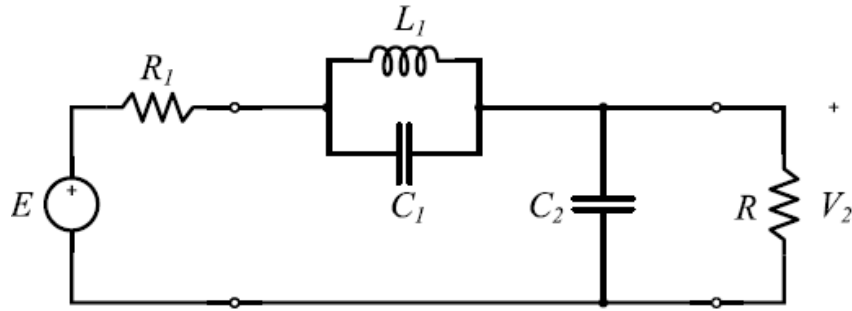

Canonic circuits

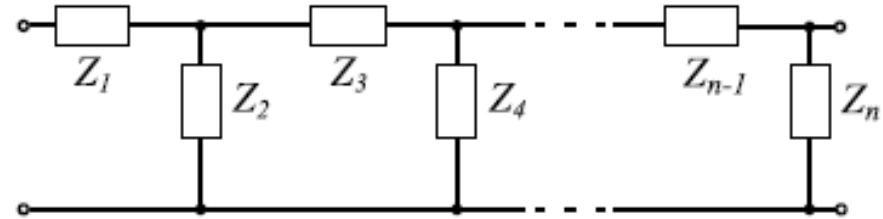


do not have L-nodes, C-nodes, L-loops or C-loops


The background features a dark gray grid pattern. In the top right and bottom left corners, there are decorative wavy lines in a bright purple color, creating a modern, abstract aesthetic.

iTMO


All-Pole Approximations

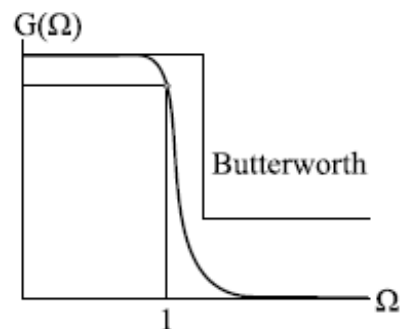


(a)

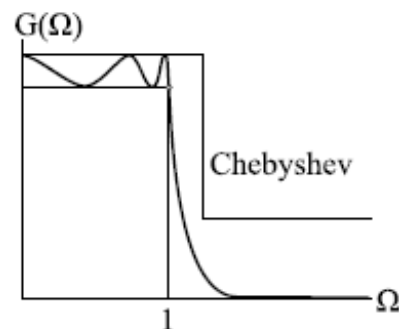


(b)

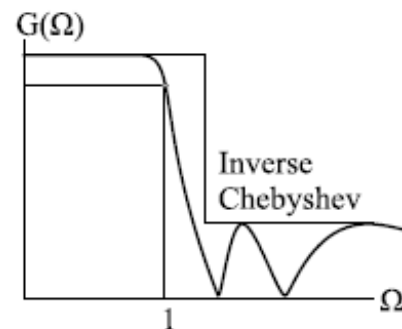


(c)

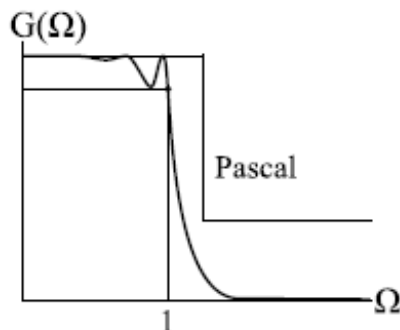

(d)

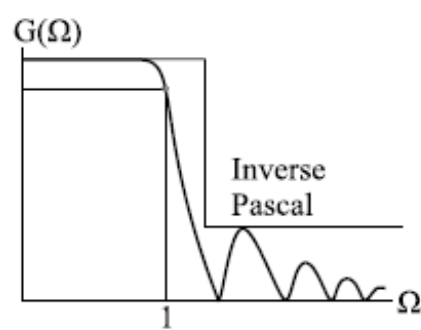

(e)

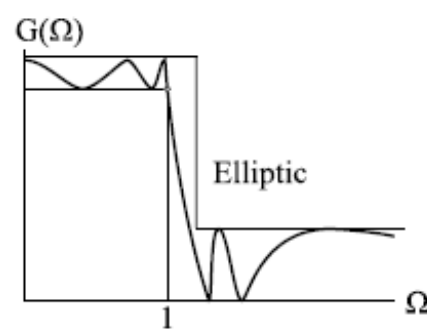

(f)

transfer function

$$H(s) = \frac{k}{D(s)} = \frac{k}{s^N + B_{N-1}s^{N-1} + \dots + B_1s + B_0}$$

where $D(s)$ is in general a polynomial in s of degree N :

$$s_p = -c \quad (c > 0)$$

acceptable of poles

$$s_p = -a \pm jb, \text{ with negative real part}$$

general form of the magnitude response of
all-pole lowpass filters

$$|H(j\Omega)| = \frac{|k|}{\sqrt{1 + [|D(j\Omega)|^2 - 1]}} = \frac{|k|}{\sqrt{1 + Q(\Omega)}} \quad G(\Omega) = |H(j\Omega)| = \frac{H_o}{\sqrt{1 + P_a(\Omega)}}$$

$$G(\Omega) = |H(j\Omega)| = \frac{H_o}{\sqrt{1 + P_a(\Omega)}}$$



$$G(\Omega) = \frac{H_o}{\sqrt{1 + \gamma^2 P_N^2(\Omega)}}$$

with $P_N(\Omega)$ being the *approximating polynomial* (complete even or odd) and γ a design parameter.

1. Sarma M. S. Introduction to electrical engineering. – New York : Oxford University Press, 2001. – C. 715-716.
2. Boylestad, Robert L. Electronic devices and circuit theory / Robert L. Boylestad, Louis Nashelsky.—11th ed.
3. ISBN 978-0-13-262226-4 Scherz P., Monk S. Practical electronics for inventors. – McGraw-Hill Education, 2016.
4. Horowitz, Paul, and Winfield Hill. "The Art of Electronics. 3rd." *New York, NY, USA: University of Cambridge* (2015).
5. All about circuits (<https://www.allaboutcircuits.com/>)
6. <https://www.electronics-tutorials.ws/>
7. <https://en.wikipedia.org/>

The background features a dark gray grid pattern. In the top right and bottom left corners, there are decorative wavy lines in a bright purple color, creating a modern, tech-like aesthetic.

iTMO

Thank you for your attention!